 


# Basic Electrical Properties of MOS Circuits

- Basic MOS operation and equations
- Small-signal characteristics
- Complementary CMOS inverter (DC characteristics)
- Noise Margin
- Static load inverters and transmission gate

# MOS Transistor Types

- MOS Transistor Symbol







nMOS  
enhancement

nMOS  
depletion

pMOS  
enhancement

- Conduction characteristics for enhancement and depletion mode MOS transistors

— Assuming fixed  $V_{DS}$

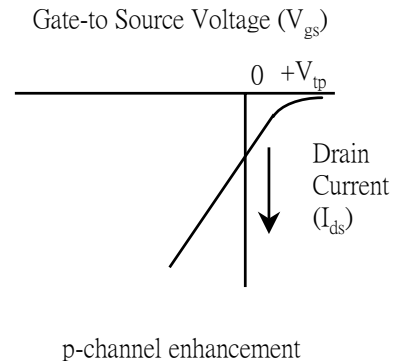 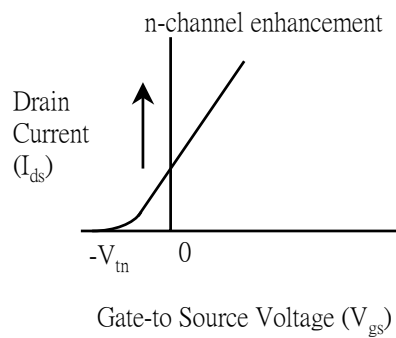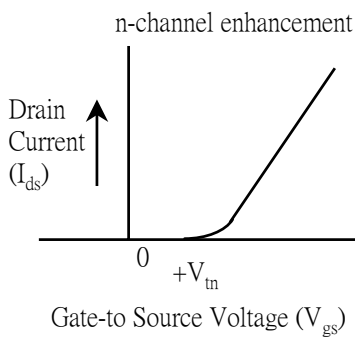


p-channel enhancement


p-channel enhancement
 
# MOS Enhancement Transistor


- Physical structure of a nMOS transistor



 
- 3 modes of transistor channel (nMOS)
  - Accumulation mode



- Depletion mode

 

- Inversion mode


 


- pMOS ( refer to textbook )


# MOS Transistor Operation

## ● Example : n MOS


1.  $V_{gs} > V_t, V_{ds} = 0$

  

 
2.  $V_{gs} > V_t, V_{gs} - V_{ds} = V_{gd} > V_t$



 3.  $V_{gs} > V_t, V_{gs} - V_{ds} = V_{gd} < V_t$




## ● I-V characteristic of nMOS

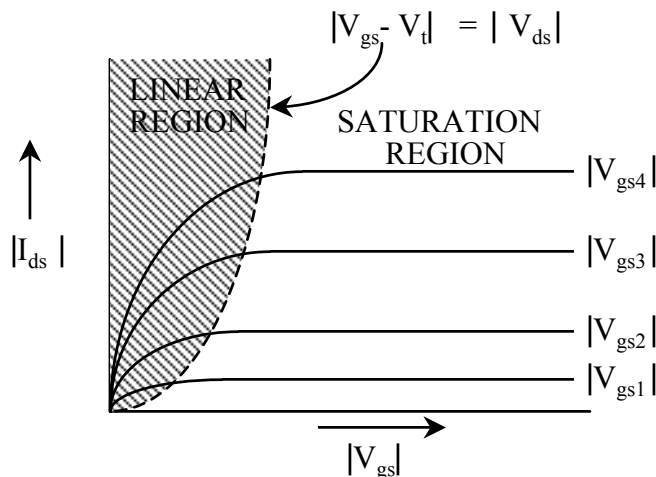
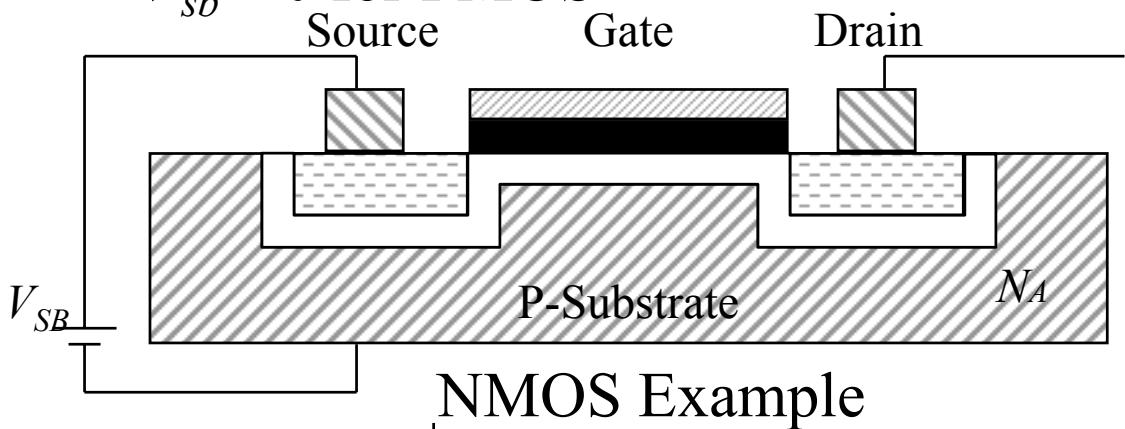
# Body Effect

- Threshold voltage is increased when back bias voltage is increased
- Junction between channel (or drain&source) and substrate must be reverse-biased to reduce current leakage

—  $V_{sb} > 0$  for NMOS  
 $V_{sb} < 0$  for PMOS



- Example
  - with body effect
  - without body effect

- $V_t = V_{fb} + 2\phi_b + \frac{\sqrt{2\epsilon_{si}qN_A(2\phi_b + |V_{sb}|)}}{C_{ox}}$

$$V_t = V_{t0} + \gamma [\sqrt{(2\phi_b + |V_{sb}|)} - \sqrt{2\phi_b}]$$

$$\gamma = \frac{t_{ox}}{\epsilon_{ox}} \sqrt{2\epsilon_{si}qN_A} = \frac{1}{C_{ox}} \sqrt{2\epsilon_{si}qN_A}$$

$V_{fb}$  : flat-band voltage       $\epsilon_{ox}$  : permittivity of gate oxide

$\phi_b$  : Fermi potential


$V_{sb}$  : substrate bias

$V_{t0}$  :  $V_t$  for  $V_{SB}=0$

$N_A$  : substrate doping concentration

# MOS Device Equation

## ● NMOS Transistor Structure

 

## ● $I_{DS}$ VS. $V_{DS}$ Relationship

$$I_{DS} = \frac{\text{charge induced in channel}(Q_c)}{\text{electron transit time}(\tau)}$$

$$\text{Transit time } \tau_{DS} = \frac{\text{length of channel}(L)}{\text{velocity}(v)}$$

$$\text{Velocity } v = \mu E_{DS}$$

where  $\mu$  is electron or hole mobility

$E_{DS}$  is electric field

$$E_{DS} = \frac{V_{DS}}{L}$$

$$\tau_{DS} = \frac{L^2}{\mu V_{DS}}$$

# MOS DEVICE Equation(Cont.)

## ● Nonsaturation Region

Eg: Average electric field  
(gate to channel)

$\epsilon$ : permittivity of insulator between gate and channel

$$E_g = \frac{(V_g - V_t) - V_{DS} / 2}{t} ; \text{ Assume average channel voltage } V_{DS} / 2$$

t: oxide thickness

$$Q_c = \frac{\epsilon W L}{t} \left[ (V_{gs} - V_t) - \frac{V_{DS}}{2} \right]$$
$$I_{DS} = \frac{\mu \epsilon}{t} \frac{W}{L} \left[ (V_{gs} - V_t) - \frac{V_{DS}}{2} \right] V_{DS}$$
$$= \mu C_{ox} \frac{W}{L} \left[ (V_{gs} - V_t) - \frac{V_{DS}}{2} \right] V_{DS}$$

$C_{ox}$ : gate capacitance/unit area

Total gate capacitance  $C_g = C_{ox} W L$

$$\text{Let } K = \mu C_{ox} \text{ or } \beta = K \frac{W}{L} = \frac{\mu C_{ox} W}{L}$$

$$\Rightarrow I_{DS} = K \frac{W}{L} \left[ (V_{gs} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$$
$$= \beta \left[ (V_{gs} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

# MOS Device Equation(Cont.)

## ● Saturation Region



$$V_{DS} = V_{GS} - V_t$$

$$I_{DS} = \frac{k}{2} \frac{W}{L} (V_{GS} - V_t)^2 = \frac{\beta}{2} (V_{GS} - V_t)^2$$

$\lambda$  : channel length modulation factor

If we include  $\lambda$ , then
 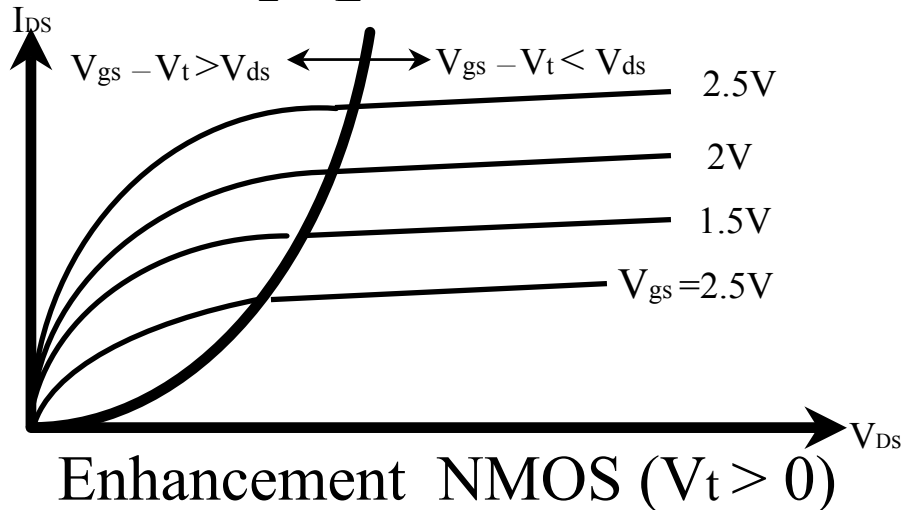
$$I_{DS} = \frac{k}{2} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$



## ● Cutoff Region

$$V_{GS} < V_t \Rightarrow I_{DS} = 0$$



# MOS Device Equation(Continued)

1. Cutoff Region  $V_{gs} - V_t < 0$

2. Nonsaturation  $0 < V_{ds} < V_{gs} - V_t$

3. Saturation  $0 < V_{gs} - V_t < V_{ds}$

$$I_{DS} = \begin{cases} 1. 0 \\ 2. \beta[(V_{gs} - V_t)V_{DS} - \frac{V_{DS}^2}{2}] \\ 3. \frac{\beta}{2} (V_{gs} - V_t)^2 \end{cases}$$

## ● Channel-length modulation

— Device in saturation

$$I_{DS} = \frac{\beta}{2} (V_{gs} - V_t)^2 (1 + \lambda V_{DS})$$

# Subthreshold Region

- i.e. weak inversion region

$$0 < V_{gs} < V_t$$

## Drain Puchthrough


When the drain is at a high enough voltage with respect to the souce, the depletion region around the drain may extend to the source, thus causing current to flow irrespective of the gate voltage( i.e., even if it is zero). This is known as a punchthrough condition. Currently, this effect is used in I/O protection circuits to limit the voltages across internal circuit nodes, although it will impact design as devices are scaled down by requiring that internal circuit voltages be reduced to a point where the effect does not occur.

## MOS Models

refer to textbook

## Small Signal AC Characteristics

- small signal model

 

# Transconductance $g_m$

- $g_m = \left. \frac{d I_{DS}}{d V_{GS}} \right|_{V_{DS} = \text{constant}}$

- For devices in saturation region

$$g_m = \frac{d I_{DS}}{d V_{GS}} = \frac{C_g \mu}{L^2} (V_{gs} - V_t); C_g = C_{ox}WL$$



$$= \beta (V_{gs} - V_t)$$

- For devices in nonsaturation region

$$g_m = \beta V_{DS}$$



- With fixed  $V_{ds}$

- With fixed  $V_{gs} > V_t$

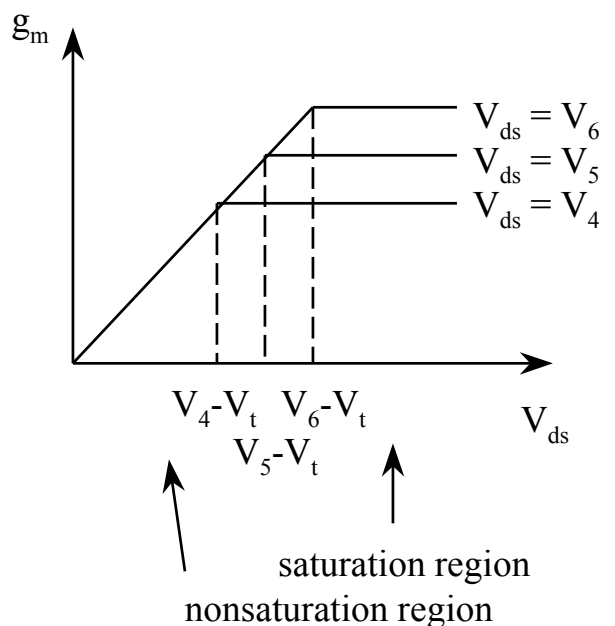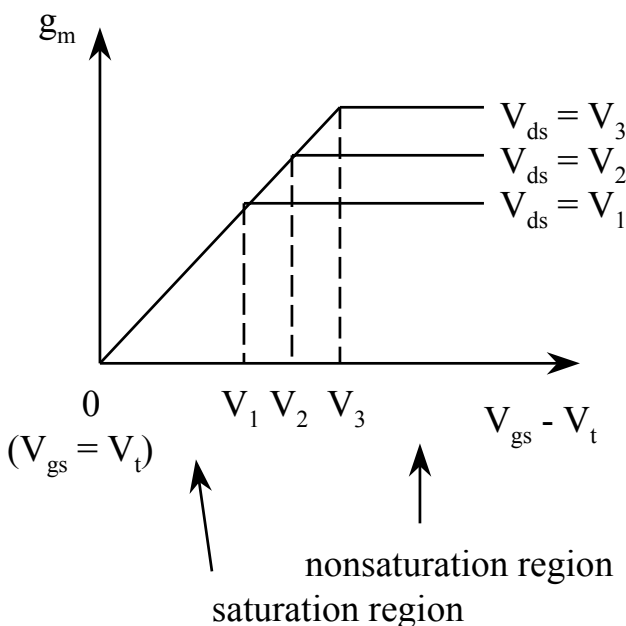


# Indication of Frequency Response

- Large signal

  


- Small signal model

 

$$V_o = -g_m V_i \left( r_0 \parallel \frac{1}{sC_L} \right)$$
 
$$\frac{V_o}{V_i} = \frac{-g_m r_0}{1 + sr_0 C_L} = \frac{-g_m r_0}{1 + j\omega r_0 C_L}$$



$$\left| \frac{V_o}{V_i} \right| = 1 \implies \omega_u = \frac{g_m}{C_L}$$

↑  
Assume  $g_m r_0 \gg 1$

- $\omega_u = \frac{g_m}{C_g} = \frac{\mu}{L^2} (V_{gs} - V_t)$

Assume  $C_L = C_g$  i.e. ability to drive itself

# Output Resistance

- Nonsaturation

- Small signal

$$g_0 = \left. \frac{dI_{DS}}{dV_{DS}} \right|_{V_{DS} \text{ small}} \approx \beta(V_{GS} - V_t)$$

- Large signal  $G_0 = \frac{I_{DS}}{V_{DS}} \approx \beta(V_{GS} - V_t)$

$$\Rightarrow \underset{\parallel}{R_0} = \underset{\parallel}{r_0} = \frac{1}{\beta(V_{GS} - V_t)}$$


$$\frac{1}{G_0} \quad \frac{1}{g_0}$$

- Saturation Region

- \*Only small signal


$$g_0 = \frac{dI_{DS}}{dV_{DS}} = \lambda I$$

$$r_0 = \frac{1}{\lambda I}$$

 
 
# Complementary CMOS Inverter

- A MOS inverter with substrate connections




- Relations between voltages for the three regions of operation of a CMOS inverter


	CUTOFF	NONSATURATED	SATURATED
p-device	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$
n-device	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{dsn} < V_{gs} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{dsn} > V_{gs} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

# Graphical Derivation of CMOS Inverter Characteristics


● transistor I-V

 

● Taking absolute value of  $I_{dsp}$

 


● Load line

 

# CMOS Inverter DC Transfer Characteristic and Operating Regions

- Transfer curve

 

- 5 regions (A, B, C, D, and E)

- In all of five regions,  $I_{dsn} = -I_{dsp}$
- Region A

$$V_{out} = V_{DD}$$

nMOS: off

pMOS: nonsaturation (triode) region



Region B: n: saturation p: nonsaturation

$$I_{dsp} = \frac{\beta_n}{2} (V_{in} - V_{tn})^2$$

$$I_{dsp} = -\beta_p \left[ \underbrace{(V_{in} - V_{DD} - V_{tp})}_{V_{gsp}} \underbrace{(V_O - V_{DD})}_{V_{dsp}} - \frac{1}{2} (V_O - V_{DD})^2 \right]$$

$$I_{dsn} = -I_{dsp}$$

$$\Rightarrow V_O = \left[ (V_{in} - V_{tp}) + \left[ (V_{in} - V_{tp})^2 - 2 \left( V_{in} - \frac{V_{bb}}{2} - V_{tp} \right) V_{DD} - \frac{\beta_n}{\beta_p} (V_{in} - V_{tn})^2 \right]^{1/2} \right] \frac{\beta_n}{\beta_p}$$

Region C: Both the n and p-device are in saturation

$$I_{dsp} = \frac{\beta_p}{2} (V_{in} - V_{DD} - V_{tp})^2$$

$$I_{dsp} = \frac{\beta_n}{2} (V_{in} - V_{tn})^2$$

$$I_{dsp} = -I_{dsn}$$

$$\Rightarrow V_{in} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$



By setting  $\beta_n = \beta_p$  and  $V_{tn} = -V_{tp}$

$\Rightarrow V_{in} = \frac{V_{DD}}{2} = V_O = V_{inv}$  where  $V_{inv}$  is gate threshold voltage

Region D & E can be similarly derived

# Noise Margin

## ● Definitions

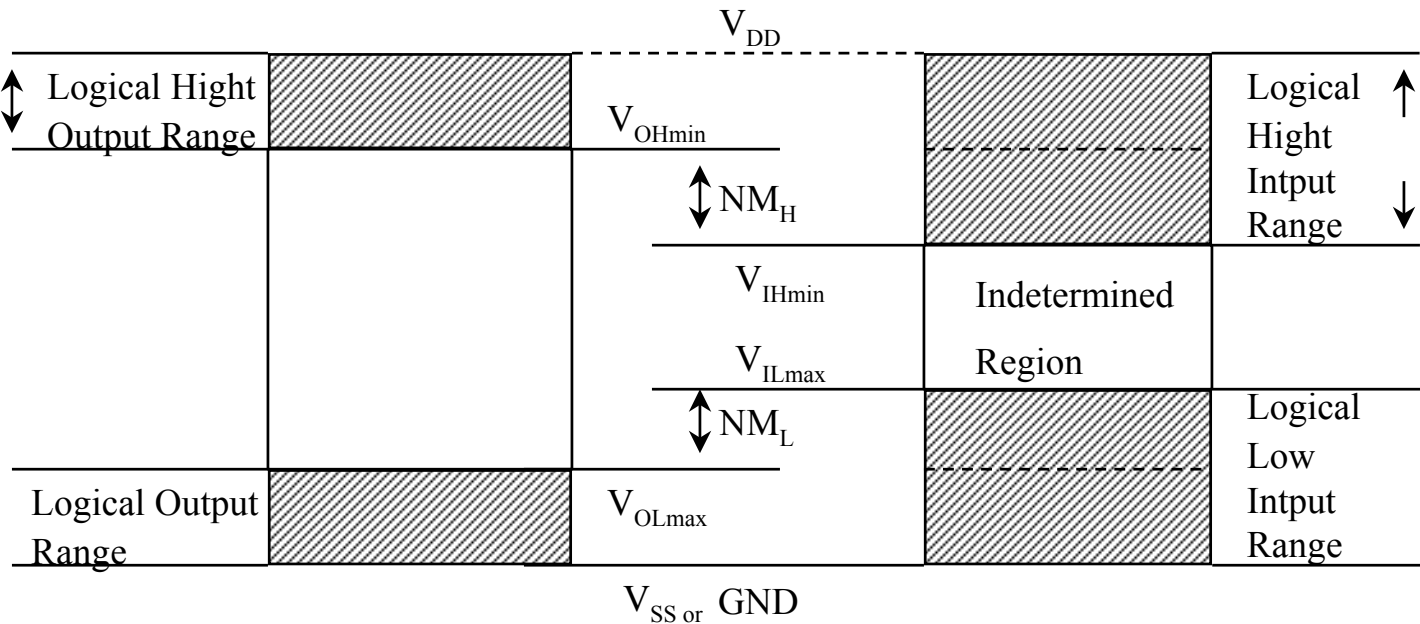 

$$NM_L = | V_{ILmax} - V_{OLmax} |$$

$$NM_H = | V_{OHmin} - V_{IHmin} |$$


$V_{IHmin}$  = Minimum HIGH input voltage

$V_{ILmax}$  = Maximum LOW input voltage

$V_{OHmin}$  = Minimum HIGH output voltage


$V_{OLmax}$  = Maximum LOW output voltage

## ● CMOS inverter noise margin

 

 
# Influence of $\beta_n/\beta_p$ Ratio on Transfer Curve

- Transfer curves for different  $\beta_n/\beta_p$  ratio



- For  $\frac{\beta_n}{\beta_p} = 1 \implies \frac{\mu_p W_p}{L_p} = \frac{\mu_n W_n}{L_n}$   
 $\implies \frac{(W_p/L_p)}{(W_n/L_n)} = \frac{\mu_n}{\mu_p} \approx 2 \sim 3$

- Noise Margin


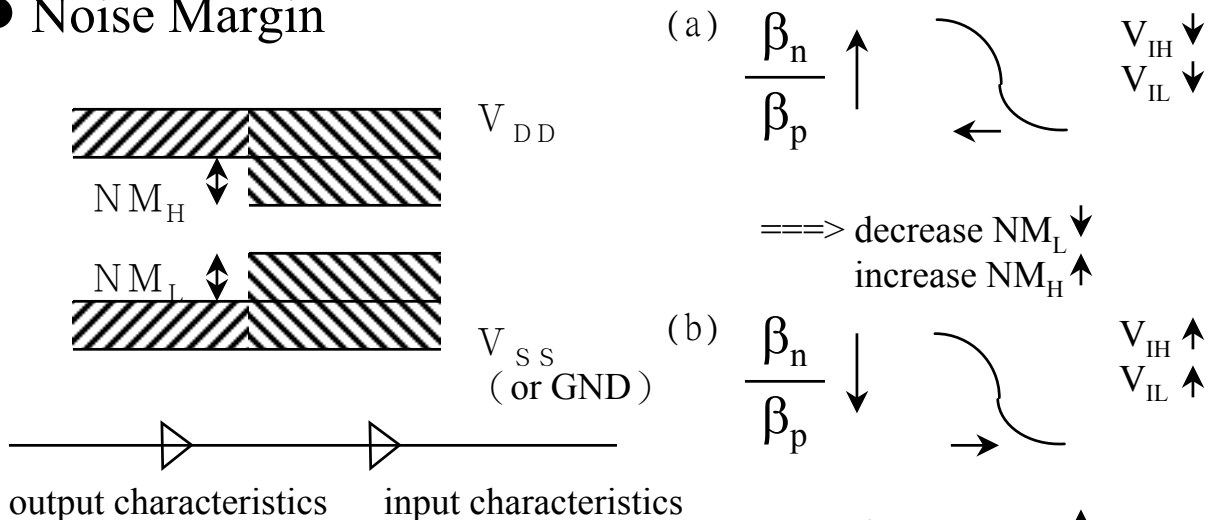


- For equal noise margins,  $NM_H = NM_L$

$$V_{inv} = 0.5V_{DD}$$

# CMOS Inverter As An Amplifier

## ● Schematic

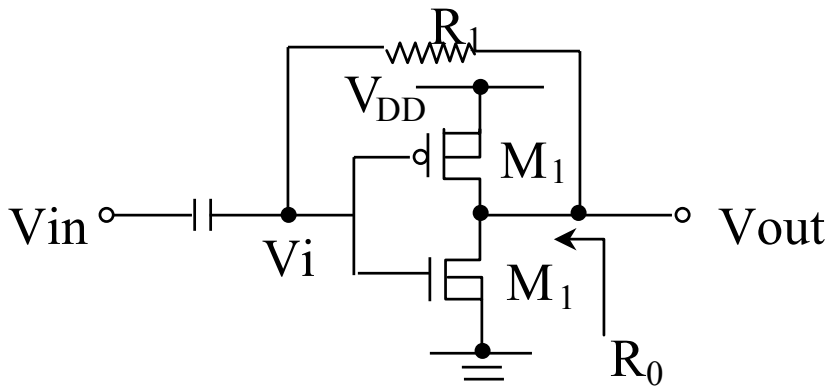 

- DC bias:  $V_i = V_{out} = V_{inv}$ .
- both  $M_1$  and  $M_2$  are biased in saturation region
- Assuming  $R_1 \gg R_0$ ,  $C$  is large enough


$$A = \frac{V_{out}}{V_{in}} \approx \frac{V_{out}}{V_i} \approx G_m R_0 = (g_{mn} + g_{mp})(r_{dsn} \parallel r_{dsp})$$

- Increase channel length  $\Rightarrow$   $\left\{ \begin{array}{l} R_0 \nearrow \Rightarrow A \nearrow \\ W_u \searrow \Rightarrow \text{speed} \searrow \end{array} \right.$

$$\left( \begin{array}{l} \lambda \sim 1/L, R_0 \sim 1/\lambda \Rightarrow R_0 \sim L \\ W_u \sim 1/L^2 \Rightarrow \text{speed} \sim 1/L^2 \end{array} \right)$$
 
# Pseudo - nMOS Inverter

- Roughly equivalent to nMOS depletion load inverter  
— consumes more power than CMOS



- $V_{in} = \text{logic } 0 \Rightarrow V_{out} \approx V_{DD}$

- $V_{in} = \text{logic } 1$

$$\frac{\beta_n}{2} (V_{in} - V_{tn})^2 = \beta_p \left[ (-V_{DD} - V_{tp})(V_{out} - V_{DD}) - \frac{(V_{out} - V_{DD})^2}{2} \right]$$



$$\Rightarrow \frac{\beta_n}{\beta_p} = \frac{(V_{DD} + V_{tp})^2 - (V_{out} + V_{tp})^2}{(V_{in} - V_{tn})^2}$$

— with  $V_{inv.} = 0.5V_{DD}$ ,  $V_{tn} = |V_{tp}| = 0.2V_{DD}$ ,  $V_{DD} = 5V$

$$\Rightarrow \frac{\beta_n}{\beta_p} = 6$$

$$(1) \text{ for } \frac{\mu_n}{\mu_p} = 2 \Rightarrow \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p} = 3$$

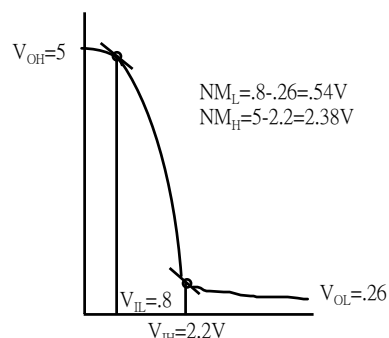 
$$(2) \text{ for } \frac{\mu_n}{\mu_p} = 3 \Rightarrow \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p} = 2$$




- In general,  $NM_H > NM_L$

# nMOS Depletion Load Inverter


- Schematic

 


- Load line

 

- Consumes more power than CMOS

 

- Transfer curve

 

- Transistor size

– Assuming  $V_t \cong 0.2V_{DD}$ ,  $V_{td} \cong -0.6V_{DD}$


$$I_{ds(pu)} = \frac{k}{2} \frac{W_{pu}}{L_{pu}} (-V_{td})^2 = \beta_{pu} (-V_{td})^2$$

$$I_{ds(pd)} = \frac{k}{2} \frac{W_{pd}}{L_{pd}} (V_{inv.} - V_{td})^2 = \beta_{pd} (V_{inv.} - V_{td})^2$$


– For  $V_{inv} \cong 1/2 V_{DD}$ ,  $\frac{W_{pu}/L_{pu}}{W_{pd}/L_{pd}} = \frac{1}{4}$  or  $\frac{1/4}{1/1}$

# Transmission Gate

- Schematic

 


- Resistance ( $\phi=High$ )

 


- Signal transmission


— nMOS pass transistor

 

— pMOS pass transistor

 


— Transmission gate

 

# Transmission Gate (cont.)


- Cascaded stage

— nMOS

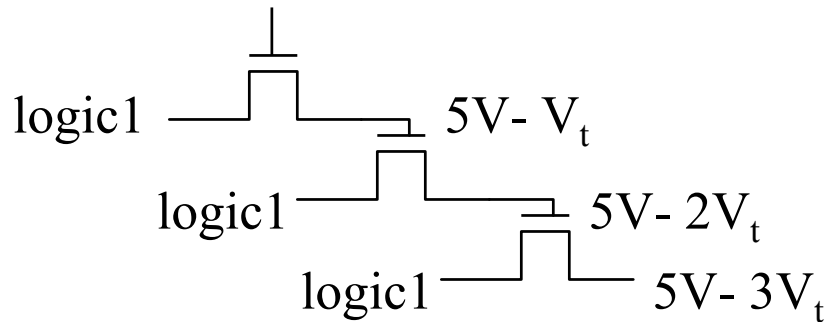

( loss of logic level 1)

— pMOS

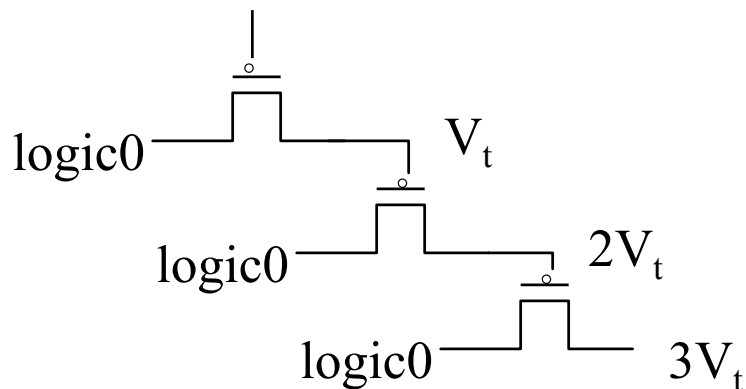

( loss of logic level 0)


— Transmission gate

good logic levels





# Tristate Inverter

- Symbol

 


- Schematic

  


- $C=1, \bar{C}=0 \implies$  inverter function  $Z=\bar{A}$
- $C=0, \bar{C}=1 \implies$  high impedance output  $Z$

- Improved type

 

eliminated metal connection

 

- eliminate a metal connection
- $\implies$  smaller size & higher speed

## Other Inverter Types

Reading Assignment