

CMOS Logic Gate Design

- To achieve correct operation of any integrated logic gate, both functional and timing constraints have to be satisfied.
- The following effects can result in incorrect functioning
 - Incorrect or insufficient power supplies, or power supply noise
 - Noise on gate inputs
 - Faulty transistors
 - Faulty connections to transistors
 - Incorrect ratios in ratioed logic
 - Charge sharing or incorrect clocking in dynamic gates
- Critical paths
 - slowest paths in a logic design
 - speed optimization is required
 - can be affected at four main levels
 1. architecture level
 2. RTL/logic gate level
 3. circuit level
 4. layout level
 - The most leverage is achieved by completing a good architecture, i.e. designing the overall function in the most efficient manner at the highest level possible.
(No amount of skillful logic design can overcome a poor architecture)
 - Once the logic level has been decided, the circuit level of design can be used to optimize a critical speed path. This may be done by sizing transistors or using other styles of CMOS logic
 - Finally, one can affect the speed of a set of logic by rearranging the physical layout.

Fan-In and Fan-Out

- Fan-in affects gate speed
e.g. If two identical transistors are connected in series, the rise (or fall)time will be approximately double that for a single transistor with the same capacitive load

- Fan-out
The capacitive load of a gate is usually determined by the number of its fan-out

- For an m-input NAND gate

1. Equal-sized gate (The gate sizes of p and n-transistors are the same)

— worst-case rise time t_r (only one p-device is on)

$$t_r = \frac{R_p}{n} (mnC_d + C_r + C_g)$$

R_p = the effective resistance of p-device in a minimum-sized inverter

n = width multiplier for p-device in this gate

k = the fan-out(in units of minimum-sized inverters)

m = fan-in of gate

C_g = gate capacitance of a minimum-sized inverter

C_d = source/drain capacitance of a minimum-sized inverter

C_r = routing capacitance

— This can be reformulated as

$$t_r = \frac{R_p}{n} (mnrC_g + q(k)C_g + kC_g)$$

$$= \frac{R_p C_g}{n} (mnr + q(k) + k)$$

$$= R_p C_g mr + \frac{R_p C_g}{n} q(k) + \frac{R_p C_g}{n} k$$

where

$t_r = C_d / C_g$, the ratio of the intrinsic drain capacitance of an inverter to the gate capacitance, $q(k)$ = a function of the fan-out representing the routing capacitance as a multiplier times the gate capacitance.

- ※ $\left(\begin{array}{l} \text{Larger } n \Rightarrow \begin{array}{l} 1. \text{ The latter two terms become smaller} \\ 2. \text{ Higher cost (I.e. larger size)} \\ 3. \text{ Heavier capacitive load for the anterior stage} \end{array} \end{array} \right)$

The above equation is of the form

$$t_r = t_{\text{internal-r}} + k * t_{\text{output-r}}$$

where $t_{\text{internal-r}} = R_p C_g m r$

$$t_{\text{output-r}} = \frac{R_p C_g}{n} \left(1 + \frac{q(k)}{k} \right)$$

Similarly, the fall time, t_f , is approximated by

$$\begin{aligned} t_f &= m \frac{R_n}{n} (mnrC_g + q(k)C_g + kC_g) \\ &= R_n C_g m^2 r + mk \frac{R_n C_g}{n} \left(1 + \frac{q(k)}{k} \right) \\ &= t_{\text{internal-f}} + k * t_{\text{output-f}} \end{aligned}$$

where R_n = the effective resistance of
a minimum-sized n-device

2. Equal-delay method (where rise and fall times are equalized)

$$\begin{aligned} t_r &= t_f \\ \implies \frac{R_p}{n} (mnrC_g + q(k)C_g + kC_g) &= m \frac{R_n}{n} (mnrC_g + q(k)C_g + kC_g) \\ \implies R_p &= mR_n \\ \implies \left[\left(\frac{W}{L} \right)_p \mu_p \right]^{-1} &= m \left[\left(\frac{W}{L} \right)_n \mu_n \right]^{-1} \\ \implies W_p &= \frac{W_n}{m} \left(\frac{\mu_n}{\mu_p} \right) \end{aligned}$$

- For an m-input NOR gate
— e.g. equal-sized method

$$\begin{aligned} t_r &= m \frac{R_p}{n} (mnrC_g + q(k)C_g + kC_g) \\ t_f &= \frac{R_n}{n} (mnrC_g + q(k)C_g + kC_g) \dots \end{aligned}$$

only one n-device
is on


Driving Large Fan-out

- Certain logic circuits can have signals that have large capacitive loads due to large fan-out
clocks and reset signals are common examples

● Example

As an example of a simple logic decision consider the implement of an 8-input AND gate driving a 1pF load (for instance, a row decoder in a RAM or ROM), we may use the following(Fig. 5.3):

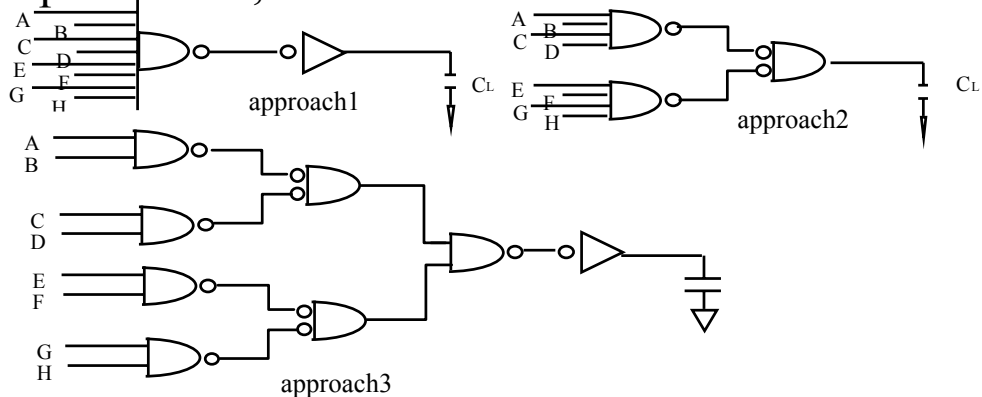- Approach 1--An 8-input NAND and an inverter
- Approach 2--Two 4-input NANDs and a 2-input NOR
- Approach 3--Four 2-input NANDs, two 2-input NORs a 2-input NAND, and an inverter



APPROACH	DELAY(ns) STAGE 1	DELAY(ns) STAGE 2	DELAY(ns) STAGE 3	DELAY(ns) STAGE 4	Total Delay(ns) (SPICE)
1	2.82 ND8 falling	3.37 INV rising			6.2 (6.5)
2	0.88 ND4 falling	4.36 NR2 rising			5.24 (5.26)
3	0.31 ND2 falling	0.4 NR2 rising	0.31 ND2 falling	2.17 INV rising	3.19 (3.46)

- The shortest delay is achieved by approach 3
- Large stage ratio may be required for driving a large output capacitive load(for all 3 approaches)

Guidelines for High-Speed Logic Design

- Use NAND structures where possible.
- Place inverters (or at worst, small fan-in NAND gates) at high fan-out nodes, if possible.
- Avoid the use of NOR structures in high-speed circuits, especially with a fan-in greater than four and where the fan-out is large.
- Use a fan-out below 5-10.
- Use minimum-sized gates on high fan-out nodes to minimize the load presented to the driving gate.
- Keep rising and falling edges sharp.
- When designing with power or area as a constraint, remember that large fan-in complementary gates will always work given enough time.


CMOS Logic Structures

- CMOS complementary Logic


e.g. $F = A \cdot B + C \cdot (D + E)$

— TRANSMIT “1’s”
 
$$F = \overline{(A \cdot B)} \cdot \overline{(C \cdot (D + E))}$$



 
$$F = \overline{(\overline{A} + \overline{B})} \cdot \overline{(C + (\overline{D} \cdot \overline{E}))}$$




— TRANSMIT “0’s” :


$$F = A \cdot B + C \cdot (D + E)$$

 

Pseudo-NMOS Logic

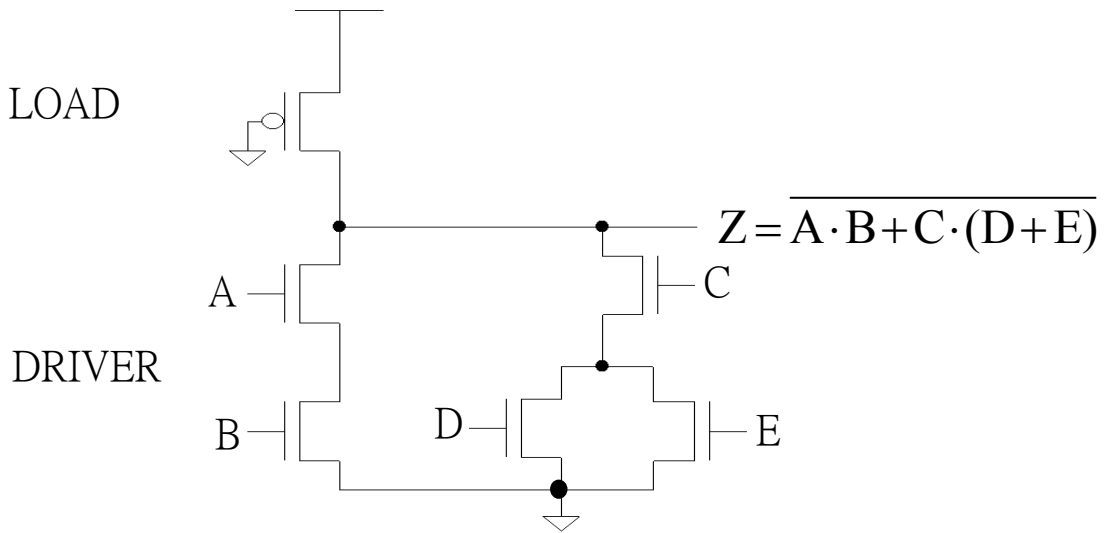

 - PMOS transistor is always ON
 - If NMOS network is OFF
Z is pulled up ; $Z = V_{DD}$
 - If NMOS network is ON
Z is pulled down ; $Z \rightarrow V_{SS}$



$$V_Z = V_{DD} \frac{2R_n}{2R_n + R_p} \quad R \propto \beta^{-1}$$

$$\frac{V_Z}{V_{DD}} = \frac{\frac{2}{\beta_N}}{\frac{2}{\beta_N} + \frac{1}{\beta_P}} = \frac{\frac{2}{\beta_N}}{\frac{2\beta_P + \beta_N}{\beta_N\beta_P}}$$

$$= \frac{2}{\beta_N} \frac{\beta_N\beta_P}{2\beta_P + \beta_N} = \frac{2\beta_P}{2\beta_P + \beta_N}$$

For $V_Z \rightarrow V_{SS}$, $\beta_n \gg \beta_p$

\Rightarrow ratioed transistors $\frac{w_n}{w_p} \gg 1$

$\frac{\beta_n}{\beta_p} \approx 6$ (refer to page 75 of textbook)



- Static P_D when pull-down network is on
- Capacitance load for any input $=C_g$
- If min. size driver transistors are used,
 $L_p > W_p$ to give proper β ratio \implies slower t_r
- Emulates NMOS circuits \implies use of existing base
- Density better than full CMOS
 ($n+1$ transistors VS. $2n$)

Comparisons for N-input CkT

	Full CMOS	pseudo NMOS
C_{IN}	$2C_g$	C_g
#T's	$2N$	$N+1$
t_f	t_f	t_f
t_r	t_r	$>t_r^*$

* depends on CkT

Dynamic CMOS Logic

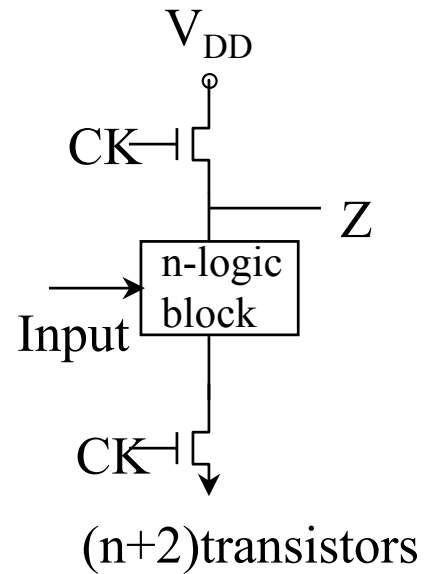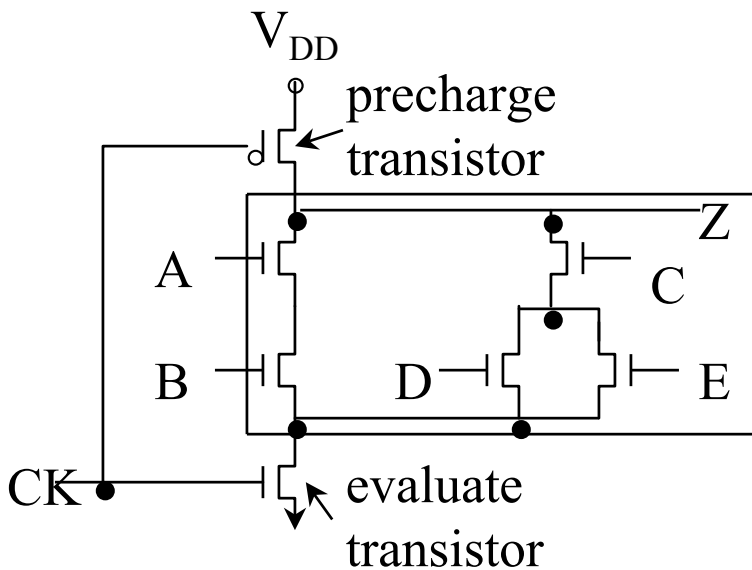

WHEN $\phi = 0$: $Z = \text{HIGH}$, precharge

WHEN $\phi = 1$: stage of n-network is evaluated

if n-network is ON, $Z = \text{LOW}$


if n-network is OFF, Z remains HIGH

$$\Rightarrow Z = \overline{AB + C(D+E)}$$

- For any input, $C_{in} = 1C_g$
- Pull-up time \sim same as pseudo N-MOS
- Pull-down time \uparrow due to evaluate time
- Restriction on inputs to charge only during precharge due to charge redistribution


Simple, Single Phase Dynamic CMOS Gates

- Cannot be cascaded

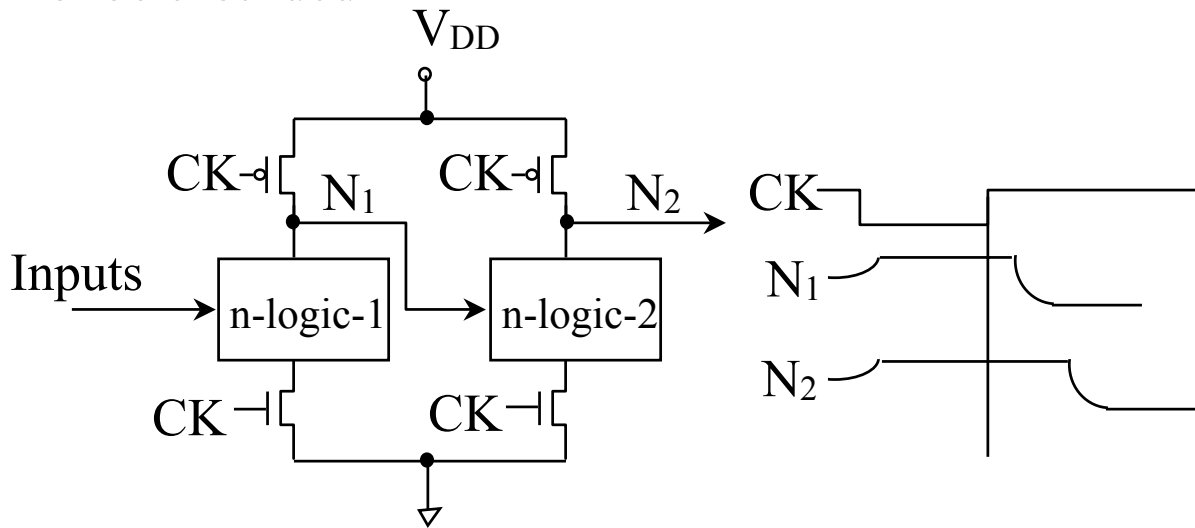

- When the gates are precharged, N_1 and N_2 are charged to V_{DD}
- During evaluate, n-logic-1 will conditionally discharge with some delay due to t
- N_1 must be fully evaluated before N_2 is evaluated; otherwise the output N_2 will be in error
- This cannot be assured with single-phase clocks
- These problems can be overcome by using multi-phase clocks and a sample and hold circuit to isolate cascaded stages and control evaluate timing


Example

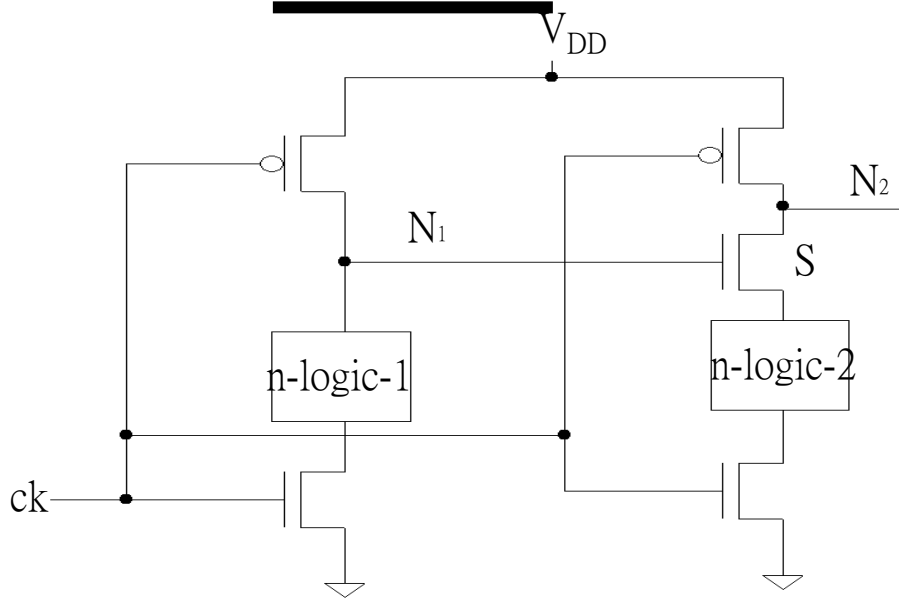

- During precharge, N_1 is automatically high and S is automatically ON
- Suppose that n-logic-1 is ON and n-logic-2 is ON
 - Immediately after precharge ends, N_2 will tend to be pulled down until N_1 is pulled down by n-logic-1 thereby turning S OFF
- To make cascaded stages (single phase clock) ok, S should be OFF until it is conditionally turned ON (by N_1)
 - Can do this by inserting an inverter between N_1 and $S \Rightarrow$ domino logic


CMOS DOMINO LOGIC

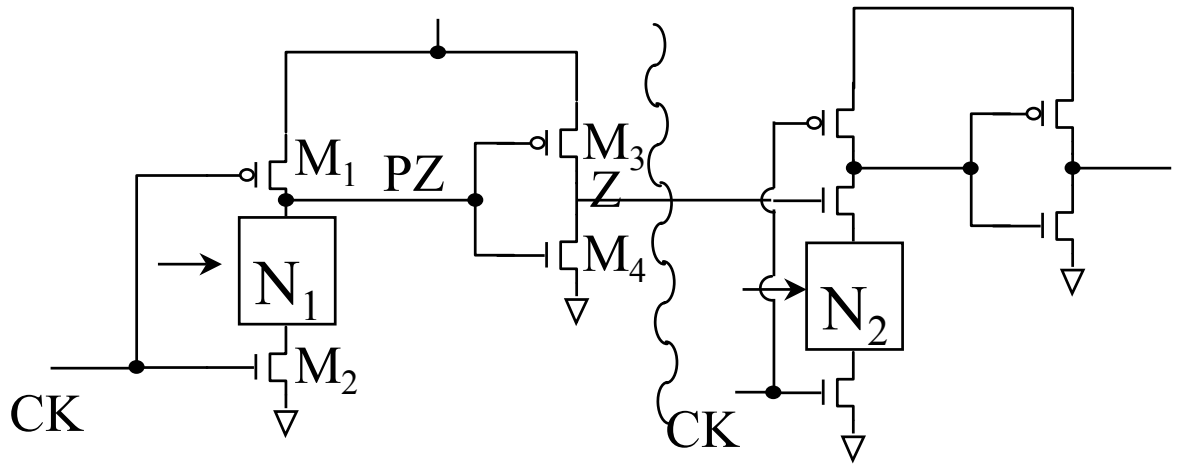- Incorporate a static (non-clocked) buffer(inverter) into each dynamic logic gate



$CK=0:$	M_1 on M_2 off	M_3 off M_4 on	PZ precharged HIGH Z precharged LOW
$CK=1:$	M_1 off M_2 on	? ?	<u>evaluate</u> $Z=PZ \implies$ causes next stage to evaluate

Example

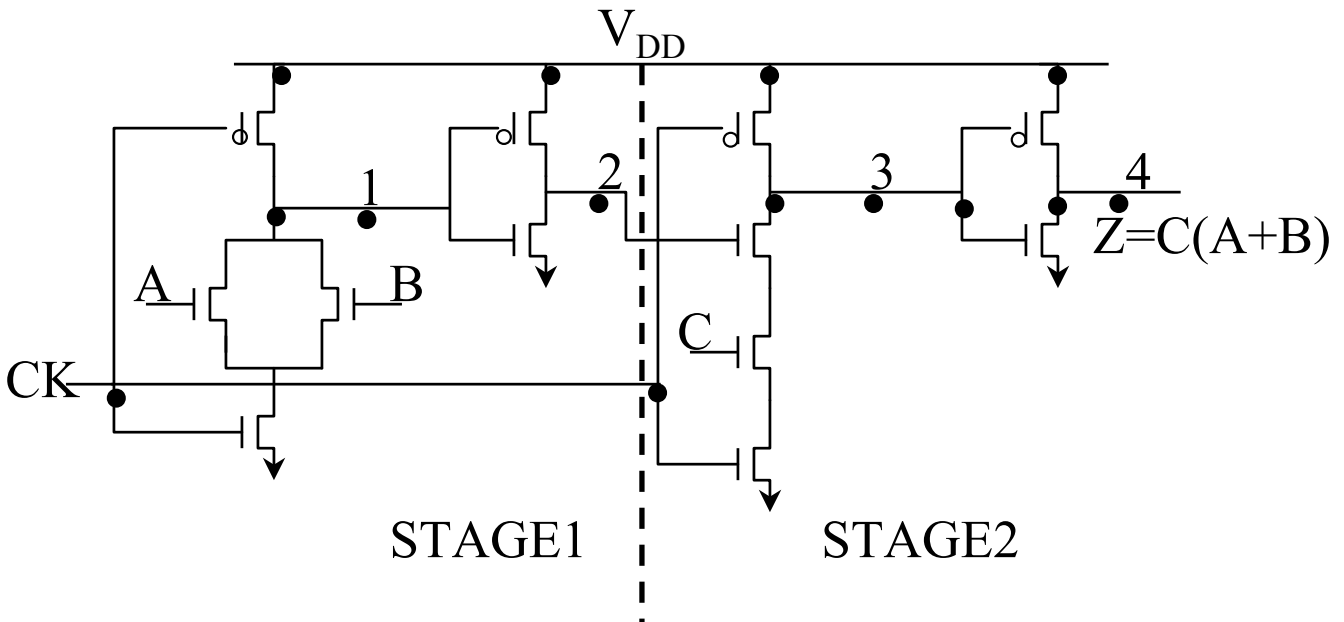

- Precharge: CK \rightarrow LOW
 — A,B,C, don't care

NODE 1 \rightarrow HIGH
 2 \rightarrow LOW
 3 \rightarrow HIGH
 4 \rightarrow LOW

PROPOGATION
 “DOMINOS”


- Evaluate: CK \rightarrow HIGH
 — Assume A=B=1 and C=0

1 \rightarrow LOW
 2 \rightarrow HIGH
 3 \rightarrow HIGH (C=0)


- ASSUME A=B=1 and C=1
- 4 \rightarrow LOW
 3 \rightarrow LOW
 4 \rightarrow HIGH

CMOS Domino Logic (Cont.)

● Static version

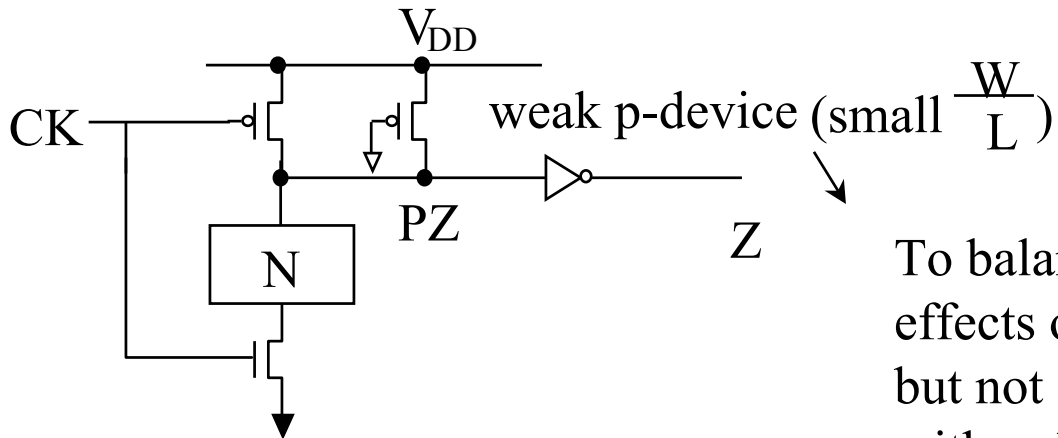


● Latched version

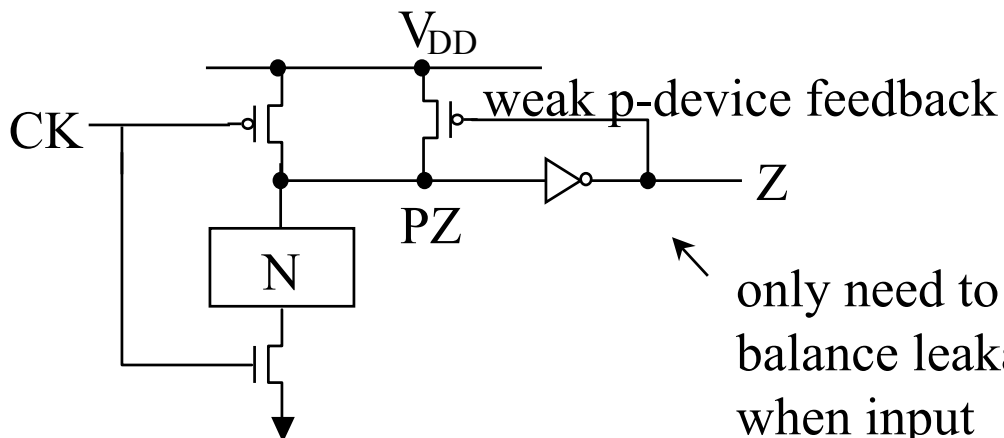

\therefore feedback only turns on weak p-device when inverter output is 0, and input is high

NP Dominio Logic (Zipper CMOS)

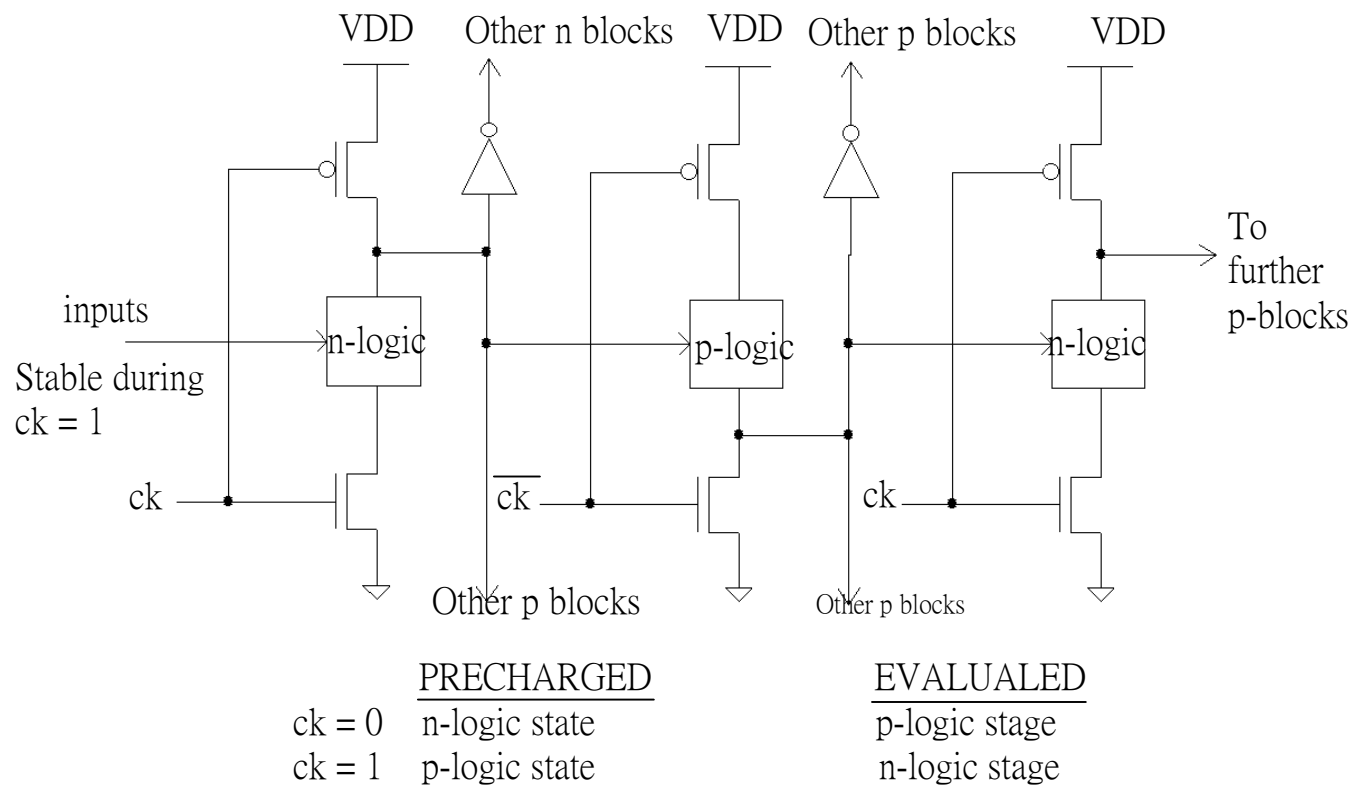- Buffer removed
- Cascaded logic blocks are alternate, p-logic and n-logic



- Advantages
 1. One clock
 2. No buffers
- Disadvantages
 1. Speed of p-blocks
 2. Charge sharing
(decreased noise margin)