

Subsystems Design

- Adder
- Counters
- Multipliers
- Memories
- PLAs
- Finite state machines

Adders

- Combinational adder
- Dynamic combinational adder
- Transmission gate adder
- Carry lookahead adder
- Manchester carry adder
- Binary lookahead adder
- Carry select adder

Combinational Adder


● Adder truth table

C	A	B	A B(G)	A+B(P)	A⊕B	SUM	CARRY
0	0	0	0	0	0	0	0
0	0	1	0	1	1	1	0
0	1	0	0	1	1	1	0
0	1	1	1	1	0	0	1
1	0	0	0	0	0	1	0
1	0	1	0	1	1	0	1
1	1	0	0	1	1	0	1
1	1	1	1	1	0	1	1


$$\text{SUM} = ABC + \overline{A}BC + A\overline{B}C + A\overline{B}\overline{C}$$

$$\text{CARRY} = AB + AC + BC = AB + C(A+B) = G + CP$$

● Logic gate

 


● Circuit Diagram

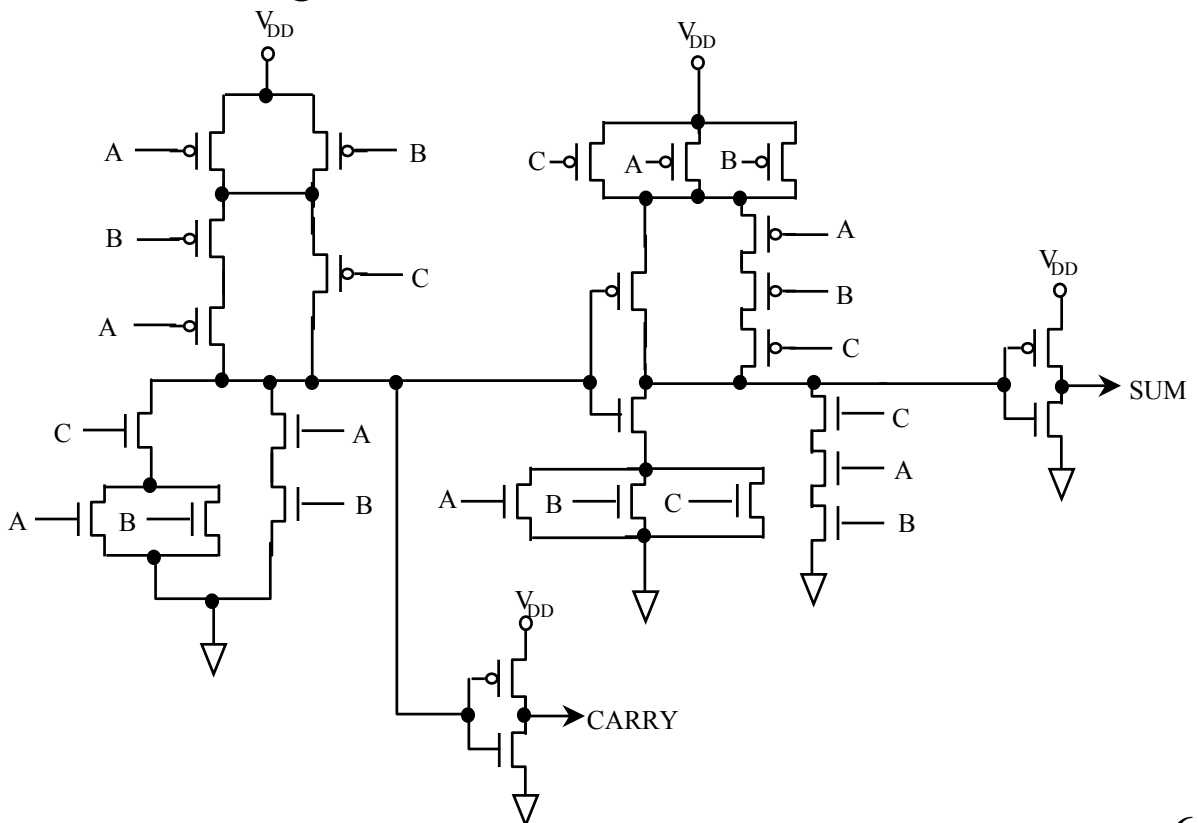

N-Bit Combinational Adder

● Ripple carry adder

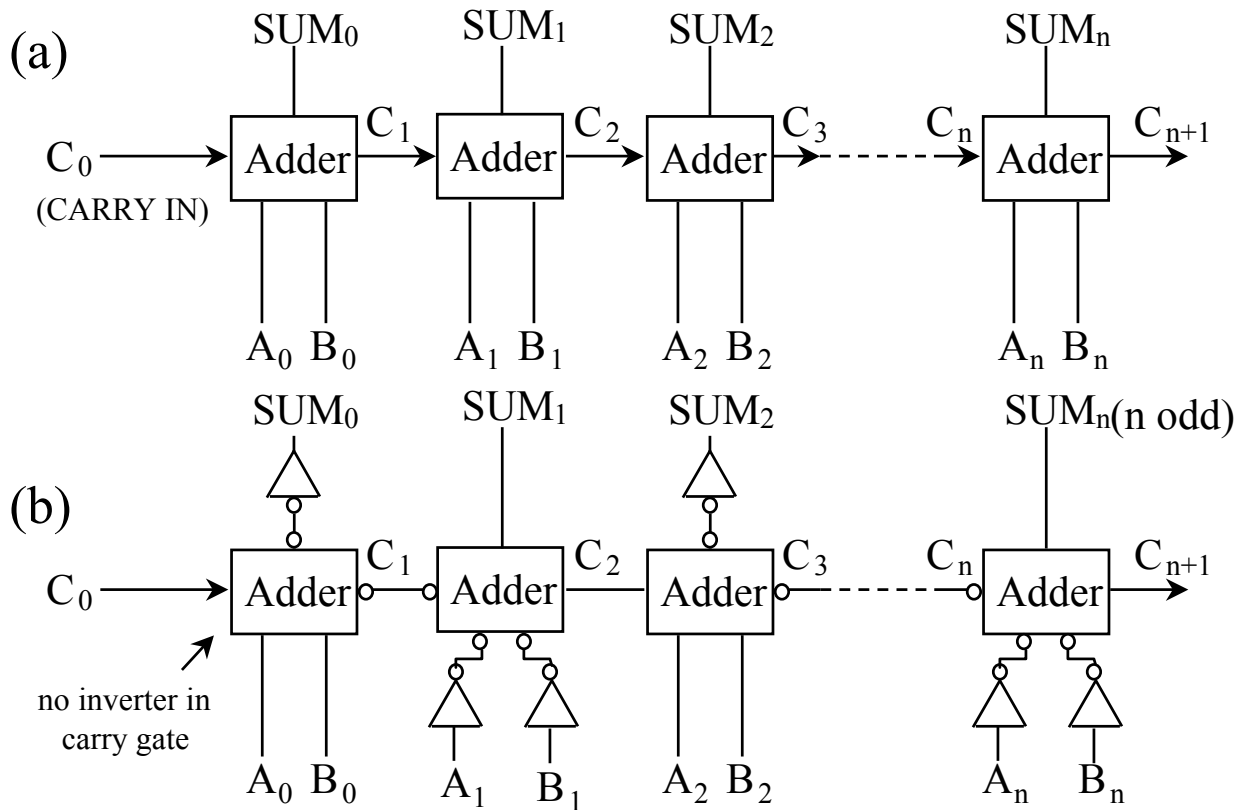


(a): long carry delay ($C_0 \longrightarrow C_{n+1}$)

(b): using inverter logic to shorten
carry delay ($C_0 \longrightarrow C_{n+1}$)

(The inverter at the carry output is omitted)


● Serial adder

- low cost
- low speed

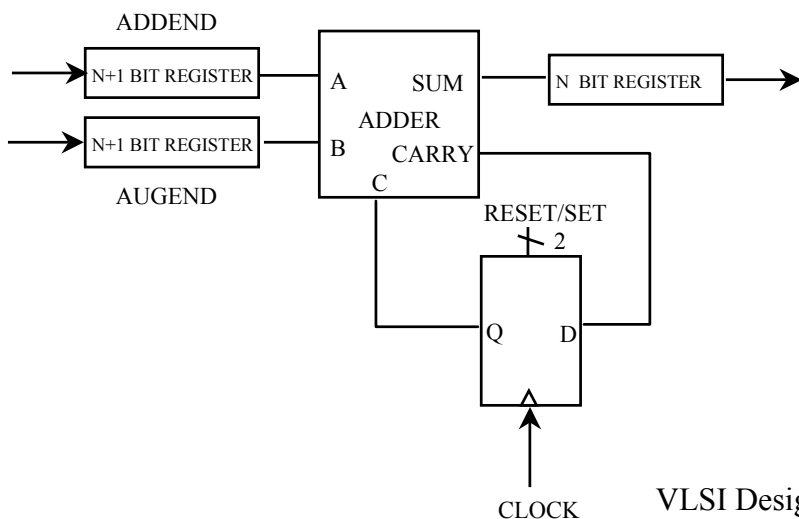


Dynamic Combinational Adder

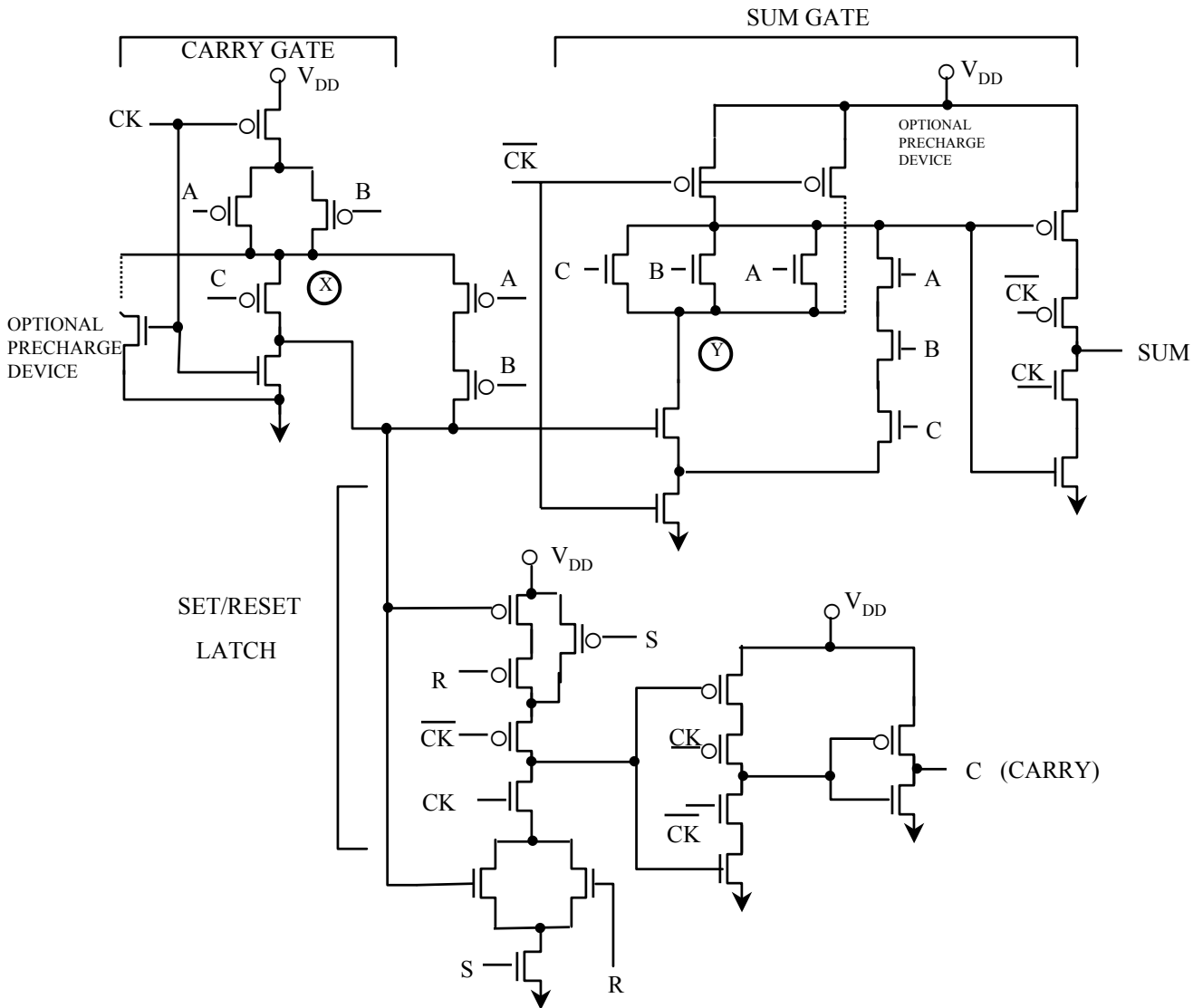- Gates are implemented using dynamic circuits




- Layout

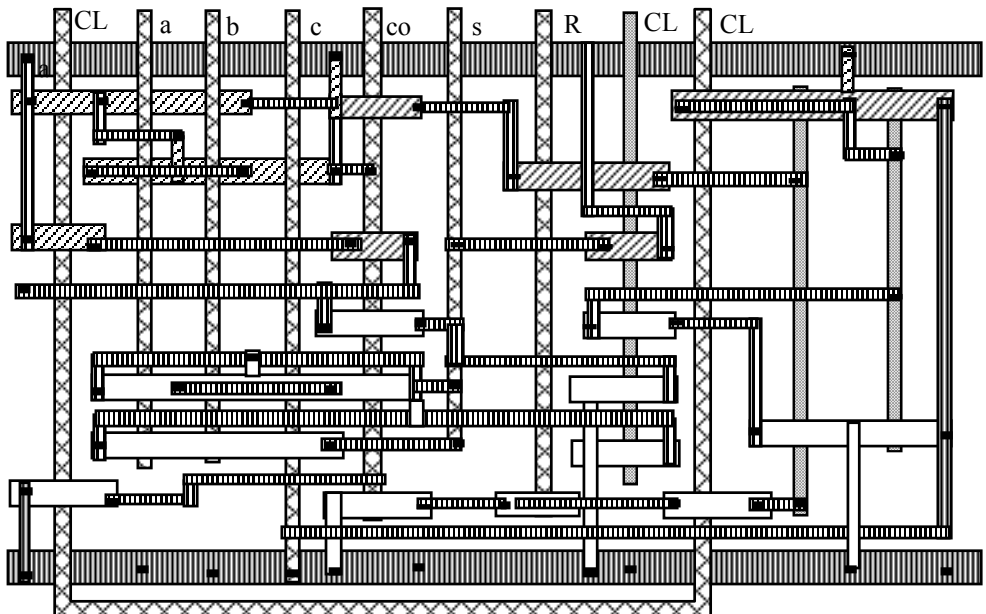


Combinational Adder Layout

- (Symbolic layout) : 3 styles

 

(a) minimum height

(b) minimum width

 


(c) Compromise between(a)&(b)




Transmission Gate (TG) Adder

- TG exclusive-or gate

 

- TG exclusive-nor gate

 


- TG Adder

$$\begin{aligned} SUM &= ABC + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} \\ &= (AB + \overline{A}\overline{B})C + (\overline{A}\overline{B} + \overline{A}B)\overline{C} \\ &= (\overline{A \oplus B})C + (A \oplus B)\overline{C} \end{aligned}$$

$$\begin{aligned} \overline{SUM} &= \overline{ABC} + \overline{\overline{A}\overline{B}C} + \overline{\overline{A}B\overline{C}} + \overline{A\overline{B}\overline{C}} \\ &= (\overline{AB} + \overline{A}\overline{B})C + (\overline{AB} + \overline{A}\overline{B})\overline{C} \\ &= (A \oplus B)C + (\overline{A \oplus B})\overline{C} \end{aligned}$$
 
$$\begin{aligned} \overline{CARRY} &= \overline{ABC} + \overline{\overline{A}\overline{B}C} + \overline{\overline{A}B\overline{C}} + \overline{A\overline{B}\overline{C}} \\ &= \overline{AB} + (A \oplus B)\overline{C} \\ &= (\overline{A \oplus B})\overline{B} + (A \oplus B)\overline{C} \end{aligned}$$



Carry Lookhead Adder

- Fast compared with ripple counter
- High cost

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

where $G_i = A_i \cdot B_i$ generate signal

$P_i = A_i + B_i$ propagate signal

$$C_i = A_i B_i + (A_i + B_i) C_{i-1}$$

$$= G_i + P_i C_{i-1}$$



$$= G_i + P_i (C_{i-1} + P_{i-1} C_{i-2})$$

⋮

$$= G_i + P_i C_{i-1} + P_i P_{i-1} C_{i-2} + P_i P_{i-1} P_{i-2} C_{i-3} + \dots$$


$$\Rightarrow \left\{ \begin{array}{l} C_1 = G_1 + P_1 C_0 \\ C_2 = G_2 + P_2 G_1 + P_2 P_1 C_0 \\ C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 C_0 \\ C_4 = G_4 + P_4 G_3 + P_4 P_3 G_2 + P_4 P_3 P_2 G_1 + P_4 P_3 P_2 P_1 C_0 \end{array} \right.$$

4-bit Full Carry Lookhead Adder

  


Carry Lookahead Adder

● Domino type

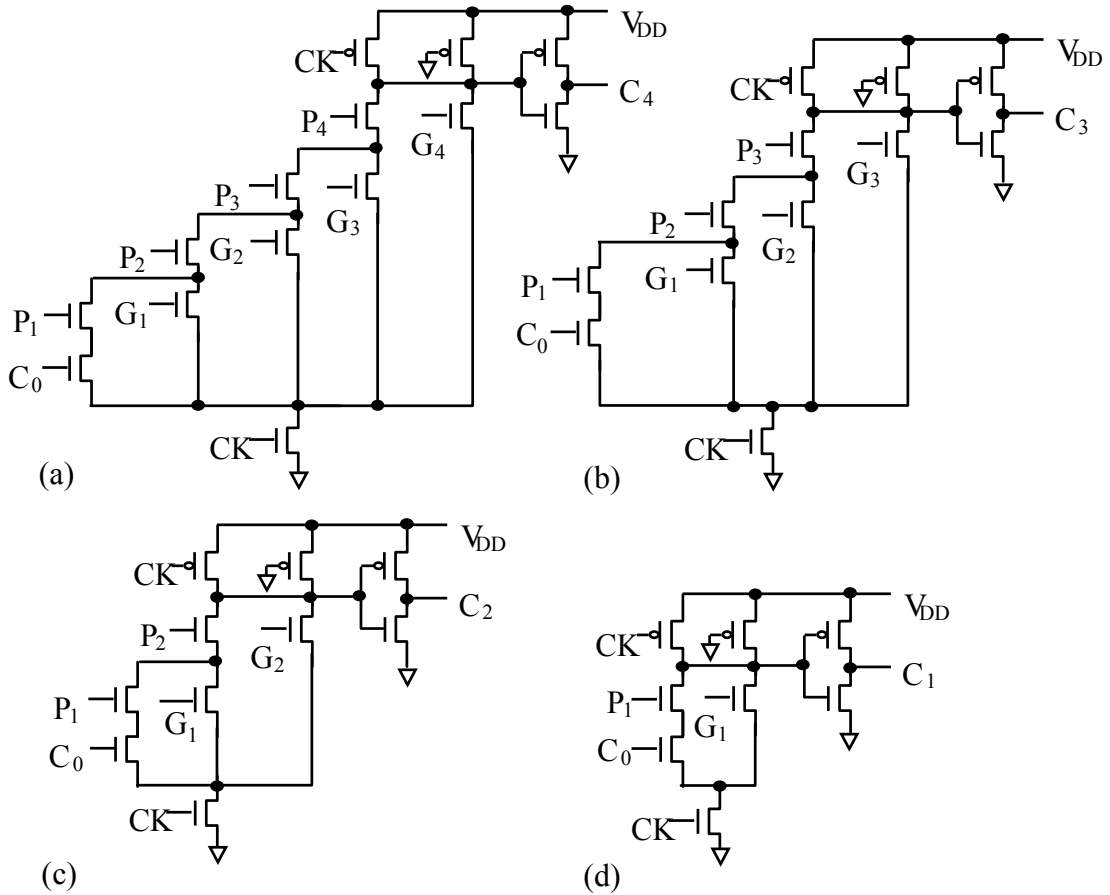


● Static type

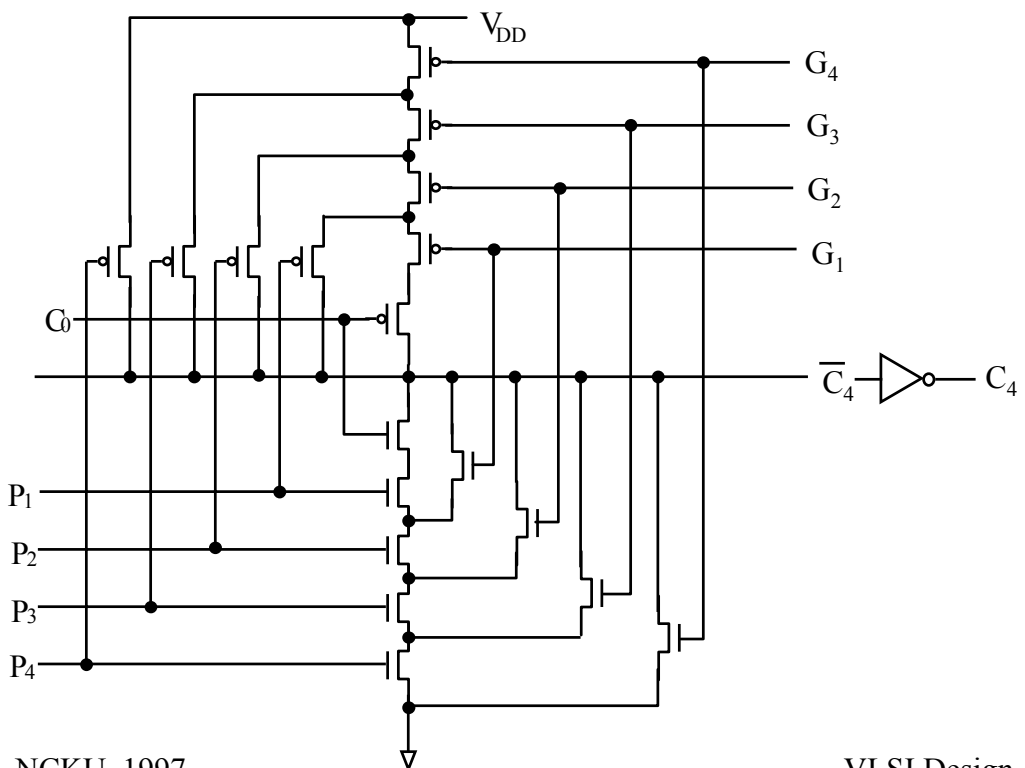

Counter


- Asynchronous counter

 - Slow: clock is provided by the previous stage
=> long counter chain delay



- synchronous counter



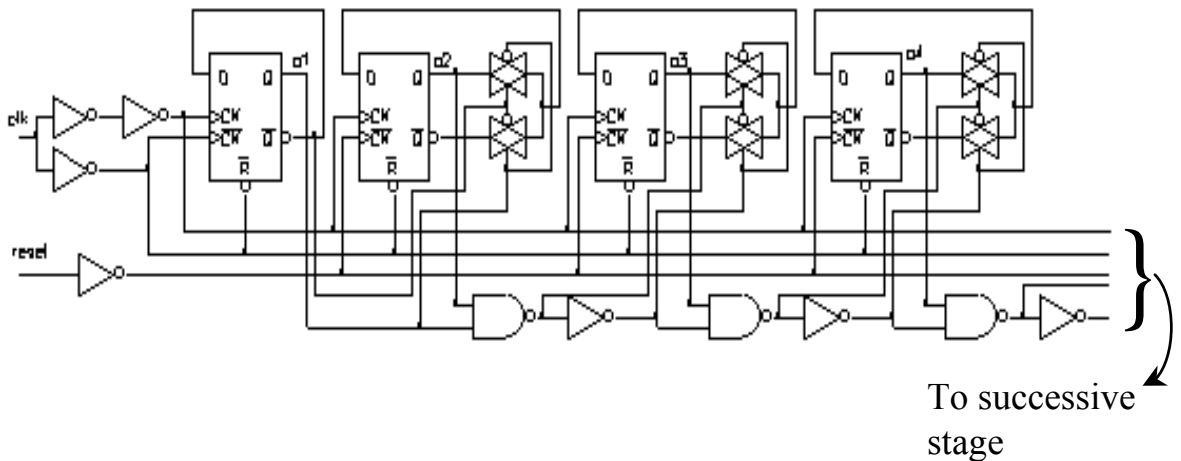
- Fast: Each stage is clocked simultaneously and the output change in a synchronous manner.



Floor plan using standard cells

● Synchronous counter

— floor plan

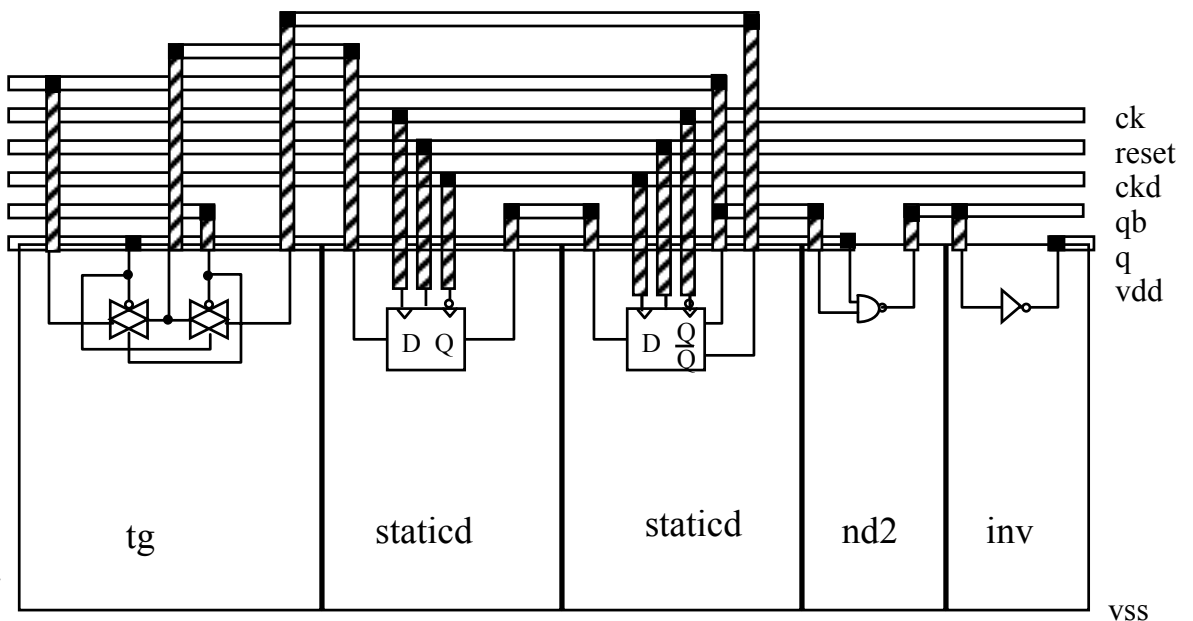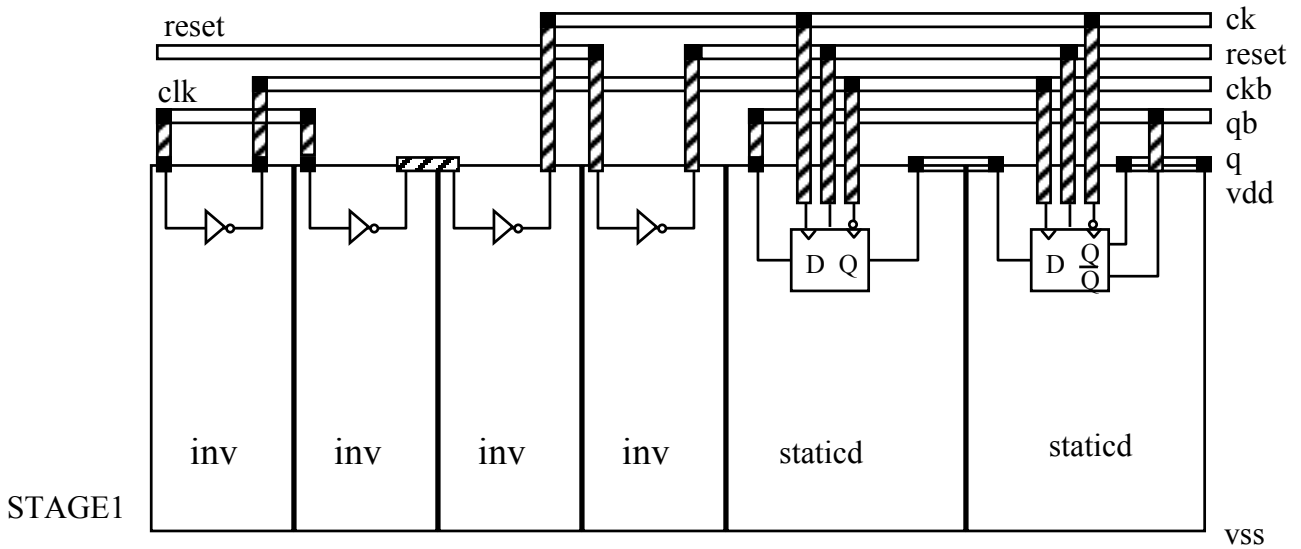 

Multiplier

- Applications

- signal processing
- correlation
- convolution
- filtering
- frequency analysis
- CPU

- Three types

- Serial
- Serial/Parallel
- Parallel


- Operations

- Evaluation of partial product
- Accumulation of shifted partial product


$$\begin{array}{r} \text{multiplicand; } 1100 : 12_{10} \\ \text{multiplier ; } 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 0111100 : 60_{10} \end{array}$$

Multipliers

- Serial

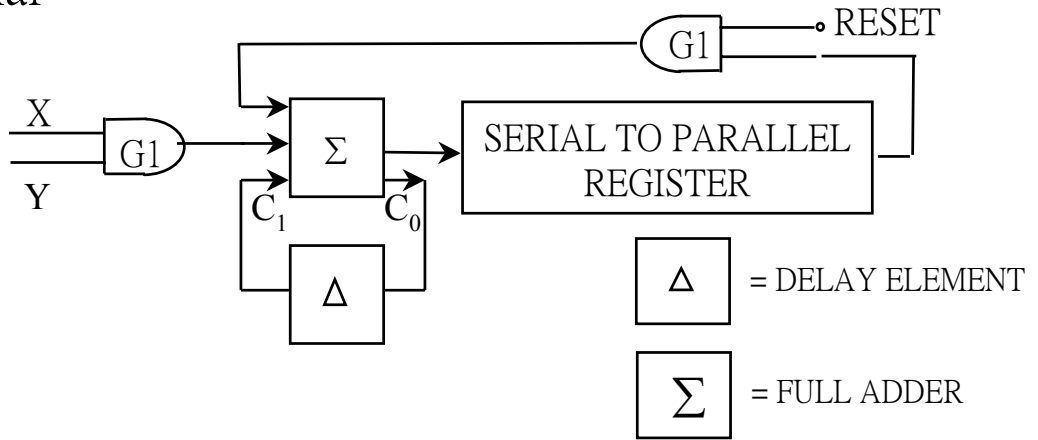


- Serial / Parallel

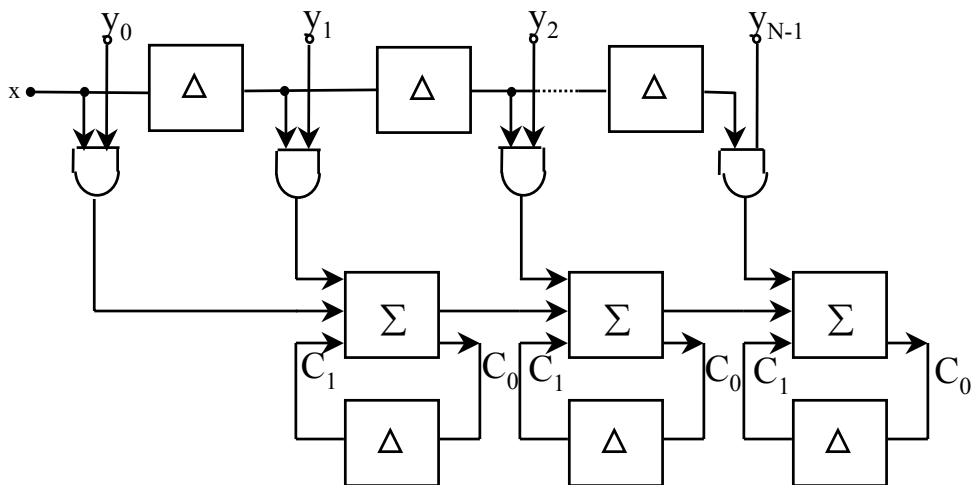


$$X = x_{M-1} \cdots x_2 x_1 x_0$$

$$Y = y_{M-1} \cdots y_2 y_1 y_0$$

 

= FULL ADDER

 


= DELAY ELEMENT

Parallel Multiplier


● TABLE 8.2 4-bit multiplier partial products

				X_3	X_2	X_1	X_0	Multiplicand	
				Y_3	Y_2	Y_1	Y_0	Multiplier	
				X_3Y_0	X_2Y_0	X_1Y_0	X_0Y_0		
				X_3Y_1	X_2Y_1	X_1Y_1	X_0Y_1		
				X_3Y_2	X_2Y_2	X_1Y_2	X_0Y_2		
				X_3Y_3	X_2Y_3	X_1Y_3	X_0Y_3		
P_7	P_6	P_5	P_4	P_3	P_2	P_1	P_0	Product	

● Multiplier array

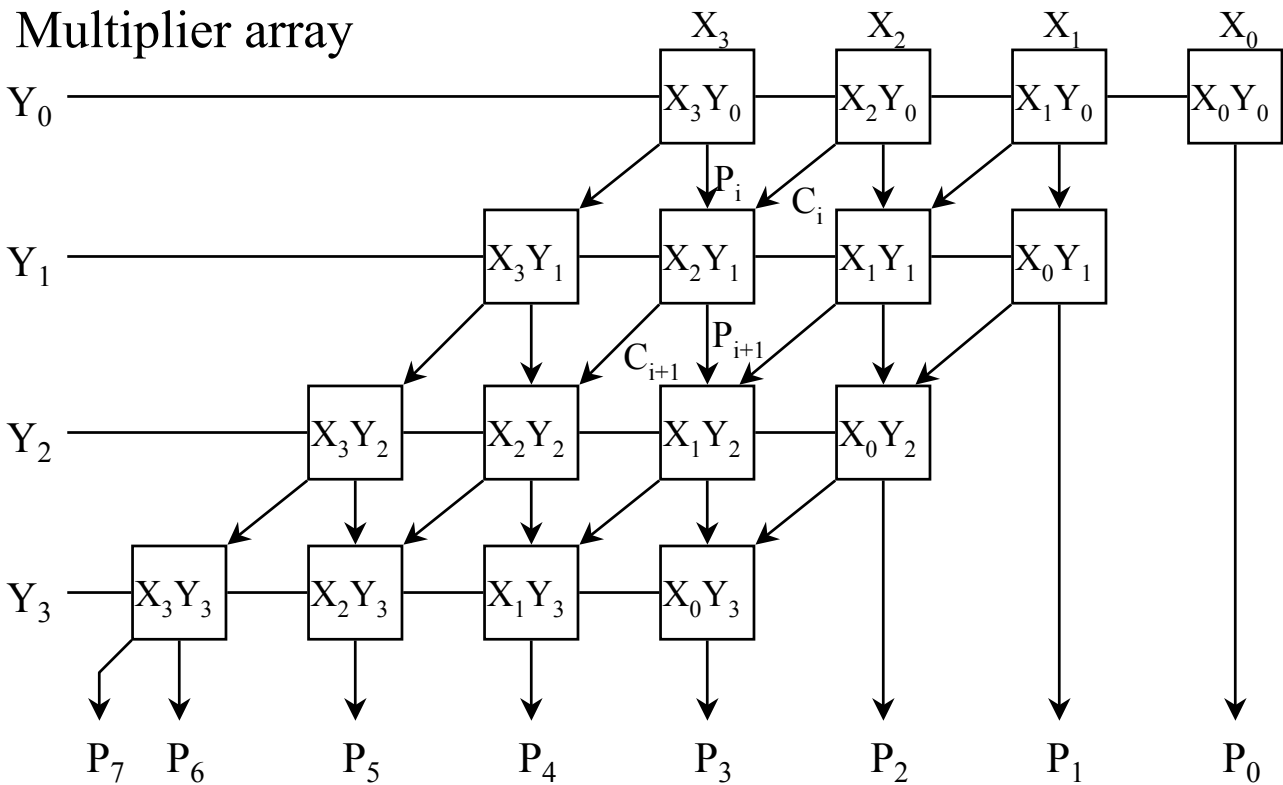


● Parallel multiplier cell

 

● Speed : parallel > serial/parallel > serial


● Cost : parallel > serial/parallel > serial

Systolic Array Multiplier

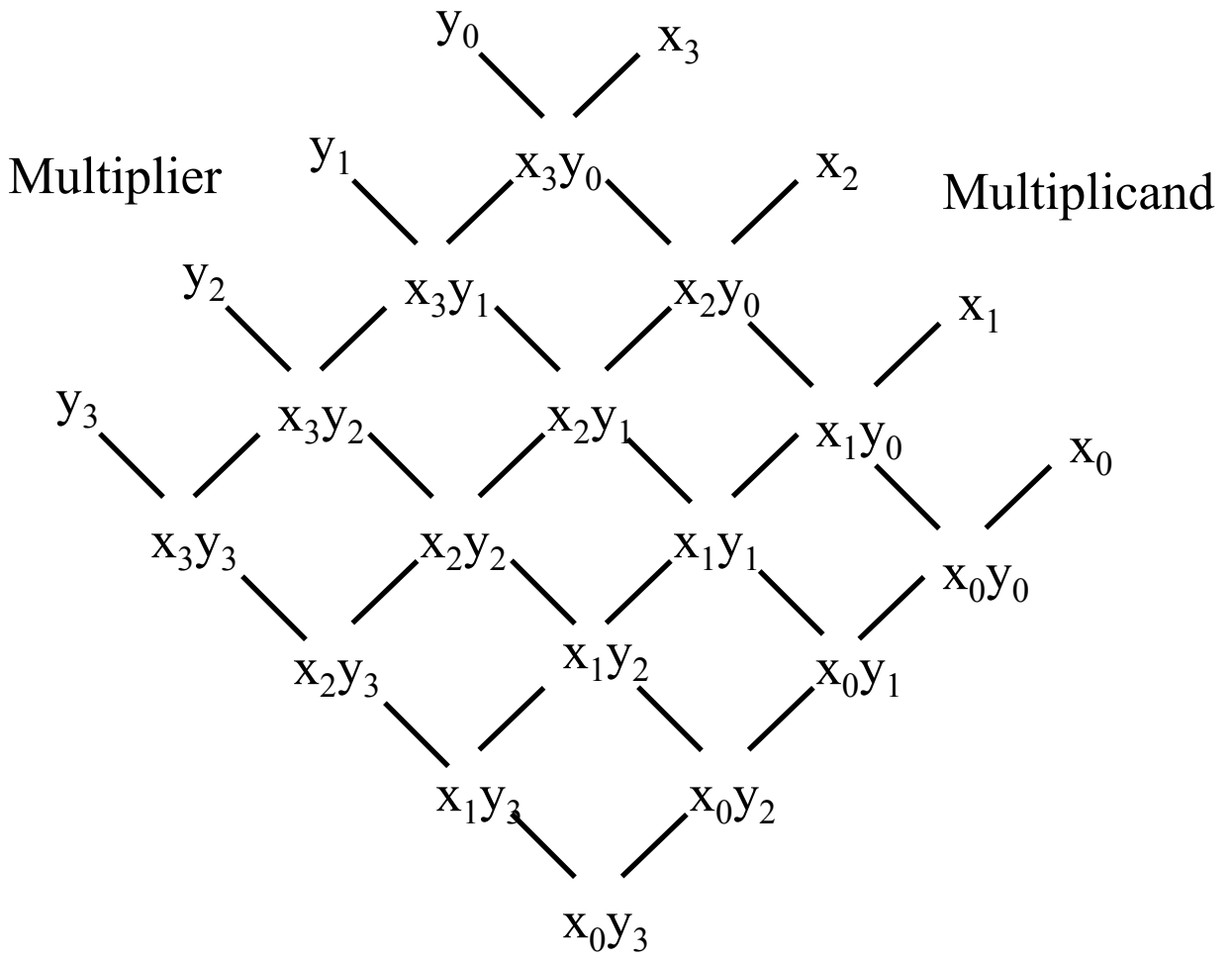

P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0 Product

— Multiplier structure

 


◇ = Basic cell

● = Latch

— Basic cell

● = Latch


GFA = Gated full adder

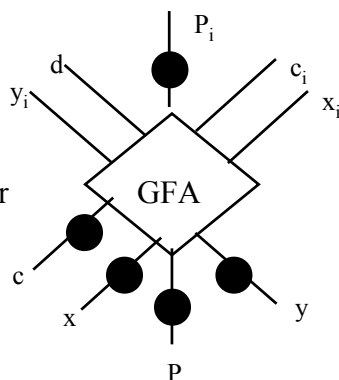

where p_i = partial product sum in
 p = partial product sum out
 c_i = carry in
 c = carry out
 d = line required for two's complement operation

Memory


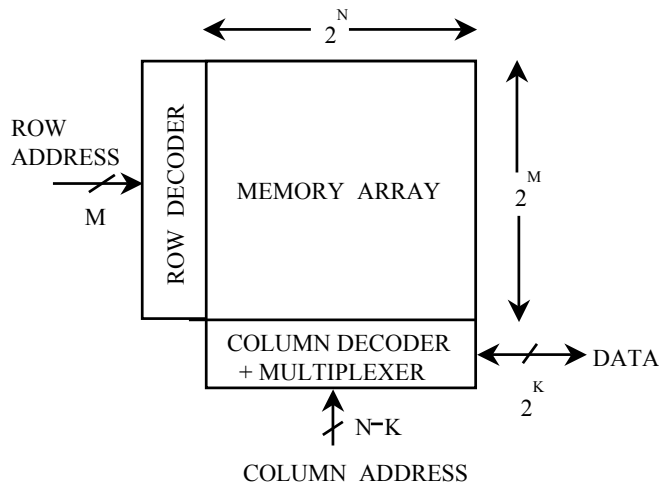
- RAM (Read & Write)
 - SRAM
 - DRAM
- ROM (Read only)
- RAM structure



- SRAM (Static random access memory)


— 4T cell

— 6T cell

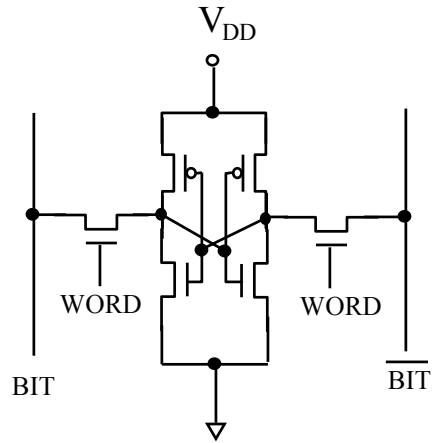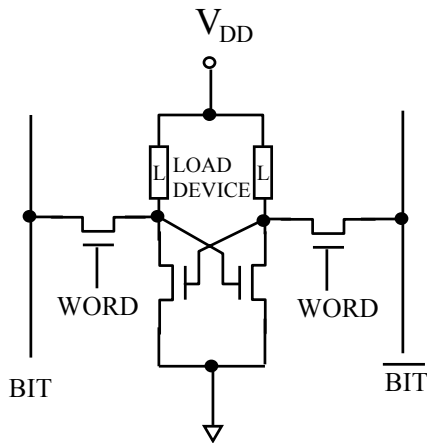

- DRAM (Dynamic random access memory)

 
- Slower than SRAM
- Less expensive than SRAM
- ☞ one transistor cell




ROM

- Read only memory

— ROM array

 

— Mask layer assignment

 


Realization of Sum of Product

● ROM

— more space
 $2^8 \times 8$

Input variables

Output functions

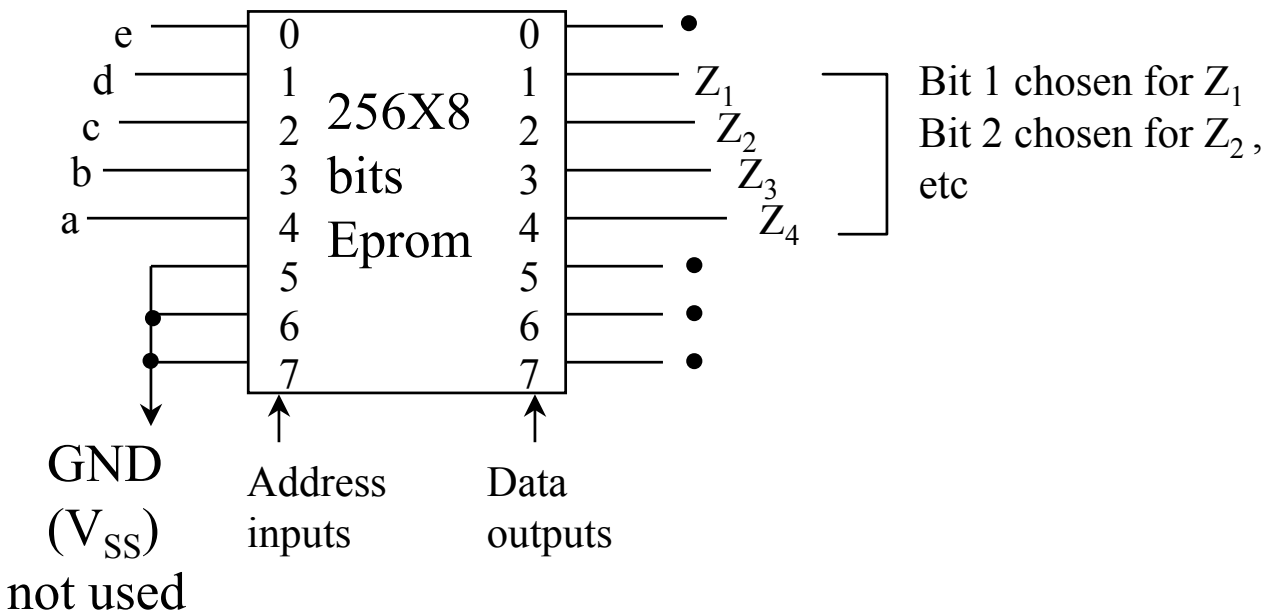

Output functions

$$Z_1 = \bar{a}\bar{b}d\bar{e} + \bar{a}b\bar{c}\bar{d}\bar{e} + bc + de = \sum m(0,3,7,11,12,13,14,15,17,19,21,23,27,28,29,30,31)$$

$$Z_2 = a\bar{c}\bar{e} = \sum m(1,3,9,11)$$

$$Z_3 = bc + de + \bar{c}\bar{d}\bar{e} + bd = \sum m(0,3,7,8,10,11,12,13,14,15,16,19,23,24,26,27,28,29,30,31)$$

$$Z_4 = \bar{a}\bar{c}\bar{e} + ce = \sum m(1,3,5,7,9,11,13,15,21,23,29,31)$$

Location/address


	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31
Bit 1	1	0	0	1	0	0	0	1	0	0	0	1	1	1	1	1	0	1	0	1	0	1	0	1	0	0	0	1	1	1	1	1
Bit 2	0	1	0	1	0	0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
Bit 3	1	0	0	1	0	0	0	1	1	0	1	1	1	1	1	1	0	0	1	0	0	0	1	1	0	1	1	1	1	1	1	
Bit 4	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	0	0	0	0	0	0	1	0	1	0	0	0	0	0	1	0	1

Realization of Sum of Product(Cont.)

● PLA(programmable logic array)

— general solution $V \times P \times Z \Rightarrow 2V \times P + P \times Z$

 — example: $5 \times 8 \times 4 \Rightarrow 10 \times 8 + 8 \times 4$



5X8X4 PLA shown symbolically and programmed for:

$$Z_1 = p_1 + p_3 + p_4 + p_5$$

$$\therefore Z_1 = abde + \bar{a}\bar{b}\bar{c}\bar{d}\bar{e} + bc + de$$

$$Z_2 = p_2$$

$$\therefore Z_2 = \bar{a}\bar{c}\bar{e}$$

$$Z_3 = p_4 + p_5 + p_7 + p_8$$

$$\therefore Z_3 = bc + de + \bar{c}\bar{d}\bar{e} + bd$$


$$Z_4 = p_2 + p_6$$

$$\therefore Z_4 = \bar{a}\bar{c}\bar{e} + ce$$

PLA Floor Plan


● Sum of product
 
$$Z = P_X + P_Y = AB + CD; \quad P_X = AB, \quad P_Y = CD$$




— Demorgan's Law

 
$$Z = AB + CD = \overline{\overline{A+B+C+D}}$$



● AND-OR

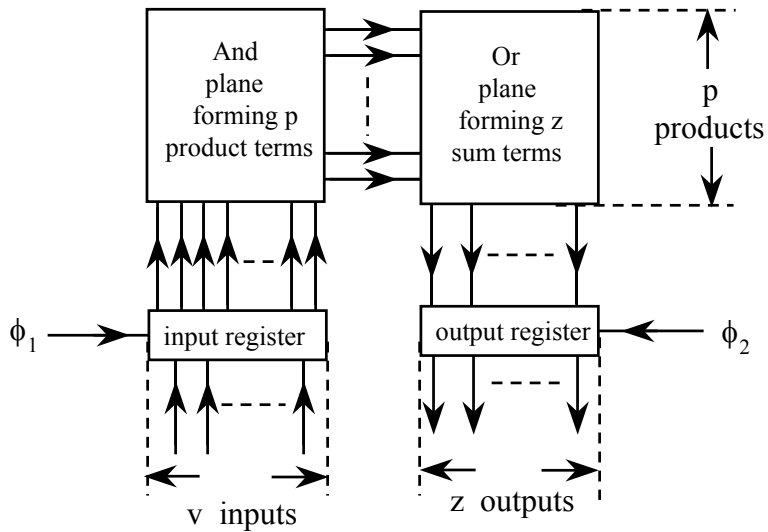

● NOR-NOR (General Solution)

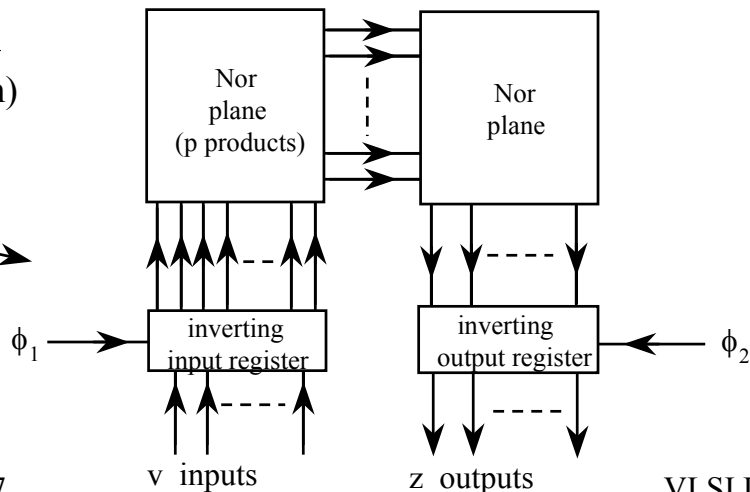

Circuit Diagram of PLA

- Cost depends on dimension $V \times P \times Z$


V : of input

P : of product term

Z : # of output

$$\text{Dimension } P \left\{ \underbrace{\quad}_{2V} \right\} + P \left\{ \underbrace{\quad}_Z \right\} = 2PV + PZ$$


- Example: $5 \times 8 \times 4$

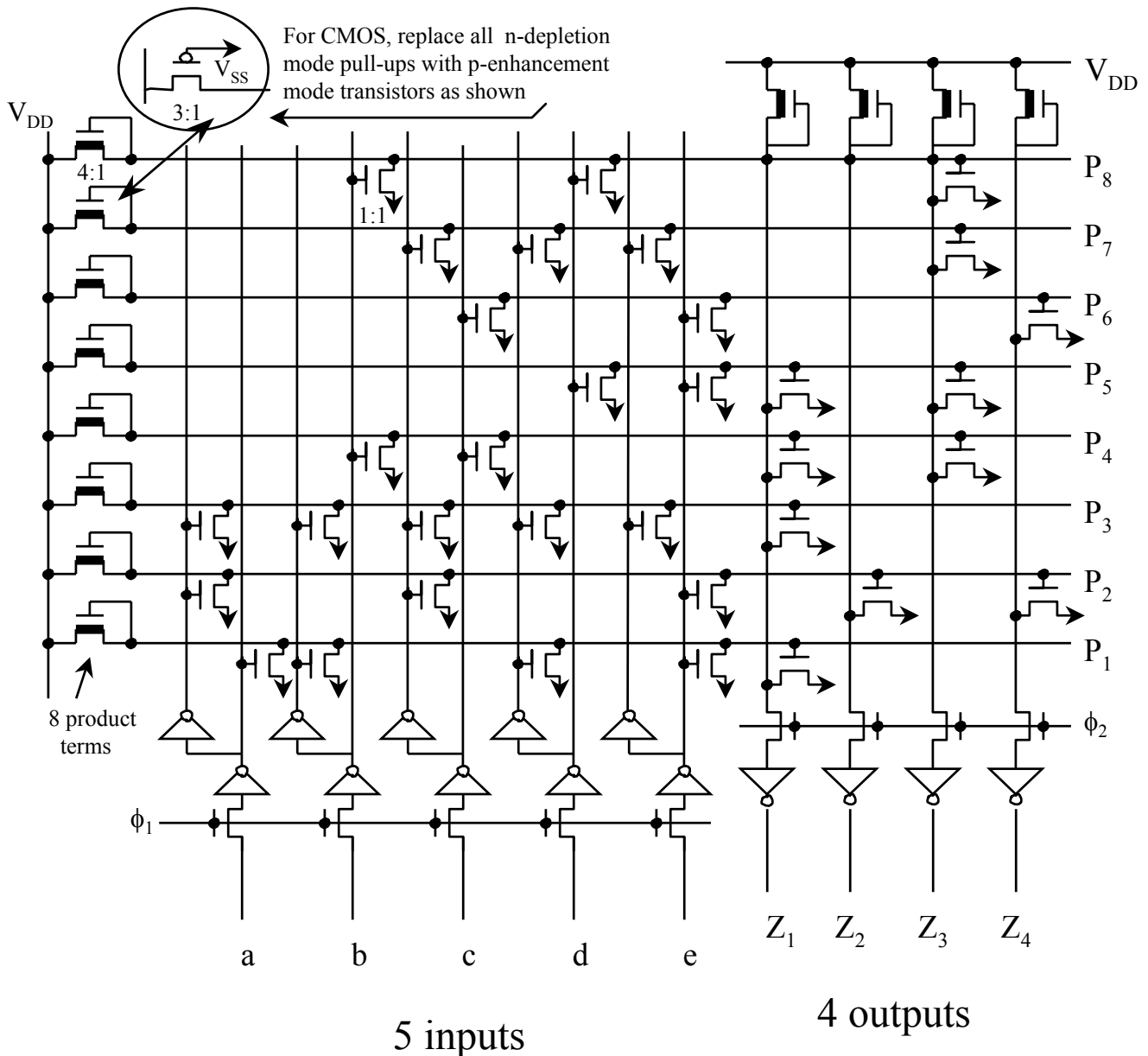


Finite State Machine (FSM)

- Sequential circuit

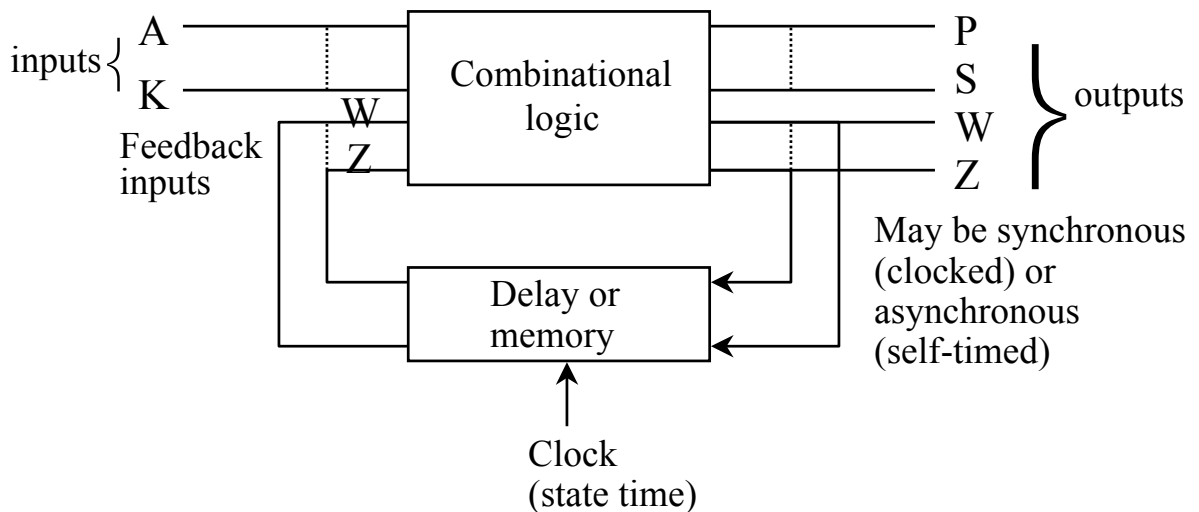- General form :
combinational logic could be implemented
by ROM, PLA, and other circuits



- PLA with feedback
(General approach)

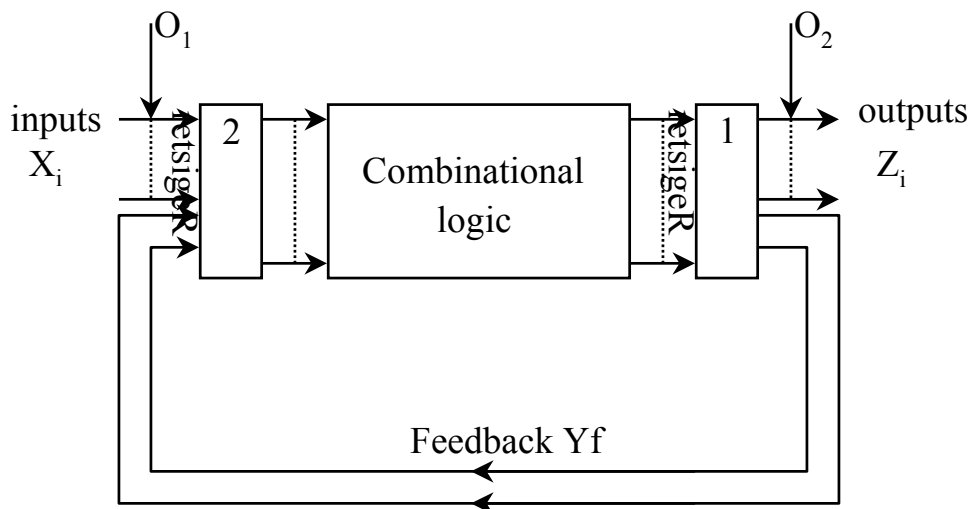

Feedback in a register transfer path implementing a finite state machine (synchronous)

FSM Design Example


● Specification

We are to design a circuit, the input to which are serial binary digits clocked by ϕ_2 and presented at an input W. The circuit is to produce an output Z=1 when the circuit has detected an odd number of 1s in groups of three bits arriving at input W. Otherwise, Z is to be 0. Groups of three bits arriving at W do not overlap, that is, bits 1, 2, and 3 from the first group, bits 4, 5, and 6 the second, bits 7, 8, and 9 the third group of three, etc. Z is to be clocked by ϕ_2 and W can be clocked into the PLA by ϕ_1 since it is available following the preceding ϕ_2 .

● Design procedure

state diagram \longrightarrow state transition table
 \longrightarrow minimization of number of product term \longrightarrow circuit \longrightarrow layout

● state diagram

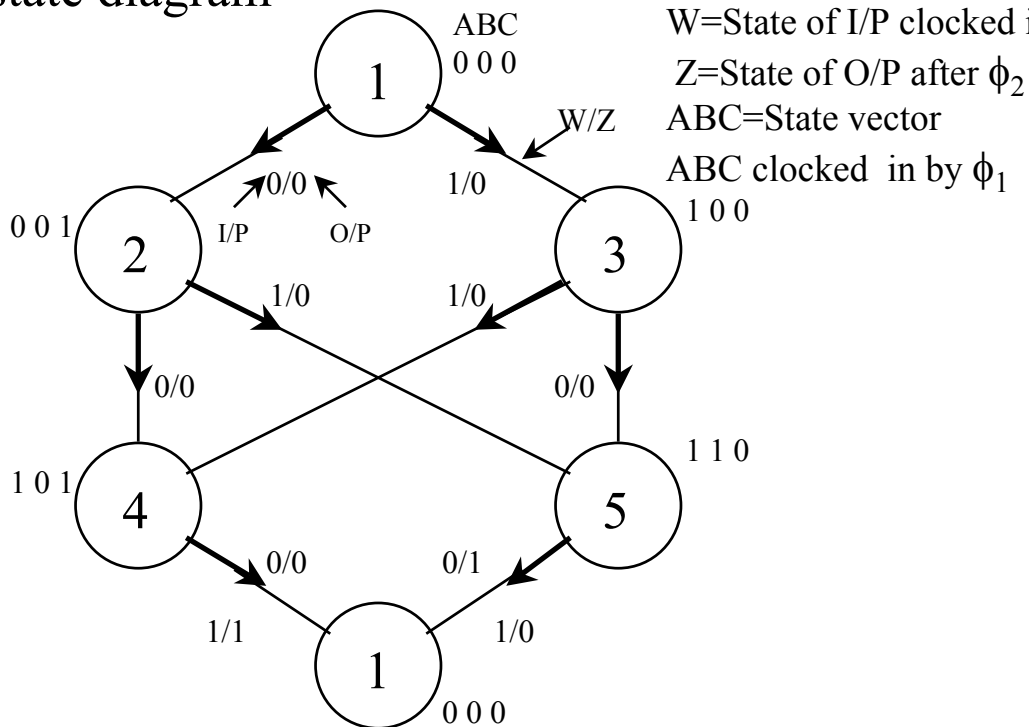

● State transition table

State number	Inputs				And term	Outputs			
	W	State vector				Next vector			Z
		A_p	B_p	C_p		A_p	B_p	C_p	
★	0	0	0	0	R_1	0	0	1	0
★	1	0	0	0	R_2	1	0	0	0
★	0	0	0	1	R_3	1	0	1	0
★	1	0	0	1	R_4	1	1	0	0
★	0	1	0	0	R_5	1	1	0	0
★	1	1	0	0	R_6	1	0	1	0
★	0	1	0	1	R_7	0	0	0	0
★	1	1	0	1	R_8	0	0	0	1
⊕	0	1	1	0	R_9	0	0	0	1
⊕	1	1	1	0	R_{10}	0	0	0	0

FSM Design Example (Cont.)

- Sum of product

$$A_n = R_2 + R_3 + R_4 + R_5 + R_6$$

$$B_n = R_4 + R_5$$

$$C_n = R_1 + R_3 + R_6$$

$$Z = R_8 + R_9$$

<i>Product term</i>	<i>Minterm Form</i>	<i>Simplified form</i>
R_1	$\overline{W} \overline{A} \overline{B} \overline{C}$	$\overline{W} \overline{A} \overline{C}$
R_2	$\overline{W} \overline{A} B \overline{C}$	$\overline{W} \overline{A} \overline{C}$
R_3	$\overline{W} \overline{A} B C$	$\overline{W} \overline{A} \overline{C}$
R_4	$\overline{W} A \overline{B} \overline{C}$	$\overline{W} \overline{A} \overline{C}$
R_5	$\overline{W} A \overline{B} C$	$\overline{W} A \overline{B} \overline{C}$
R_6	$\overline{W} A B \overline{C}$	$\overline{W} A B \overline{C}$
R_7	$\overline{W} A B C$	$\overline{W} A \overline{C}$
R_8	$\overline{W} A \overline{B} C$	$\overline{W} A \overline{C}$
R_9	$\overline{W} A B \overline{C}$	$\overline{W} B$
R_{10}	$\overline{W} A B C$	$\overline{W} B$

And plane (Nor plane)

$$\overline{R}_1 = \overline{W+A+C} \quad \text{that is } R_1 = \overline{W} \overline{A} \overline{C}$$

$$\overline{R}_2 = \overline{\overline{W}+A+C} \quad \text{-etc.-}$$

$$\overline{R}_3 = \overline{W+A+\overline{C}} \quad \text{-}$$

$$\overline{R}_4 = \overline{\overline{W}+A+C} \quad \text{-}$$

$$\overline{R}_5 = \overline{W+\overline{A}+B+C} \quad \text{-}$$


$$\overline{R}_6 = \overline{\overline{W}+\overline{A}+B+C} \quad \text{-}$$

$$\overline{R}_8 = \overline{\overline{W}+A+\overline{C}} \quad \text{-}$$

$$\overline{R}_9 = \overline{W+B} \quad R_9 = \overline{W} B$$


- minimization of number of product term (Homework)

- Floor plan

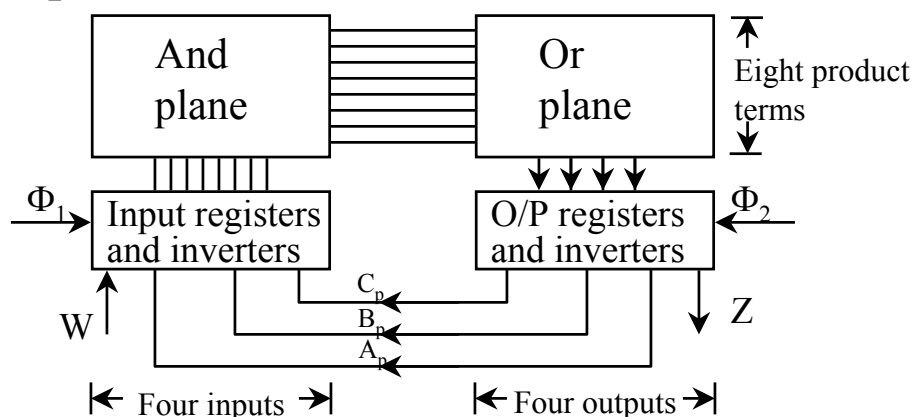


FSM Design Example (Cont.)

● Circuit diagram

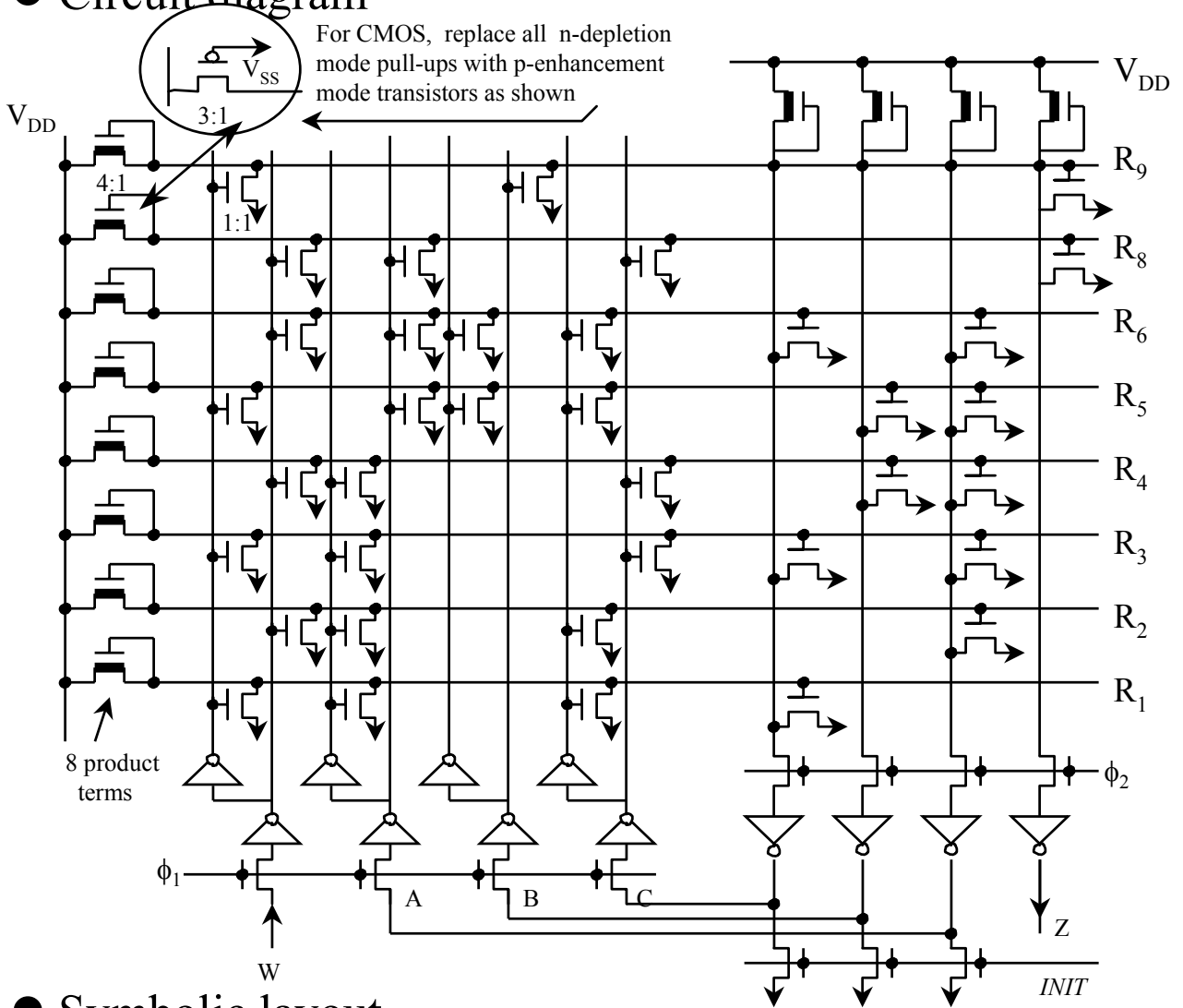


● Symbolic layout

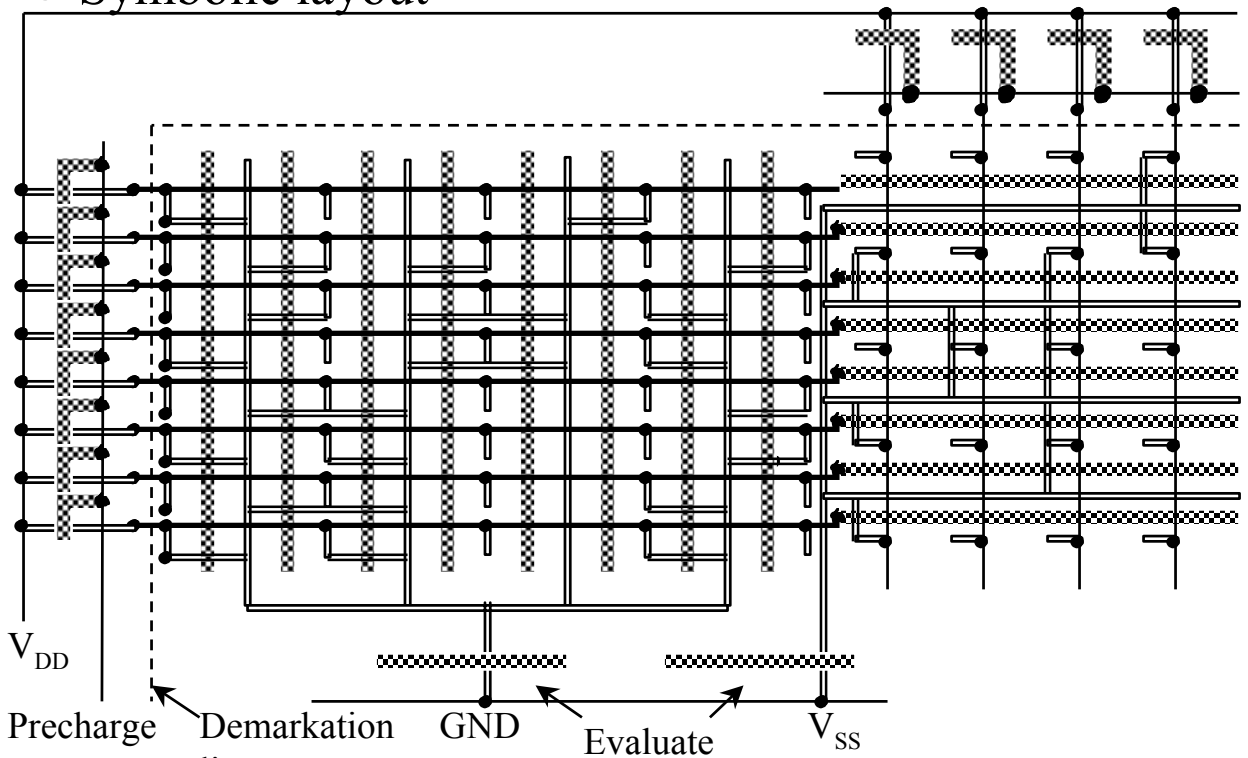

FSM Design Example(Cont.)

- FSM layout cell

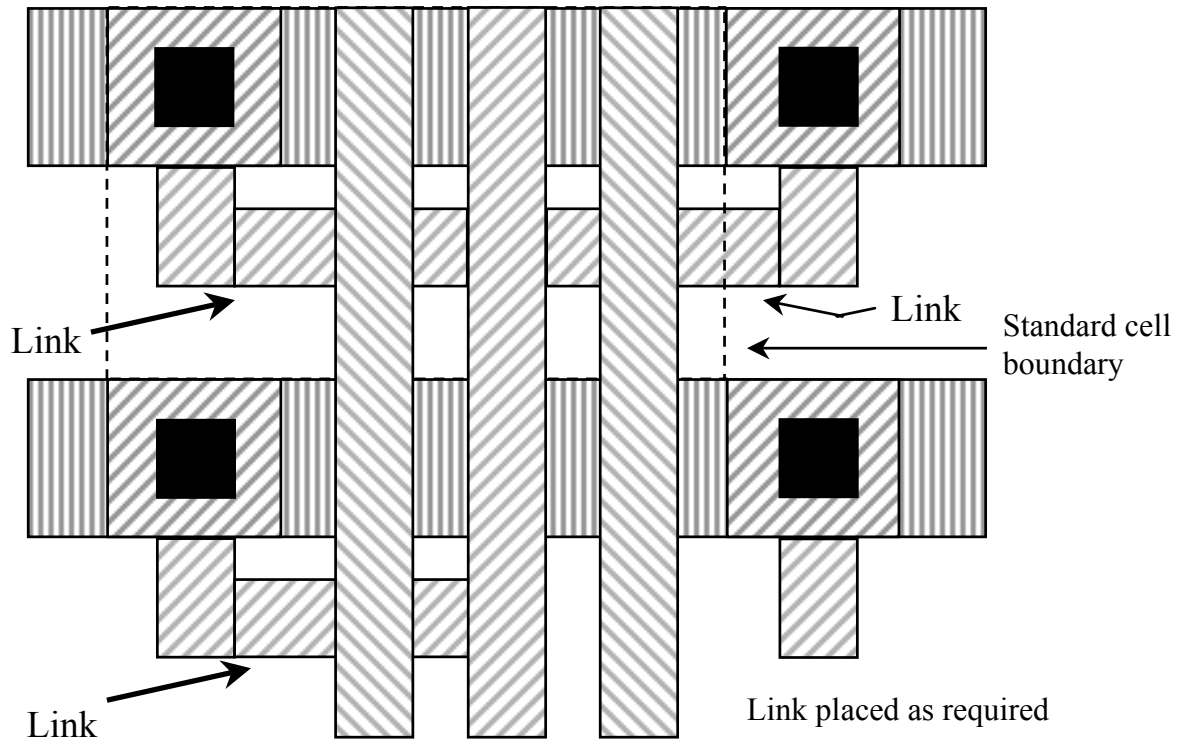

- Standard cell approach