
 


BiCMOS Digital Circuit Design


- Review of CMOS & NMOS Inverter Design
 - delay time
 - pair delay
 - driving large capacitive loads
- Features of BiCMOS Digital Circuit
- BiCMOS Inverters
 - basic type
 - delay time
 - improved type
 - full swing
 - design example
 - a. size optimization
 - b. driving large capacitive loads
- BiCMOS Gate
- Power-Supply Sensitivity
 - voltage scaling
 - low voltage gate
- I/O Interface
 - input
 - output
 - logic conversion

NMOS DIGITAL CIRCUITS

● Static inverters

 



D:

 

— Static power dissipation during $V_{out}=V(0)$

Switching Characteristics of CMOS Inverter


● CMOS inverter

 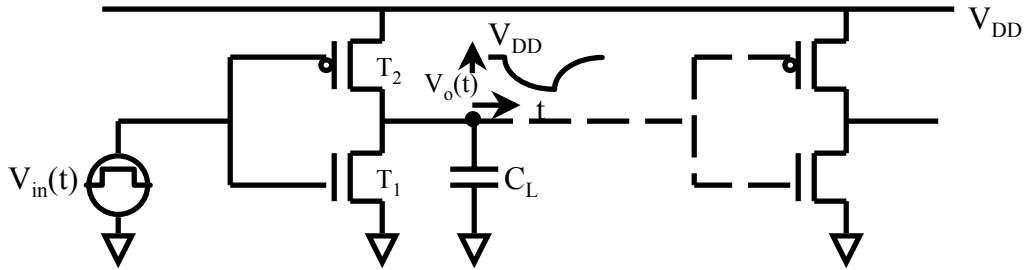

● Trajectory of n-transistor operating point during switching in CMOS inverter

— Input transition : $X_1 \rightarrow X_2$

Output transition: $X_2 \rightarrow X_3$


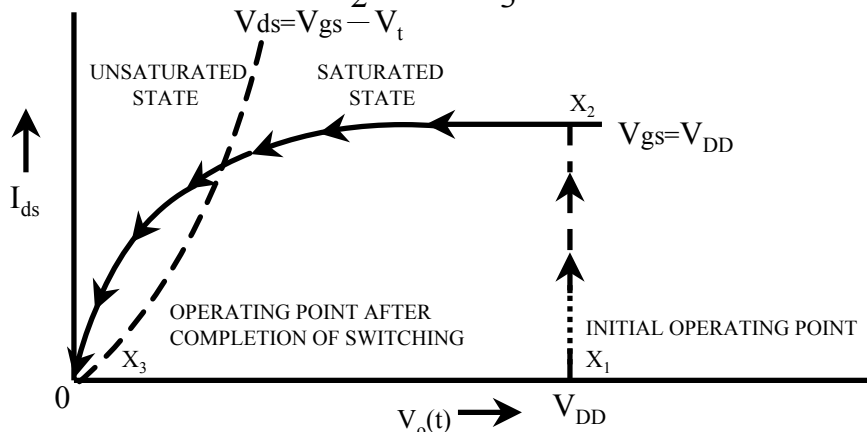


Rise Time and Fall Time of CMOS Inverter

> Equivalent Circuit



> Fall
 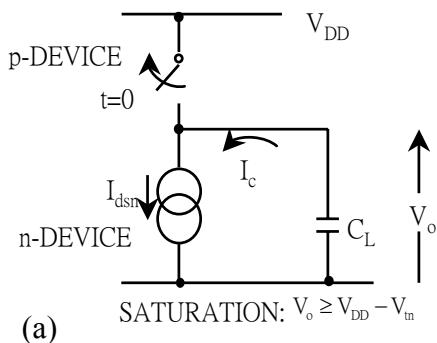
$$\begin{pmatrix} V_{in} \uparrow \\ V_o \downarrow \end{pmatrix}$$



> Rise
  
$$\begin{pmatrix} V_{in} \downarrow \\ V_o \uparrow \end{pmatrix}$$



> $t_f = t_{f1} + t_{f2}$; fall time

$$\begin{array}{c} \uparrow t_{f1} \quad \uparrow t_{f2} \\ V_o = 0.9V_{DD} \quad V_o = 0.1V_{DD} \\ V_o = V_{DD} - V_{tn} \end{array}$$

$$\begin{array}{c} \downarrow t_{f1} \quad \downarrow t_{f2} \\ \left\{ \begin{array}{l} I_{DS(PMOS)} = 0 \\ I_{DS(NMOS)} \text{ in saturation} \end{array} \right. \rightarrow \left\{ \begin{array}{l} I_{DS(PMOS)} = 0 \\ I_{DS(NMOS)} \text{ in triode} \end{array} \right. \end{array}$$

Fall Time (Cont.)

● t_f

— $V_o : 0.9 V_{DD} \longrightarrow V_{DD} - V_{tn}$

— NMOS in saturation region

$$C_L \frac{dV_o}{dt} - \frac{\beta_n}{2} (V_{DD} - V_{tn})^2 = 0$$

$$\begin{aligned} t_{f1} &= \frac{2C_L}{\beta_n (V_{DD} - V_{tn})^2} \int_{V_{DD} - V_{tn}}^{0.9V_{DD}} dV_o \\ &= \frac{2C_L (V_{tn} - 0.1 V_{DD})}{\beta_n (V_{DD} - V_{tn})^2} \end{aligned}$$

● t_{f2}

— $V_o : V_{DD} - V_{tn} \longrightarrow 0.1 V_{DD}$

— NMOS in triode region

$$C_L \frac{dV_o}{dt} = \frac{\beta_n}{2} [2(\overset{\uparrow}{V_{DD}} - V_{tn})V_{ds} - V_{ds}^2]$$

$$t_{f2} = \frac{C_L}{\beta_n (V_{DD} - V_{tn})} \int_{0.1V_{DD}}^{V_{DD} - V_{tn}} \frac{dV_o}{\frac{V_o^2}{2(V_{DD} - V_{tn})} - V_o}$$

Fall Time (Cont.)

$$\bullet t_{f2} = \frac{C_L}{\beta_n (V_{DD} - V_{tn})} \ln\left(\frac{19V_{DD} - 20V_{tn}}{V_{DD}}\right)$$

$$t_f = t_{f1} + t_{f2}$$

$$= \frac{2C_L}{\beta_n (V_{DD} - V_{tn})}$$

$$\times \left[\frac{V_{tn} - 0.1V_{DD}}{V_{DD} - V_{tn}} + \frac{1}{2} \ln\left(\frac{19V_{DD} - 20V_{tn}}{V_{DD}}\right) \right]$$

$$\bullet \text{ e.g. } V_{DD} = 5V, V_{tp} = -1V, V_{tn} = 1V$$

$$t_f \approx \frac{4C_L}{\beta_n V_{DD}}$$

● Rise time

$$\text{Similarly, } t_r \approx \frac{4C_L}{\beta_p V_{DD}}$$

Fall Time and Rise Time (Cont.)

- $$t_f \approx \frac{4C_L}{\beta_n V_{DD}}$$
$$t_r \approx \frac{4C_L}{\beta_{pl} V_{DD}}$$

- For equally sized n and p devices

$$\beta_n = 2\beta_p$$

$$t_f = \frac{t_r}{2}$$

- For $t_r = t_f$
 $\Rightarrow \beta_p = \beta_n \quad \Rightarrow W_p = 2.5W_n$

For simplicity, 2 is used sometimes.

$$t_{df} = \frac{t_f}{2}$$

$$t_{dr} = \frac{t_r}{2}$$

Equivalent Circuit

- Equivalent Resistance

$$t_f = \frac{4C_L}{\beta_n V_{DD}} = R_{eq} C_L$$

$$R_{eq} = \frac{4}{\beta_n V_{DD}} \quad \text{for minimum sized NMOS}$$

$$R_{eq}(\text{PMOS}) = \frac{4}{\beta_p V_{DD}} \approx 2.5 R_{eq} \quad \text{for minimum sized PMOS}$$


- Equivalent capacitance

$$C_{eq} = C_{gs} \text{ of minimum sized transistors}$$

Inverter-pair Delay


> CMOS

 (a) $W_p = 2.5W_n$; W_n and L are minimum size



$$t_{\text{inv-pair}} = t_f + t_r = 3.5R_{\text{eq}} C_{\text{eq}} + 3.5R_{\text{eq}} C_{\text{eq}} \\ = 7R_{\text{eq}} C_{\text{eq}}$$

 (b) $W_p = W_n$; All minimum sized devices




$$t_{\text{inv-pair}} = 5R_{\text{eq}} C_{\text{eq}} + 2R_{\text{eq}} C_{\text{eq}} \\ = 7R_{\text{eq}} C_{\text{eq}}$$

— $W_p = 2.5W_n \implies V_{\text{inv}} = 2.5V$ } same delay time
 $W_p = W_n \implies V_{\text{inv}} = 2.2V$ } $V_{\text{inv}} \sim 10\%$ variation

Inverter-pair Delay (Cont.)


- Driving same size inverter

 

L&W are minimum size

$$\text{Inverter-pair Delay} = 7R_{eq}C_{eq} = 7\tau$$

where $\tau = R_{eq}C_{eq}$

 

$$\text{Inverter-pair Delay} = 7n^2 R_{eq}C_{eq} = 7n^2 \tau$$


where $\tau = R_{eq}C_{eq}$

(Depends on channel length
independent of channel width)

*Recall that
$$W_u = \frac{g_m}{C_g} = \frac{\mu}{L^2} (V_{gs} - V_t)$$

Driving Large Capacitive Loads

> CMOS

 

(i) If L_p & L_n are minimum channel length ,

$$t_{\text{inv-pair}} = 7f \tau$$

(ii) If L_p & L_n are not minimum channel length,
additional calculation is required to obtain

$$t_{\text{inv-pair}}$$

- Delay per stage (minimum L)

(i) For ΔV_{in} : (a) 3.5τ ($W_p = 2.5W_n$), (b) 2τ ($W_p = W_n$)

(i) For ∇V_{in} : (a) 3.5τ ($W_p = 2.5W_n$), (b) 5τ ($W_p = W_n$)

> NMOS

$$t_{\text{inv-pair}} = 5f \tau$$

Delay per stage = $f \tau$ for ΔV_{in}

Delay per stage = $4f \tau$ for ∇V_{in}

Driving Large Capacitive Loads (Cont.)

$$\text{Let } y = \frac{C_L}{\square C_g} = f^N$$

($\square C_g$: gate capacitance of the first stage inverter)

$$\ln y = N \ln a$$

$$N = \frac{\ln y}{\ln a}$$

For N even , total delay

$$t_d = \frac{N}{2} 7a \leftarrow 3.5Na \leftarrow (\text{CMOS})$$

$$(\text{or}) = \frac{N}{2} 5a \leftarrow 2.5Na \leftarrow (\text{NMOS})$$

$$\text{Delay} \propto Nf \leftarrow \frac{\ln y}{\ln a} f \leftarrow$$

(for both CMOS and NMOS)

\implies For minimum t_d

$$\frac{d}{df} \left(\frac{\ln y}{\ln f} f \leftarrow \right) = 0 \implies \text{obtain } f = e \text{ to have the minimum value of } Nf \leftarrow$$

Driving Large capacitive Loads (Cont.)

Assuming $f = e$, then

$$N = \ln(y)$$

Overall delay t_d

(i) N even: $t_d = 2.5 Ne \tau$ (NMOS)
or $t_d = 3.5 Ne \tau$ (CMOS)

(ii) N is odd

$$\left. \begin{array}{l} t_d = [2.5(N-1)+1]e\tau \text{ (NMOS)} \\ t_d = [3.5(N-1)+2]e\tau \text{ (CMOS)} \end{array} \right\} \text{ for } \Delta V_{in}$$

$$\left. \begin{array}{l} t_d = [2.5(N-1)+4]e\tau \text{ (NMOS)} \\ t_d = [3.5(N-1)+5]e\tau \text{ (CMOS)} \end{array} \right\} \text{ for } \nabla V_{in}$$

** For optimum speed $f=e=2.71828$


But values from 2 to 10 may be used to obtain more flexibility and reduce cost(# of stages)

Features of BiCMOS Digital Circuit


- Combines CMOS and bipolar
 - CMOS
 - Low power dissipation
 - High density
 - Bipolar
 - High drive capability
 - Small swing logic
- “System on a chip” is possible
 - Mixed analog/digital
 - Analog circuit can be incorporated
 - High voltage, high power interface
 - (e.g. sensor, drive, ...) can be incorporated if special process is developed

BiCMOS Inverter

● Basic type

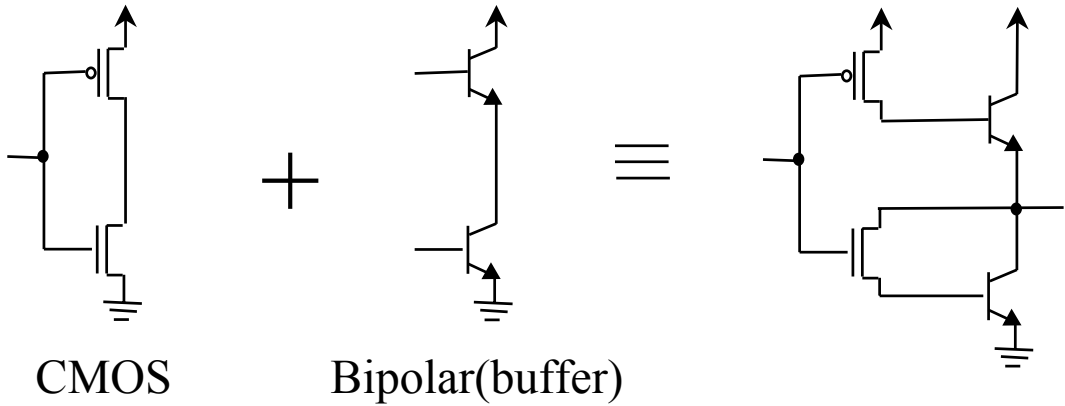

● Physical structure

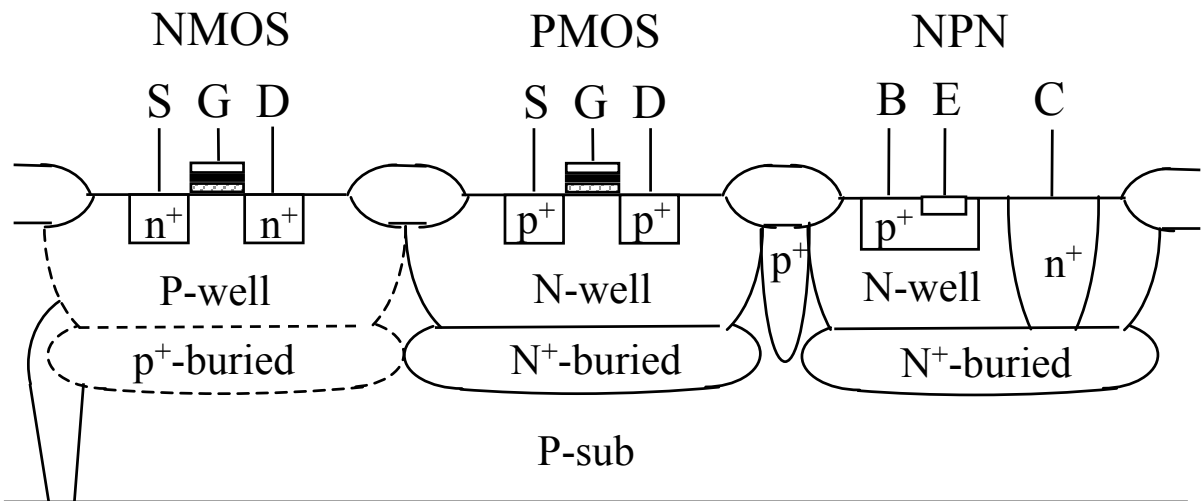


can be added to increase latchup immunity

PMOS drain and NPN base may be merged to reduce
 (a) area
 (b) capacitance
 (c) # of contact



Pull-up of BiCMOS Inverter

● Basic type BiCMOS inverter

 

● Pull-up

  — assume (initial condition) $V_{BE1} = 0$ & Q_2 are off



C_B is the capacitance at the Q_1 base node


C_{S1} is the capacitance at the output node when $C_L = 0$

— $t_{dl} = \frac{V_{BE} C_B}{I_{DN}}$...time required to turn on Q_1

— $\frac{t_r}{2} = \frac{V_{inv} (C_L + C_{S1})}{\beta I_{DP}}$...time required to change C_L TO V_{inv}

where $I_{DP} \approx \frac{\mu_p C_{OX}}{2} \left(\frac{W}{L}\right)_{M1} (V_{dd} - V_{BE} - V_{tp})^2$

— β vs. I_c


 


— delay time $t_{dr} = t_{dl} + \frac{t_r}{2}$

Pull-down of BiCMOS Inverter

● Pull-down

  — assume **1** M_1 & Q_1 are off **2** initial condition $V_{BE2} = 0$



where C_L is added capacitive load

C_S is the capacitance at the output node when $C_L = 0$

$$— t_{df} \approx \frac{V_{BE} C_B}{I_{DN}} + \frac{V_{inv} (C_L + C_{S1})}{\beta I_{DN}} = t_{d2} + \frac{t_f}{2}$$

$$\text{where } I_{DN} \approx \frac{\mu_n C_{OX}}{2} \left(\frac{W}{L}\right)_{M2} (V_{DD} - 2V_{BE} - V_{tn})^2$$

$$V_{SB} \approx V_{BE}$$

(body effect)



— β vs. I_c



● Adjusting the size of M_1 and M_2 , one can obtain $t_{dr} = t_{df}$

Delay Time of CMOS Inverter


● CMOS inverter

  

$$\bullet t_d \cong \frac{V_{inv.} (C_L + C_{S2})}{I_D} \text{ (rough estimation)}$$

$$\text{where } I_D \cong \frac{\mu C_{ox}}{2} \left(\frac{W}{L}\right) (V_{DD} - V_t)^2$$

 Delay Time Comparison between BiCMOS and CMOS




- Rough estimation

$$t_d = \begin{cases} t_1 + \frac{V_{inv.}(C_L + C_{s1})}{\beta I_D}; & \text{BiCMOS} \\ \frac{V_{inv.}(C_L + C_{s2})}{I_D}; & \text{CMOS} \end{cases}$$

Drawbacks of Basic-Type Inverter

- No path to discharge the bases

 

- Not full swing, i.e. not ($0 \sim V_{DD}$)

- swing: $V_{BE} \sim (V_{DD} - V_{BE})$


- Incompatible with CMOS logic

As described in the introduction, most digital circuits of a large chip use CMOS logic instead of BiCMOS for two reasons:

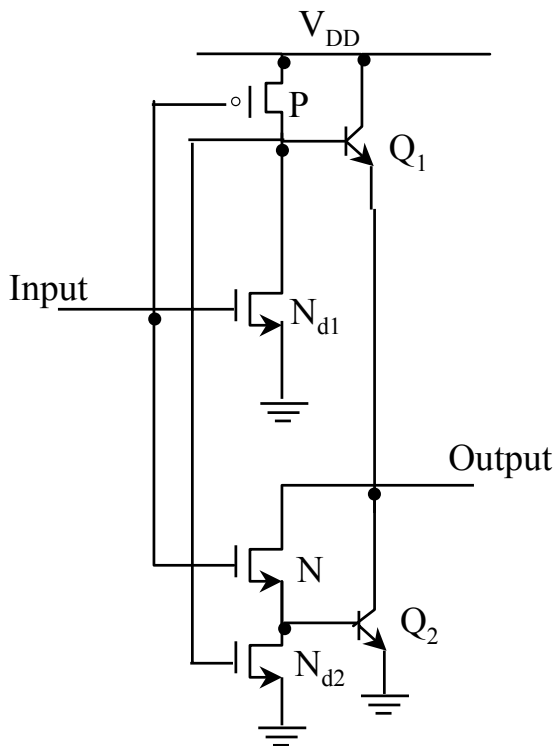1. high density
2. low power

BiCMOS Inverter with MOS Discharge


- Conventional BiCMOS inverter
- First proposed by Hung-Chung Lin
- Swing : $V_{BE} \sim (V_{DD} - V_{BE})$




- Q_1 is reverse-biased when output = “low”
(i.e. $V_{BE1} < 0$ when Output = V_{BE})
 \Rightarrow longer time to turn on Q_1
when Output = “Low” \rightarrow “High”

Improved BiCMOS Inverters

 - Discharges the bases
 - Transistor discharge
 - => Swing : $V_{BE} \sim (V_{DD} - V_{BE})$




- Resistor discharge
 - => Full swing

 



- Many other examples

Resistor-Discharge BiCMOS Inverters

 - a. Path to discharge the bases
- b. Full swing





- Pull-up

  

M2 turned off by input initially
 Q₂ discharged initially
 Q₁ turned off during
 (base is discharged through R₁)

- Pull-down

  


Alternative Full-Swing BiCMOS Inverters

[L. Wissel CICC 1992]

CMOS-compatible BiCMOS logic
Full-swing “finisher” is required

— Latch


Increased power dissipation

 

— CMOS Parallel


High input capacitance

Not partial for all functions

 

— “Feedback”

Added capacitance on base nodes

 


Design Example



[L. Wissel CICC 1992]

● BiCMOS circuit FET vs. NPN size optimization

— Model

 

 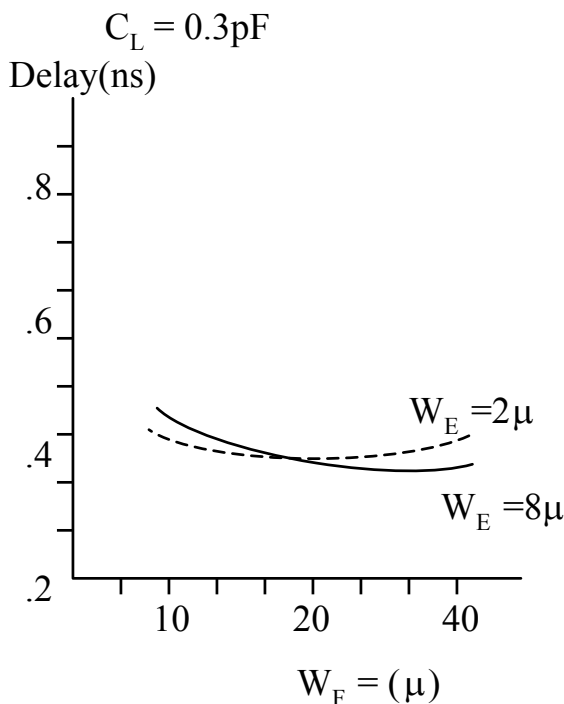
— Delay vs. FET width
(Emitter width as parameter)




Design Example (Cont.)

[L. Wissel CICC 1992]

 - Driving large capacitive load
 - CMOS-BiCMOS comparison
 - layout and speed



- Performance

 


- Layout size


CMOS "A"



CMOS "B"

 

CMOS "C"

 


BiCMOS



BiCMOS Gate

- Basic type

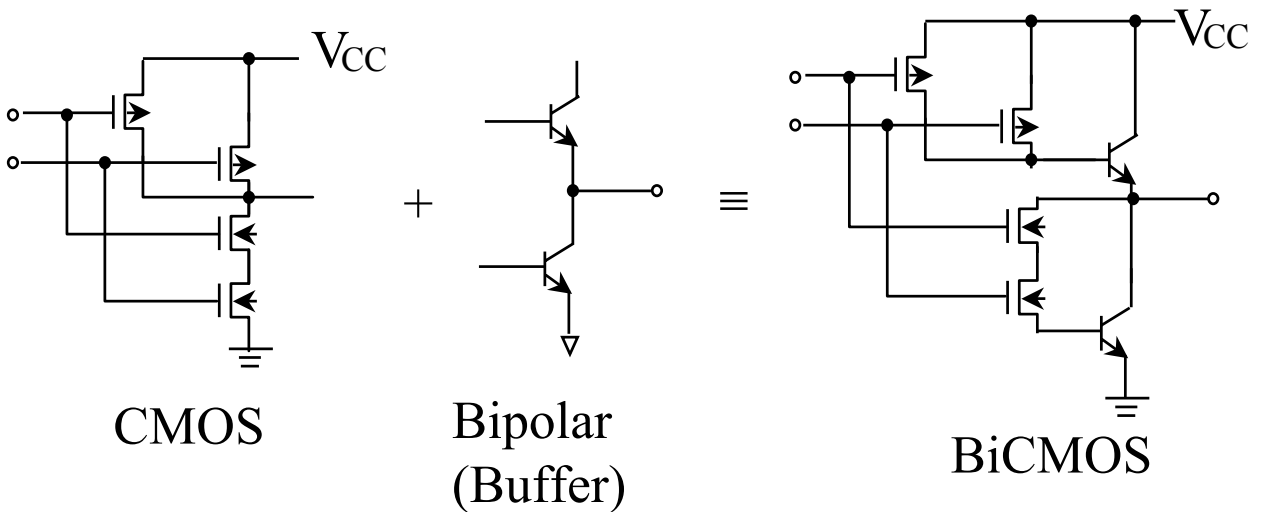


- Similar methods as used in the inverter design


1. delay time calculation
2. path to discharge the bases
3. full-swing

Power-Supply Sensitivity


$V_{DD} = 5.0V$

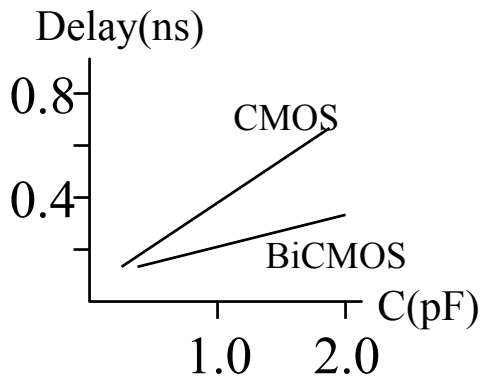


$V_{DD} = 2.5V$

 



Input Waveform

 

Critical switching window

 

Critical switching window

  

Voltage Scaling

● BiCMOS (full swing)

$$-\beta I_{DP} = \beta K_P (V_{DD} - V_{tp})^2 \quad \text{where} \quad k = \frac{\mu C_{ox} W}{2 L}$$

$$\begin{aligned} -\beta I_{DN} &= \beta K_N (V_{DD} - V_{BE} - V_{tn})^2 \\ &= \beta K_n V_{DD}^2 \left(1 - \frac{V_{BE}}{V_{DD}} - \frac{V_{tn}}{V_{DD}}\right)^2 \quad \text{----- (1)} \end{aligned}$$



● CMOS

$$\begin{aligned} -I_{DP} &= K_P (V_{DD} - V_{tp})^2 \\ -I_{DN} &= K_n (V_{DD} - V_{tn})^2 \\ &= K_n V_{DD}^2 \left(1 - \frac{V_{tn}}{V_{DD}}\right)^2 \quad \text{----- (2)} \end{aligned}$$


● From (1) & (2)

$$V_{DD} \downarrow \Rightarrow \left(\frac{1 - \frac{V_{BE}}{V_{DD}} - \frac{V_{tn}}{V_{DD}}}{1 - \frac{V_{tn}}{V_{DD}}} \right) \downarrow \Rightarrow \frac{I_{DN(BiCMOS)}}{I_{DN(CMOS)}} \downarrow$$
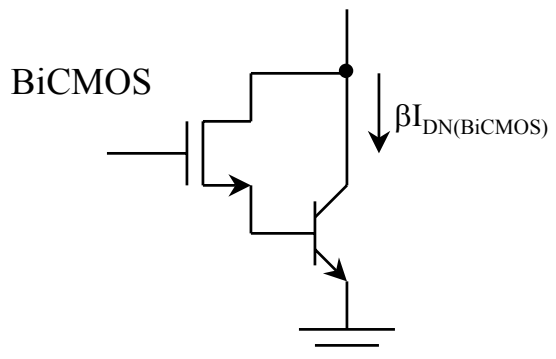 
$$\Rightarrow \frac{\beta I_{DN(BiCMOS)}}{I_{DN(CMOS)}} \downarrow \Rightarrow \frac{t_{d(BiCMOS)}}{t_{d(CMOS)}} \downarrow$$




Low-Voltage BiCMOS Gates

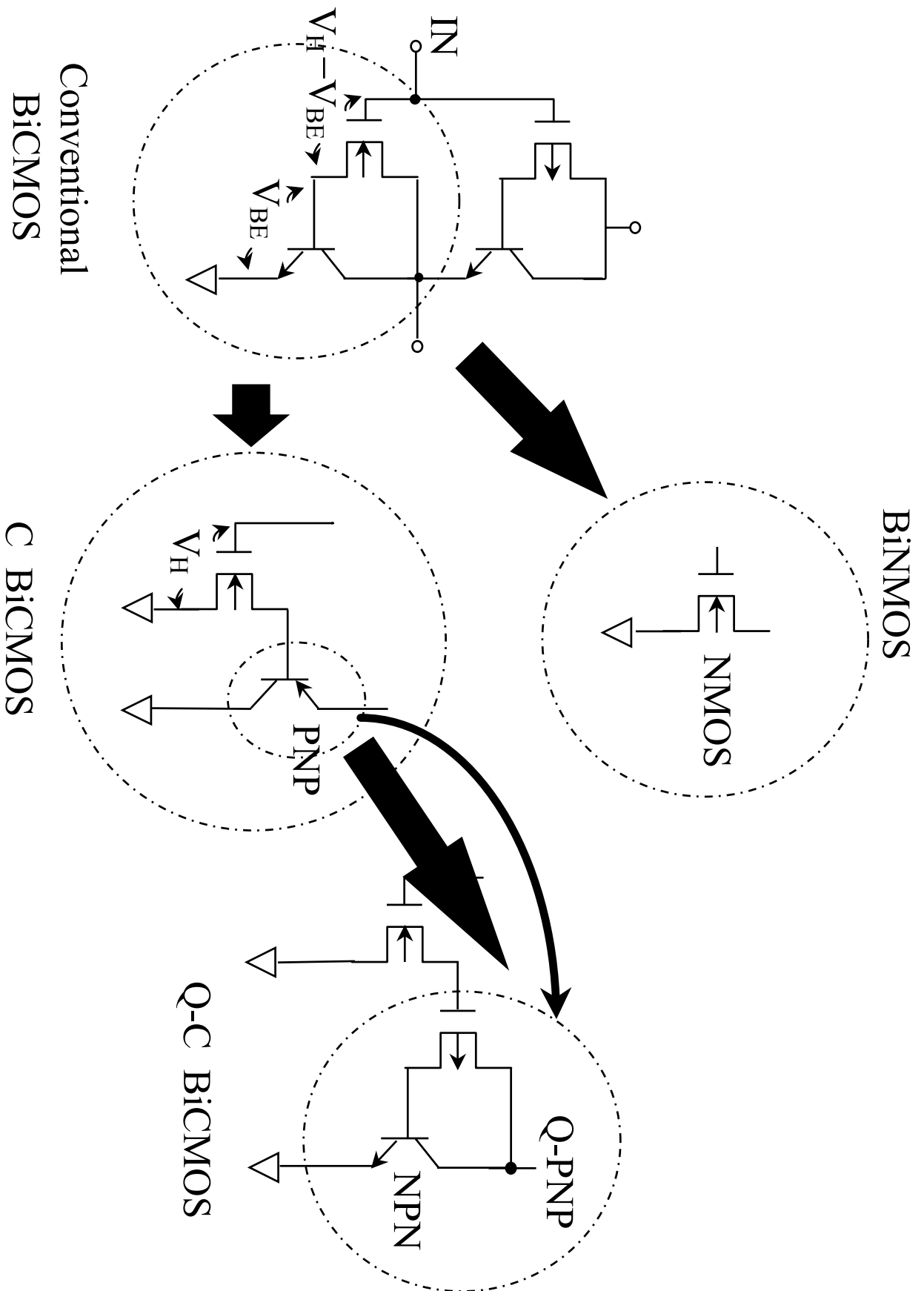

Delay Time


[Y.Kobayshi]

 

$$L_g = 0.3\mu\text{m}, f_T (\text{npn}) = 24 \text{ GHz}, f_T (\text{pnp}) = 10 \text{ GHz}$$

Delay Time (Cont.)

[Y.Kobayshi]

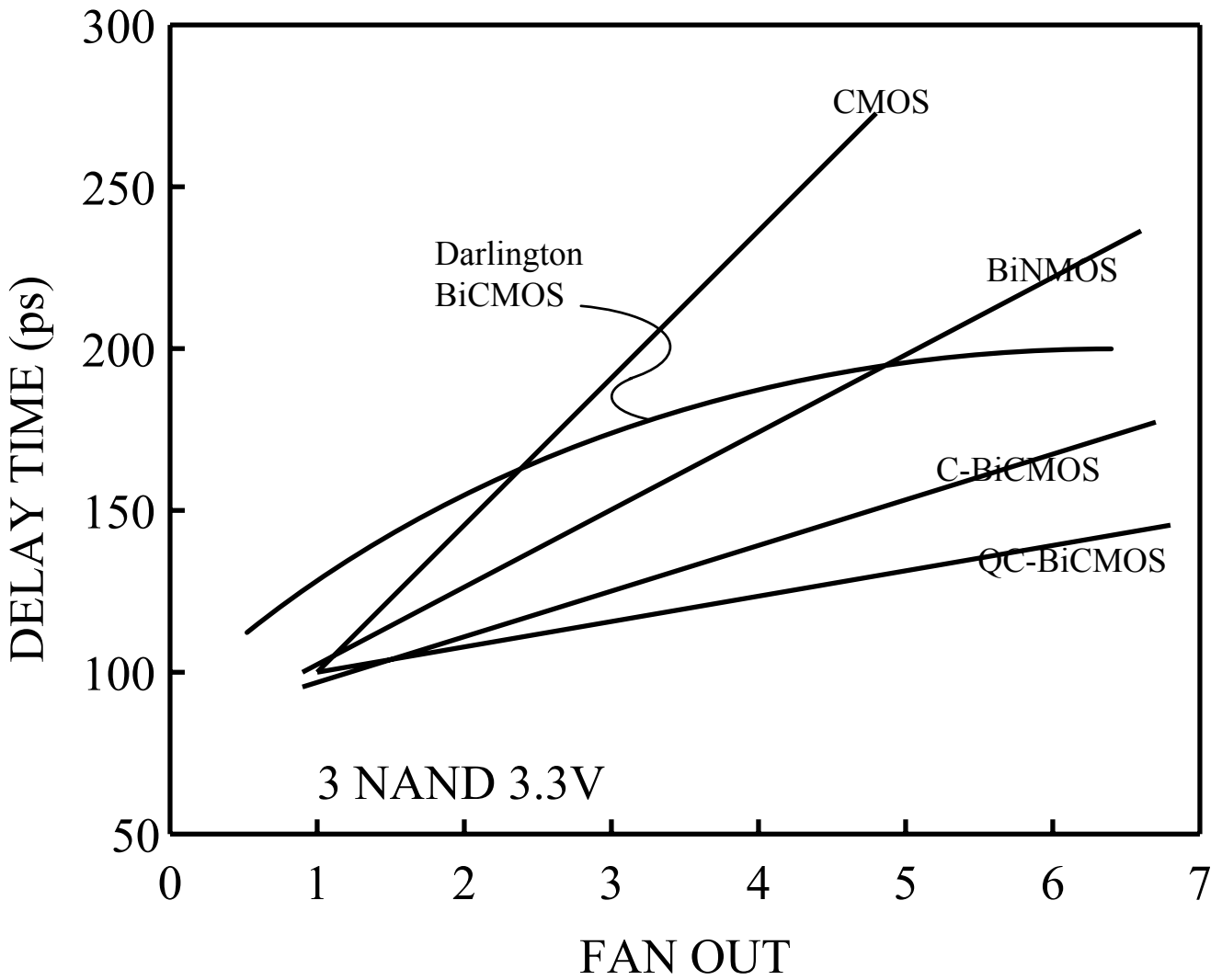


TTL, ECL and CMOS Logic

- Level conversion circuits for different logics
- Input BiCMOS buffers of various logics
- Output BiCMOS buffers of various logics
- Example : ECL-CMOS interface


High Speed BiCMOS IC

- ECL I/O example

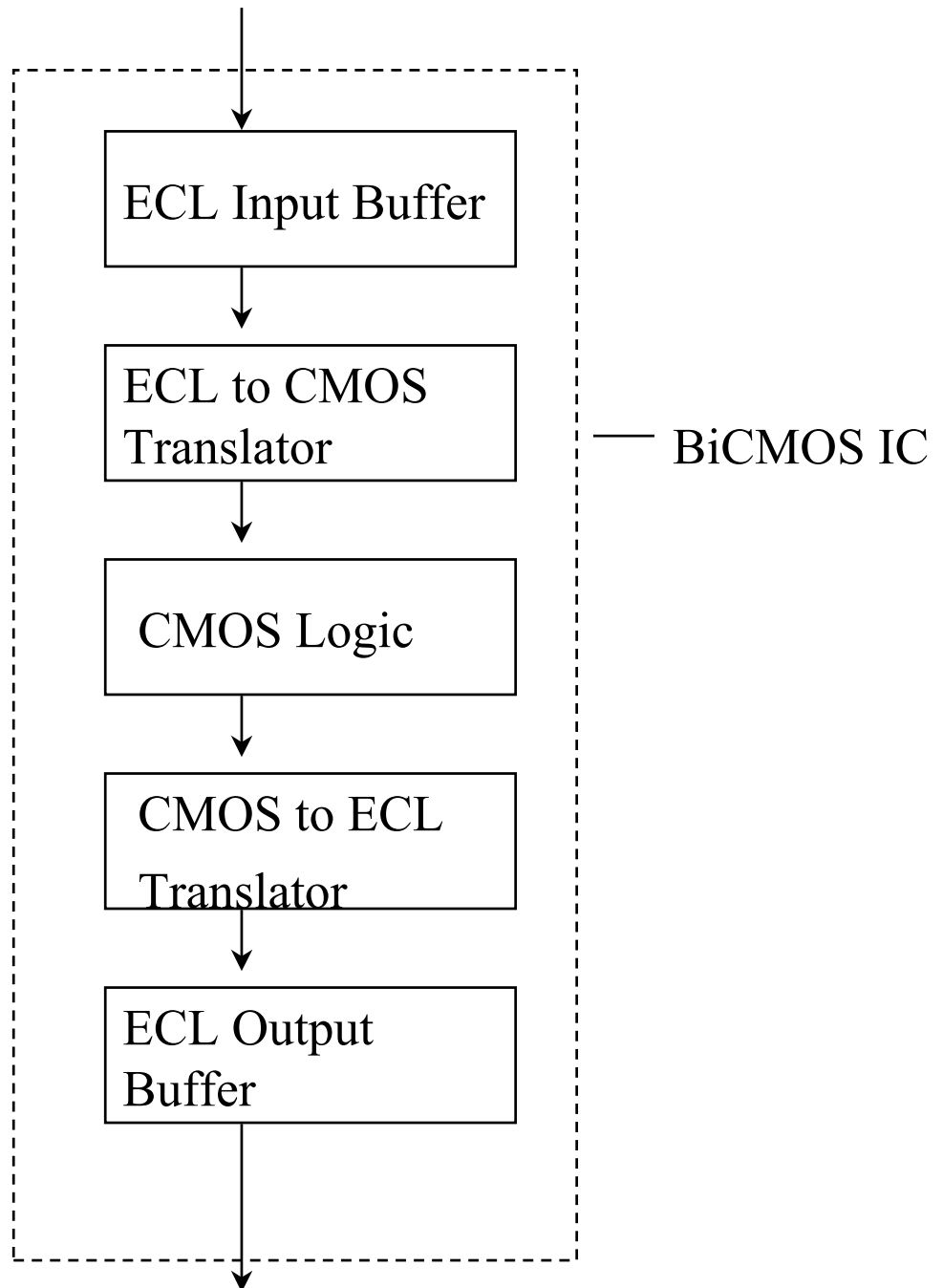


ECL-CMOS Interface

● ECL-to-CMOS converter

 


● CMOS-to-ECL converter

 

Noise Coupling of Mixed ECL/CMOS Circuits


[L.Wissel CICC 1992]

 - Large CMOS waveform couples noise into ECL signal lines
- Model
 - 2 mm quiet ECL line, with partial adjacency to a switching CMOS line



$$C_L = 0.4 \text{ pF}, C_C = 0.07 \text{ pF}$$
 
$$\Delta V_{ECL} = \left(\frac{C_C}{C_L + C_C} \right) \Delta V_{CMOS}$$



- CMOS switching can induce noise as large as ECL signal