

Analog IC Design Homework 6 (1/5)

- 1. Use CIC 0.18um 1.8V Virtual Process SPICE Model (cic018.l)
- 2. Please express the steady-state output (V_{out}) of the **multiplying-by-four gain amplifiers** (as shown in Fig. 1 & Fig. 2) in terms of A , C_1 , C_2 , C_3 , C_4 , V_{in} , V_{CM} , and V_{offset} , and explain the difference between Fig. 1 & Fig. 2.
- 3. Please design the **multiplying-by-four gain amplifiers** (as shown in Fig. 1 & Fig. 2) including two-stage OPAMP, bias circuit and non-overlapped clock circuit (as shown in Fig. 3). Then verify your design with Spectre/HSPICE. Assume $C_1=C_2=C_3=C_4=1\text{pF}$ and $C_L=1.5\text{pF}$
 - ◆ (a) With $V_{in}=V_{CM}+0.025\text{V}$ and $V_{offset}=0\text{V}$
 - ◆ (b) With $V_{in}=V_{CM}+0.025\text{V}$ and $V_{offset}=0.05\text{V}$
- Note
 - ◆ OPAMP and bias circuit should be included in your homework
 - You can use the OPAMP and bias circuit designed in homework 2
 - ◆ Follow design rules of maximum and minimum transistor width and length
 - ◆ Please set the common mode voltage V_{cm} in a reasonable voltage
 - ◆ **Please use Cadence Virtuoso to build schematic and export the .cir file for verification**

Analog IC Design Homework 6 (2/5)

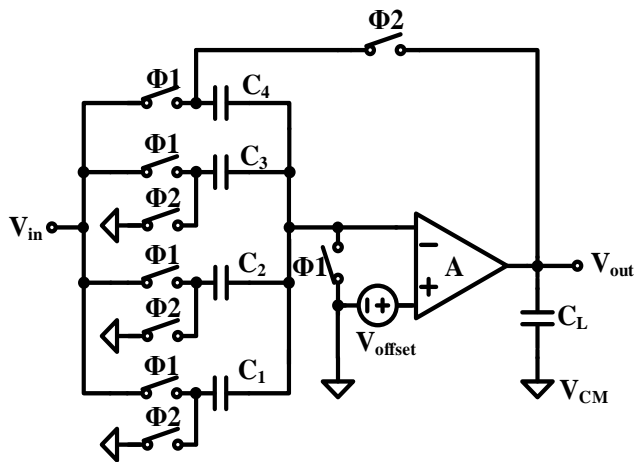


Fig. 1

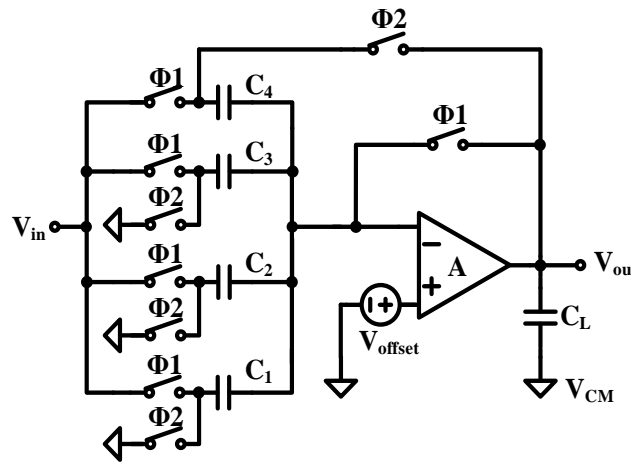


Fig. 2


 
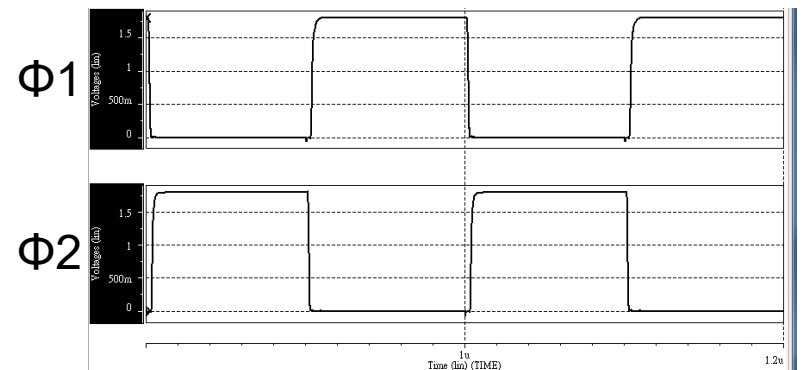


Fig. 3

- You should define the clock characteristics as the one shown in Fig. 3.

$$\text{Accuracy} = \left[1 - \frac{|v_{OUT} - (4v_{IN} - 3V_{CM})|}{4(v_{IN} - V_{CM})} \right] \times 100\% @ t = 1.275\mu\text{s}$$

 - The waveform of V_{out} , $\Phi1$ and $\Phi2$



Analog IC Design Homework 6 (3/5)

- Your report should include
 - ◆ Design flow (Example: The analysis of switches and non-overlap clock circuit)
 - ◆ Spectre/HSPICE verification results
 - The waveform of V_{out} , $\Phi1$ and $\Phi2$
 - Accuracy of the multiplying-by-four gain amplifiers (Please refer to testbench)
 - ◆ Virtuoso schematic (Include the .cir file and circuit diagram)
 - ◆ Total current and power consumption
 - ◆ Area
 - MOSFET: Please calculate the sum of the $W*L$ for all the MOS used in the designed circuit $A_{MOS} = \sum W_i \times L_i$
 - Resistor / Capacitor: Just show the resistance / capacitance (if used)
 - ◆ Table of specifications

	Fig. 1		Fig. 2	
Area (μm^2)				
Power consumption (μW)				
Accuracy (%)	w/o offset	w/ offset	w/o offset	w/ offset

- Note: The total current, power consumption and area should include bias circuits, two-stage OPAMP and non-overlapped clock circuit

Analog IC Design Homework 6 (4/5)

● Grading



- ◆ Customization of the .sp file will not be accepted
- ◆ Please use Virtuoso Spectre or HSPICE to verify your circuit
- ◆ Under the condition of all circuits are composed of MOS, R and C and meet the test conditions, the higher accuracy, area, and power consumption will receive higher scores
- ◆ Please clearly describe the design flow in your report and attach your calculation process (Do not copy)
- ◆ Report with simulation results only but no design flow will get deducted points according to the situation
- ◆ Report with advanced discussion and analysis will receive higher scores

● Precautions

- ◆ Deadline: [12/18/2022 \(Sun.\) 23:59:59 pm](#) (不接受作業補交)
- ◆ Personal work, please upload **Word and Virtuoso library (or HSPICE code)** to moodle
- ◆ Please compress files into a .zip file and name it as HW#_student ID, ex: HW6_E24064088 Font size: 12pt (Chinese: 標楷體, English: Times New Roman)
- ◆ Refer to the IEEE submission regulations, set the picture resolution to 300dpi.
- ◆ Upload file size is recommended to be 2MB

Analog IC Design Homework 6 (5/5)

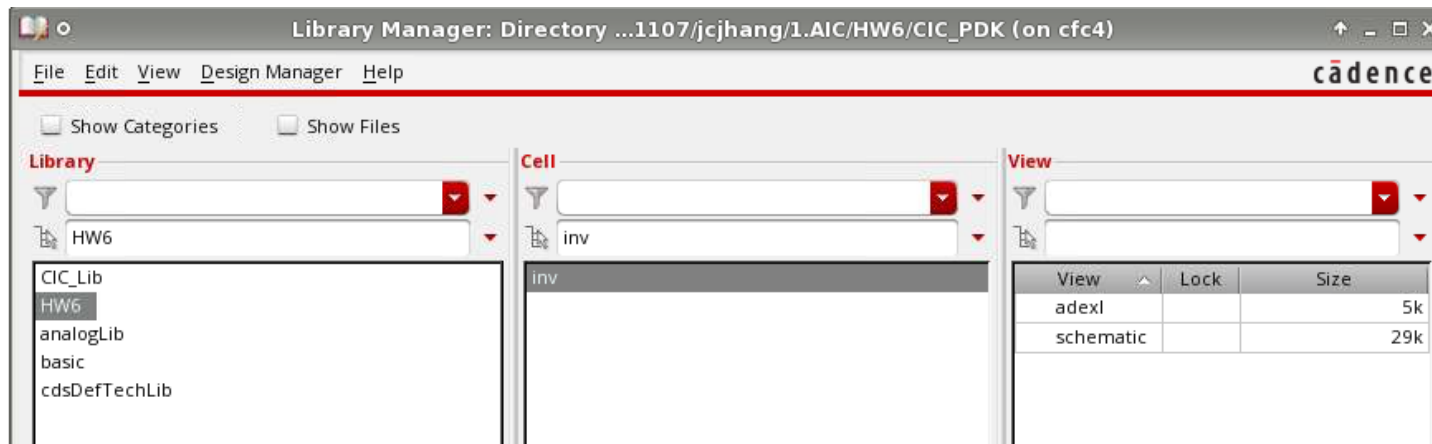
 
- Virtuoso library folder
 - ◆ Add virtuoso folder into the zip file (make sure your file can be opened by virtuoso)




- Use the resistor and capacitor in analogLib library (res, cap)

Appendix 1: Circuits for Reference (1/4)

- Bias circuit & Two-stage OPAMP

  


- Non-overlapped clock circuit

 

Appendix 1: Circuits for Reference (2/4)

Design Flow of Bias Circuit

- Step 1: 設定 I_{M6} 跟 $V_{\text{eff}6}$ → Find $\left(\frac{W}{L}\right)_6$
 - ◆ $I_{M6} = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_6 (V_{\text{gs}6} - V_t)^\alpha (1 + \lambda V_{\text{DS}})$
 - $I_{M6} = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_6 V_{\text{eff}6}^\alpha (1 + \lambda V_{\text{DS}})$
- Step 2: 設定 R → Find $\left(\frac{W}{L}\right)_5$
 - ◆ $V_{\text{eff}6} = V_{\text{eff}5} + I_{M5} * R$
 - ◆ $I_{M5} = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_5 V_{\text{eff}5}^\alpha (1 + \lambda V_{\text{DS}})$
 - ◆ $I_{M5} = I_{M6}$
- Step 3: 設計 $M1 \sim M4$ 之 size，使其操作在飽和區且 V_{eff} 符合限制
- Step 4: 設計 start up circuit

 

Appendix 1: Circuits for Reference (3/4)

Design Flow of Two Stage OPAMP

- Step 1: 決定 C_C (一般 C_C 值會小於 C_L ，太大會增大整體面積，太小會受到雜散電容的影響)
- Step 2: 由 $\varphi_m = 90^\circ - \tan^{-1}(f_t/f_{P2}) = 63^\circ \rightarrow f_{P2} = \frac{g_{m13}}{2\pi C_L} \approx 2 f_t$ 且 $f_t = \frac{g_{m8}}{2\pi C_C} \rightarrow$ 求得 g_{m13}
- Step 3: 由 Slew rate(SR) $< \frac{I_{11}}{C_C}$ & $\frac{I_{12}}{C_C + C_L} \rightarrow C_C$ 已知且SR須同時滿足兩公式 \rightarrow 求得 I_{11} 、 I_{12}
- Step 4: 由 DC Gain $A_0 = \frac{\alpha I_{D8}}{V_{eff8}} (r_{o8} || r_{o10}) g_{m13} (r_{o12} || r_{o13}) \rightarrow I_{12} = I_{13} \rightarrow$ 求得 V_{eff8}
- Step 5: 求出W/L (由上述條件可算出除了 $M_9 \sim M_{10}$ 跟 M_C 的(W/L)值)
 - ◆ M_9 跟 M_{10} 的size決定 V_{gs13} 的大小，調整(W/L) $_{9 \sim 10}$ 得到先前算出的 V_{eff13}
 - ◆ M_C 的size可由設計好的 R_C 值及公式 $R_C = \frac{1}{Kn'(\frac{W}{L})_{M_C} (V_{GS_{M_C}} - V_t)}$ 求出
- Note: n_3 與 V_{out} 的偏壓點會決定 M_8 、 M_{10} 、 M_{12} 跟 M_{13} 的操作區域
 - ◆ 如果 V_{out} 的偏壓點過低，讓 M_{13} 接近Linear region，會影響Gain的大小(ro變小)
 - ◆ 若往下拉力量太強，只要稍微降低 V_{gs13} ，就可以讓 V_{out} 的偏壓點上升
 - ◆ 若 V_{OUT} bias 偏低，可以 $M_9 \uparrow$, $M_{10} \uparrow$ 或 $M_{13} \downarrow$

Appendix 1: Circuits for Reference (4/4)


Information of Slew Rate

- 講義6-29, 6-30所推得結果: Slew rate(SR) = $\frac{I_{11}}{C_c}$ → 不完全適用於這次作業


- ◆ 因為講義上之範例，第二級為ideal OP且無 C_L

- ◆ 當 I_{12} 足夠大 → Slew rate(SR) = $\frac{I_{11}}{C_c}$

 - ◆ 當 I_{12} 不夠大 → Slew rate(SR) < $\frac{I_{11}}{C_c}$ & $\frac{I_{12}}{C_c + C_L}$






- Rising & Falling 之 Slew rate(SR)

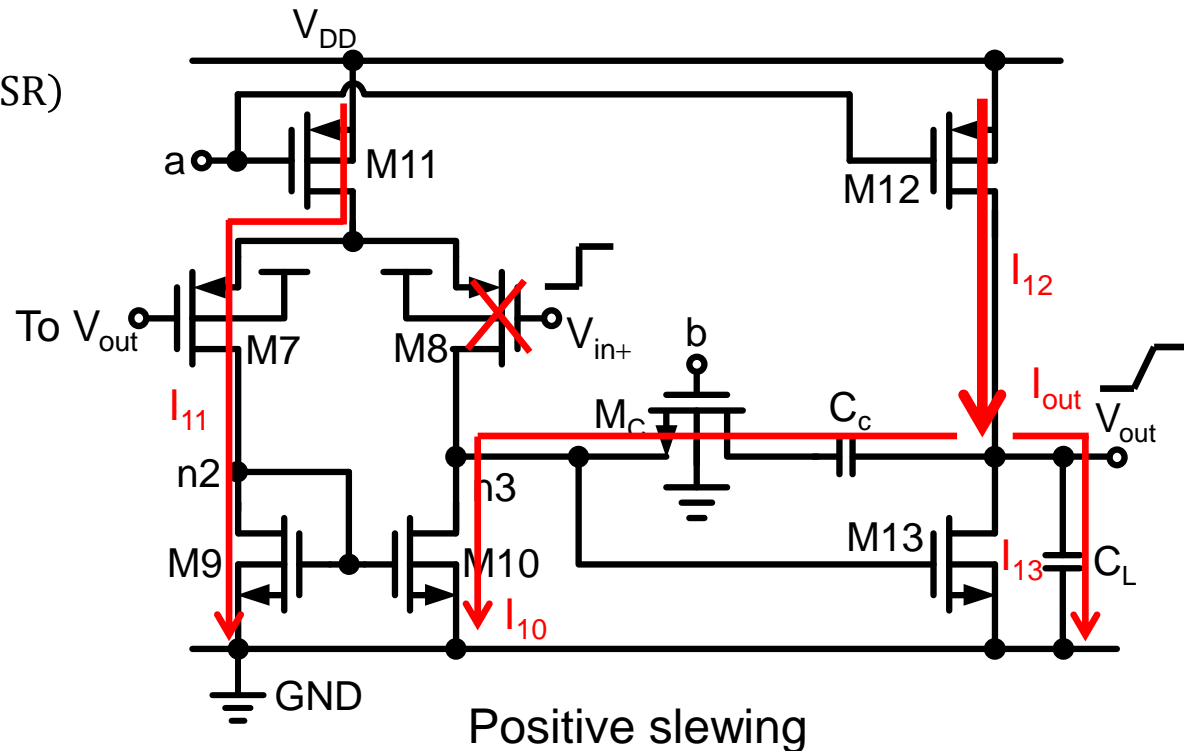




Appendix 2: Virtuoso Spectre Simulator (1/12)

- Terminal: cd CIC_PDK (0.18um virtual process virtuoso library)
- Terminal: source sourceMe
- Terminal: virtuoso & → Create a Library for CIC018 Model

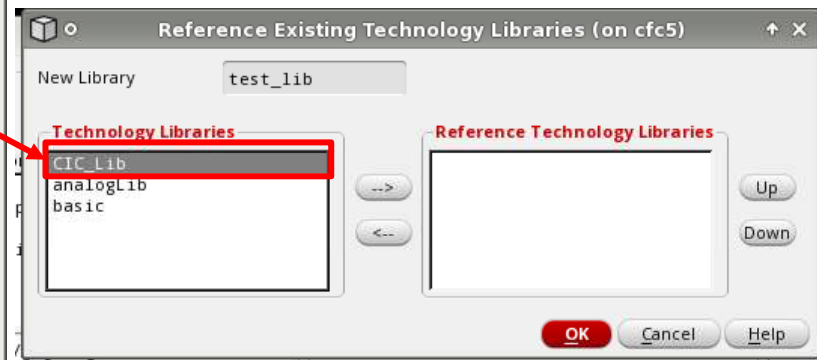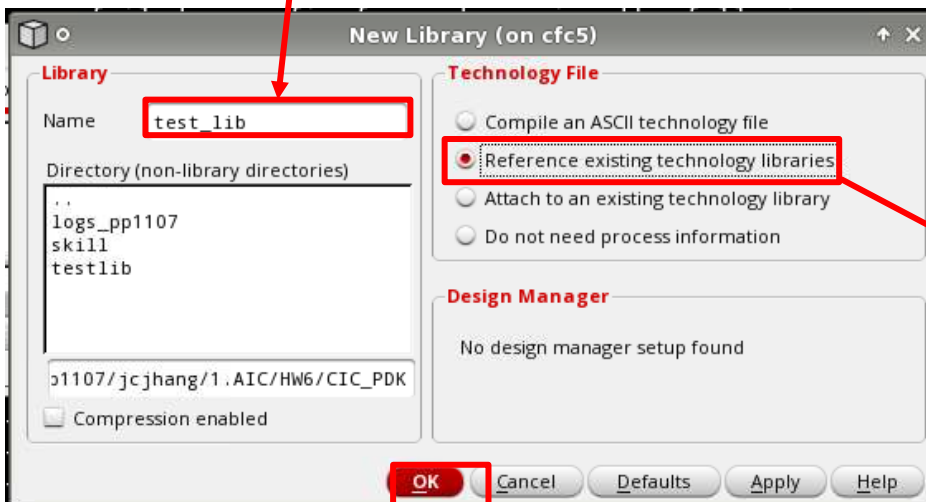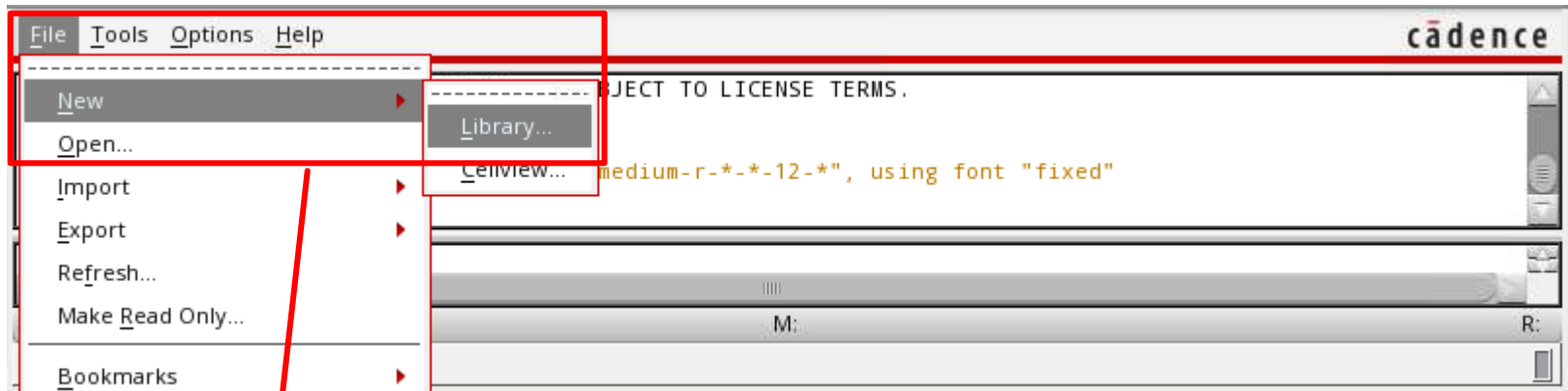



Appendix 2: Virtuoso Spectre Simulator (2/12)

- Create Cell View

  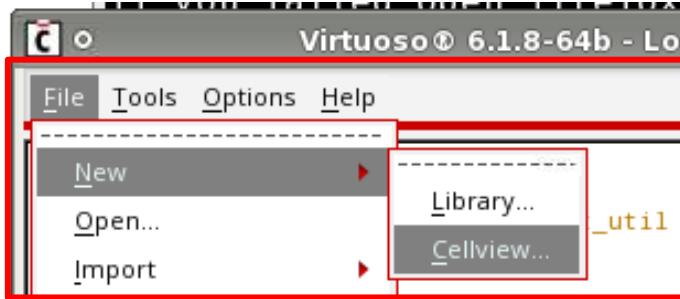


Appendix 2: Virtuoso Spectre Simulator (4/12)

- Editing Interface → Add an Instance (Press 'i' to add instance)
- Press 'q' to edit object properties → Please show properties in your schematic circuit

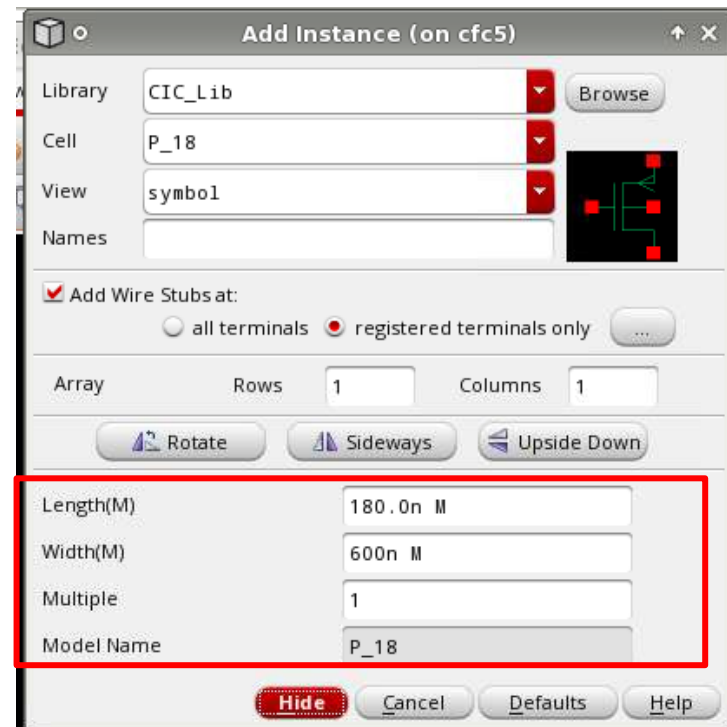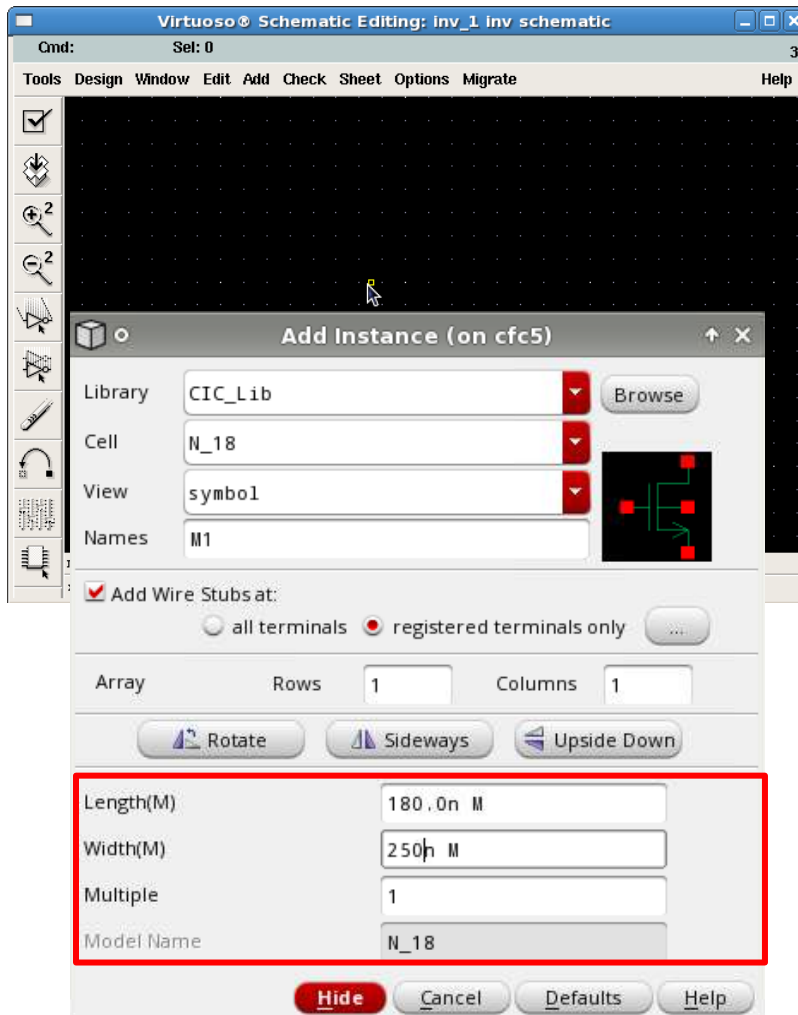

Appendix 2: Virtuoso Spectre Simulator (5/12)

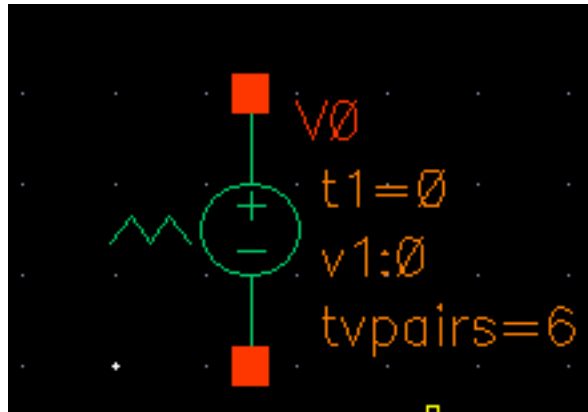- Piece-Wise Linear Voltage Source (Cell name: vpwl)
 - ◆ In analogLib



Property Value

Library Name analogLib

Cell Name vpwl

View Name symbol



Instance Name V0

CDF Parameter	Value
Frequency name for 1/period	
Number of pairs of points	6
Time 1	0 s
Voltage 1	0 V
Time 2	1u s
Voltage 2	0 V
Time 3	1.5u s
Voltage 3	1.8 V
Time 4	2.5u s
Voltage 4	1.8 V
Time 5	3u s
Voltage 5	0 V
Time 6	4u s
Voltage 6	0 V



Period of the PWL 4u s

Appendix 2: Virtuoso Spectre Simulator (6/12)

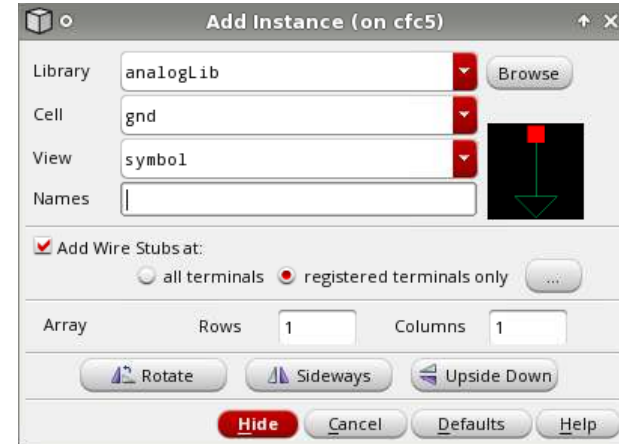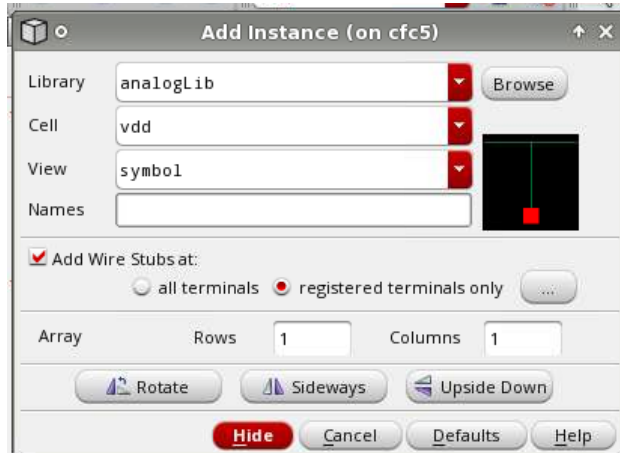- Global VDD and GND (Cell name: VDD and GND)





- Set VDD as 1.8V → Add a 1.8-V DC voltage source (Cell name: VDC)

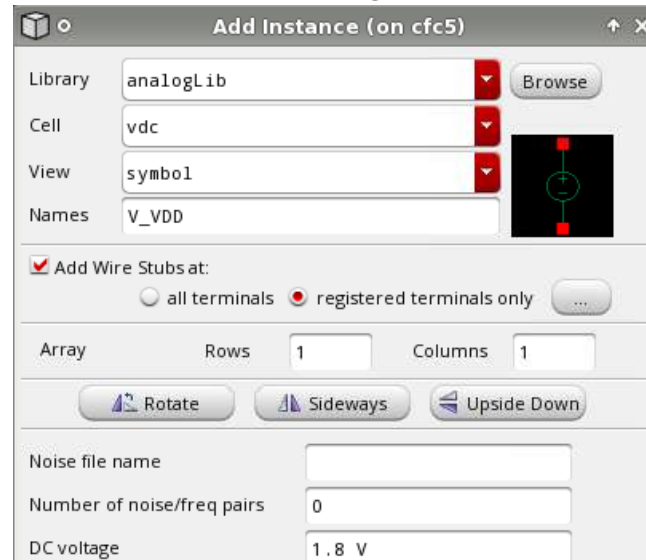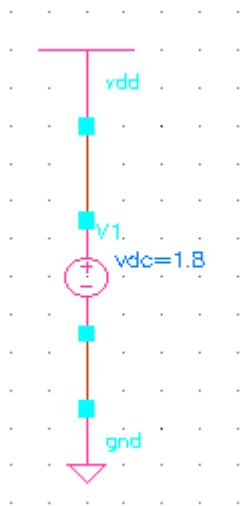


Appendix 2: Virtuoso Spectre Simulator (7/12)

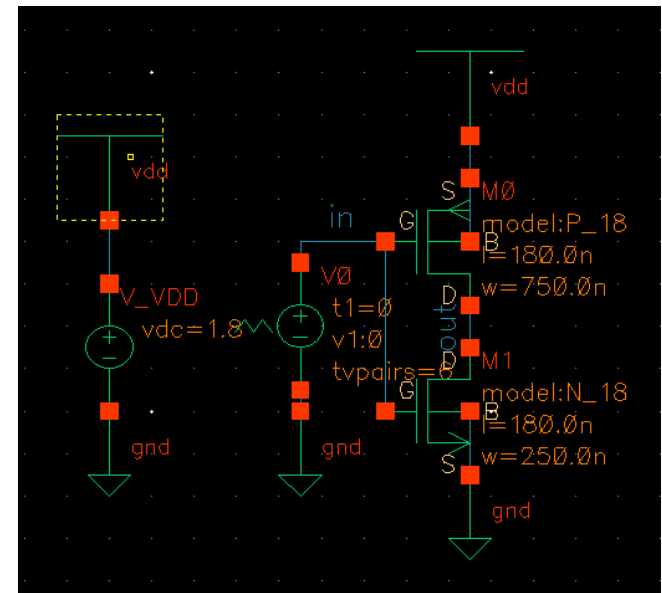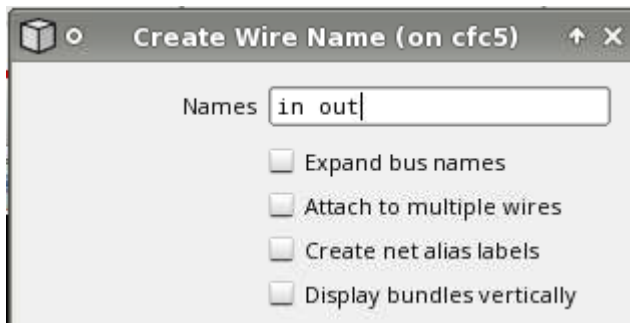- Wiring and Wire Name setting
 - ◆ 'w' for wiring
 - ◆ 'l' (lower case of L) for adding wire name
 - Attach the auxiliary line to the wire to be named




- Simulation by Spectre
 - ◆ Check and save it before using spectre for simulation → Launch → ADE XL

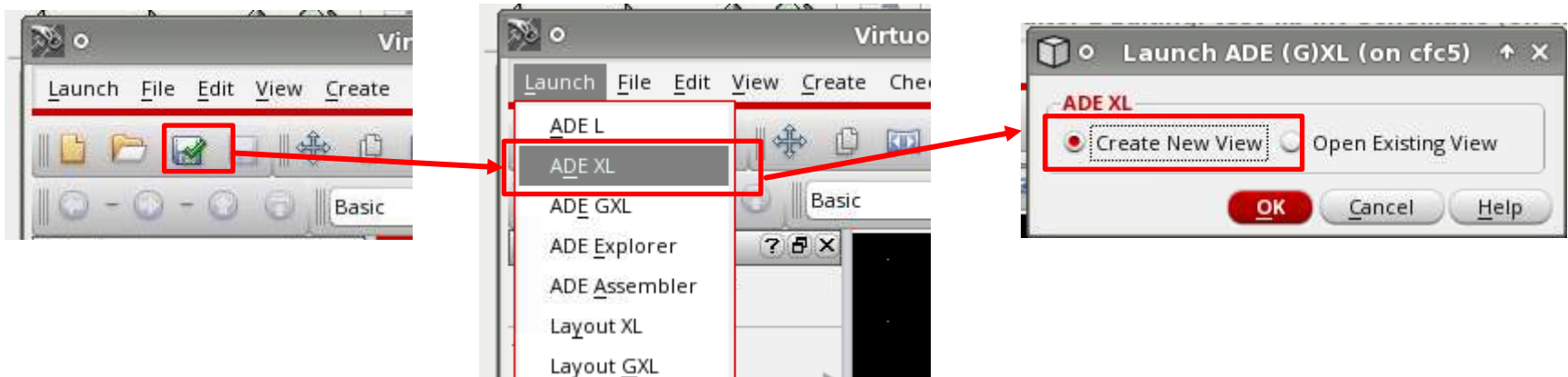


Appendix 2: Virtuoso Spectre Simulator (8/12)

- Create a test for the schematic



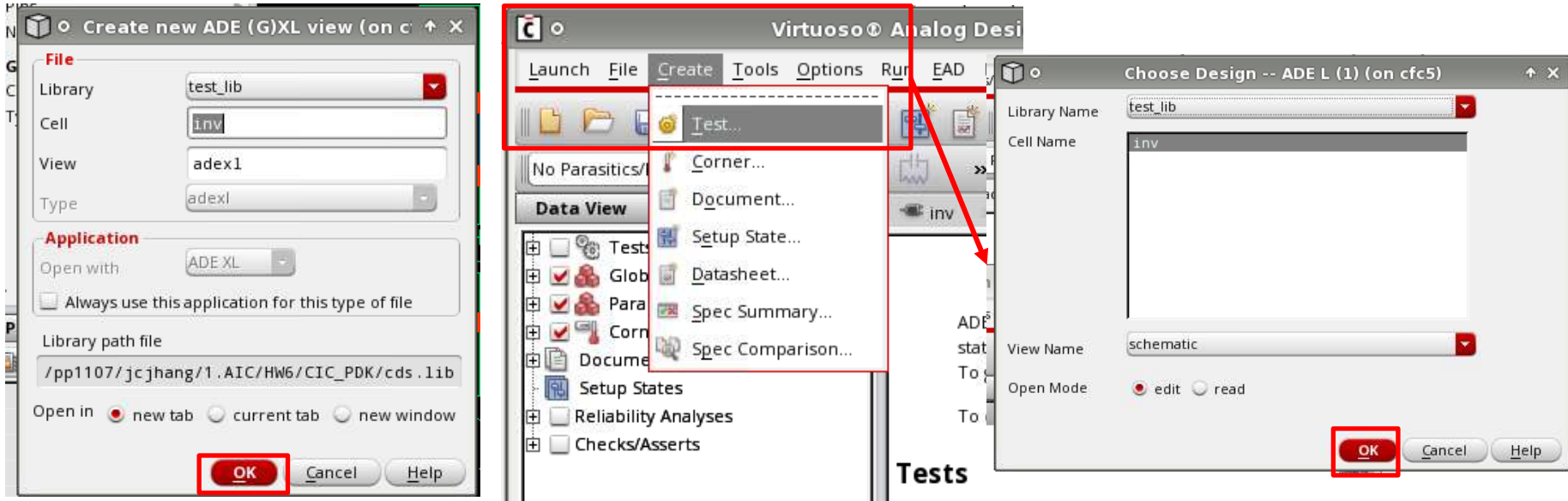


- Select CIC018 Model

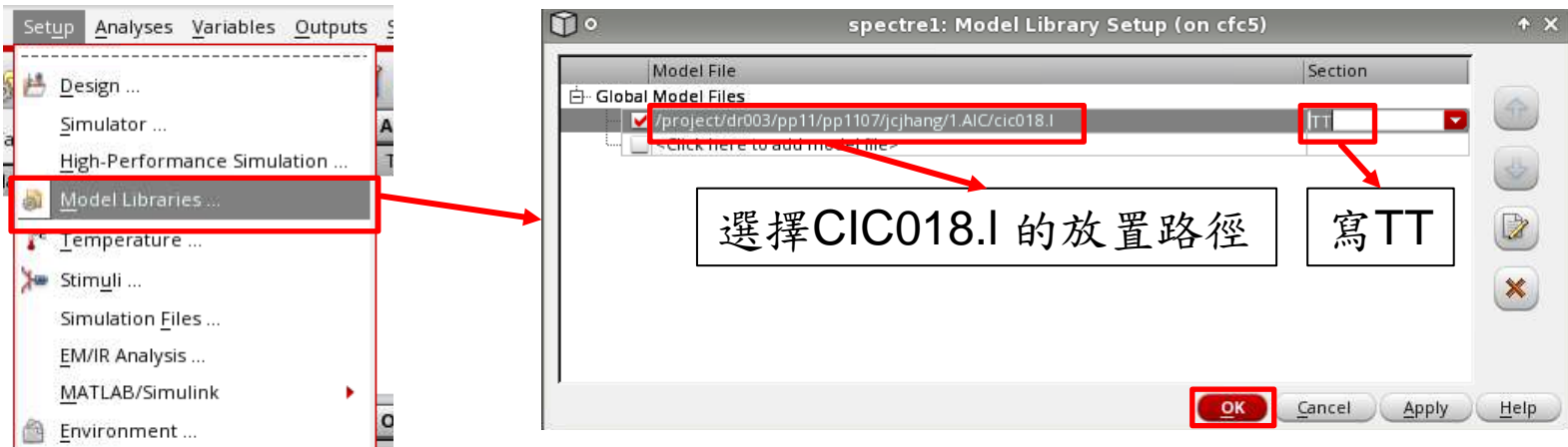



Appendix 2: Virtuoso Spectre Simulator (9/12)

- Choose Analysis: .tran (Transient) → Plot Result → Click the wire to be plotted
- Press 'ESC' after selection

 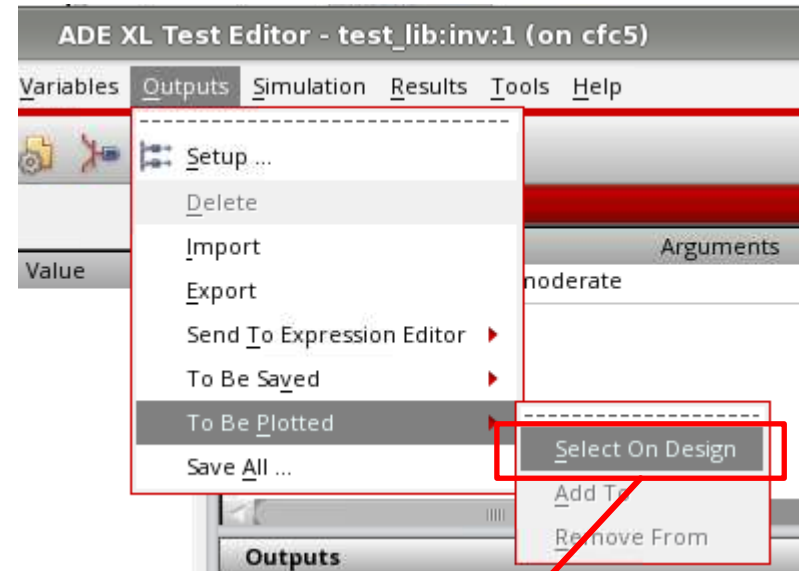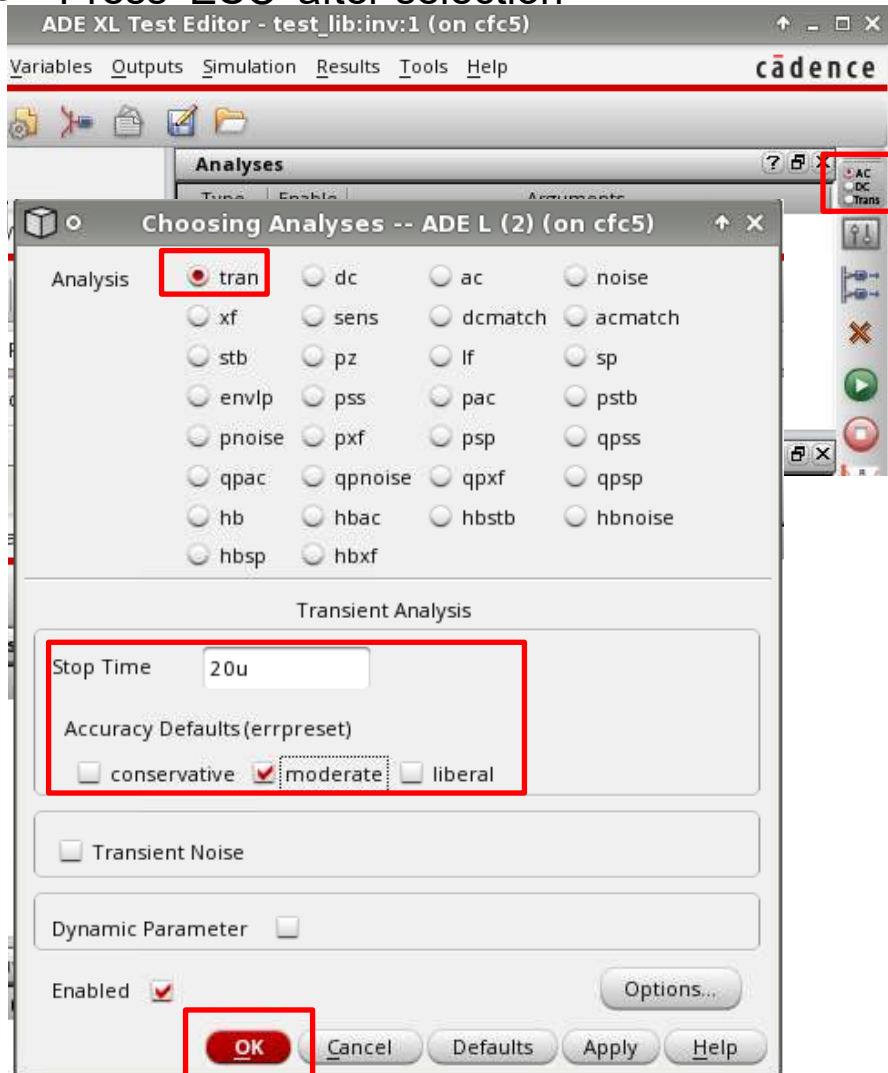


Appendix 2: Virtuoso Spectre Simulator (10/12)

- Run Simulation → Waveform Window

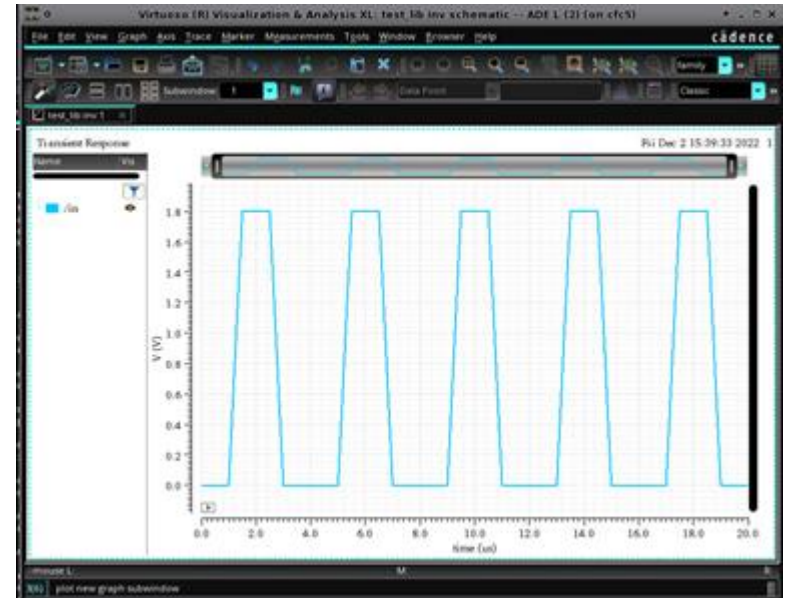
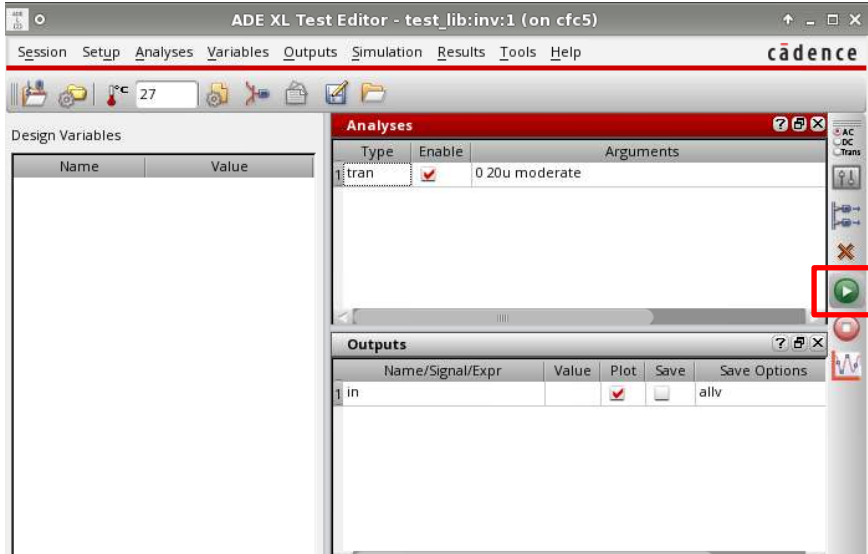


- Delete → Delete output variable

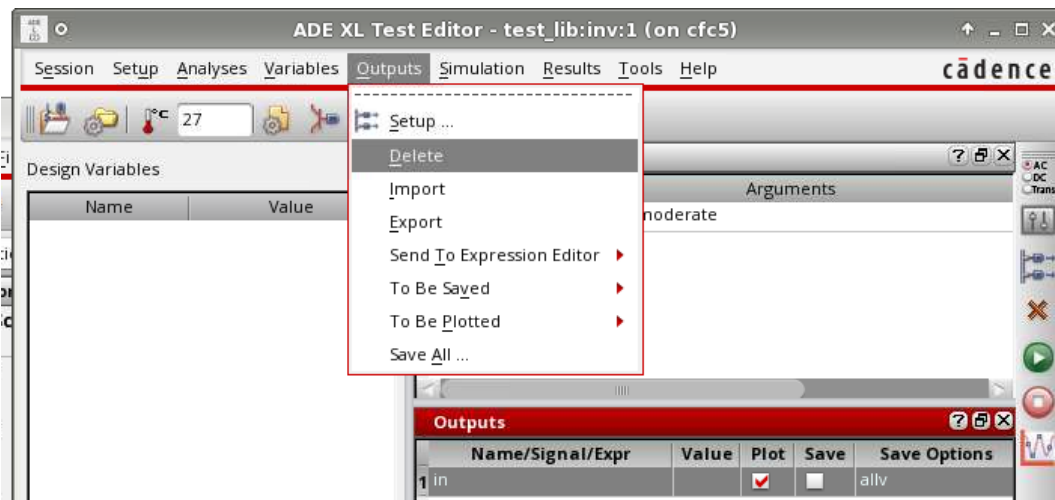

Appendix 2: Virtuoso Spectre Simulator (11/12)

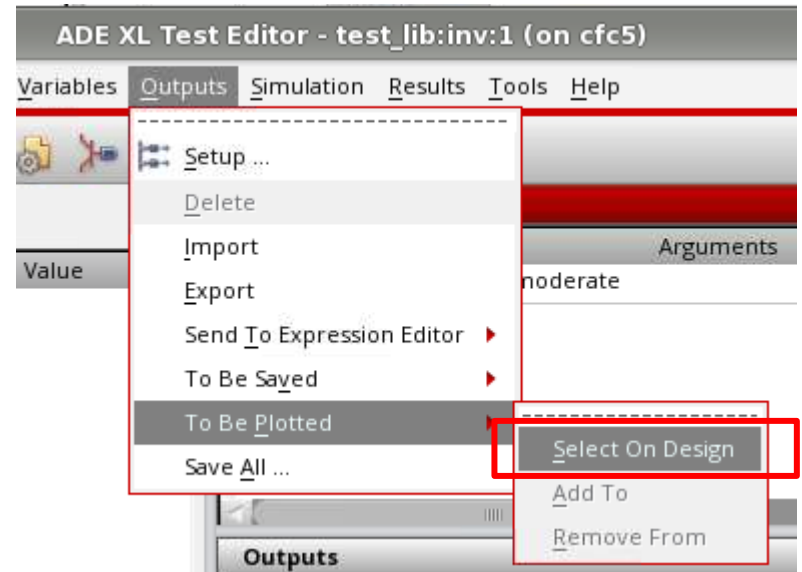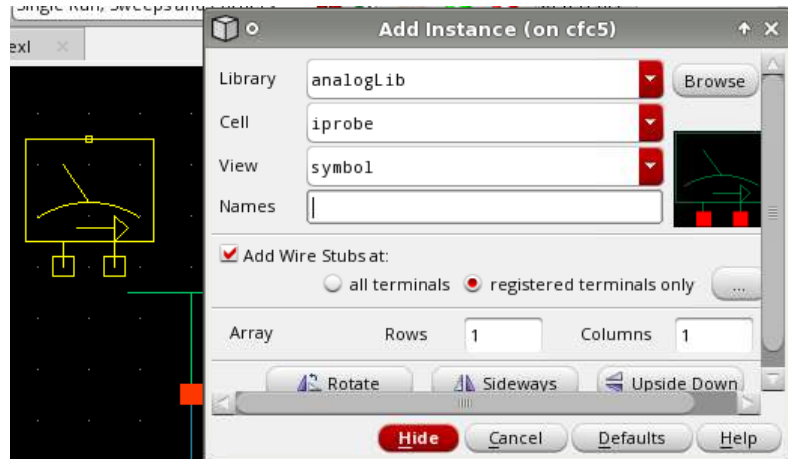- Way 1 to get power: iprobe in analogLib



- 點iprobe component

