

1. For the system in Fig. P1(a), the sampling frequency  $f_s$  of the ideal ADC is 150 kHz and the spectrum of  $x_a(t)$  is shown in Fig. P1(b).

(a) Please design the cut off frequency  $\omega_c$  of the ideal low pass filter shown in Fig. P1(c) to avoid the aliasing effect when the down-sampling factor is 3. (5%)

(b) Please plot the spectra of,  $x_d[n]$ ,  $x_{LPF}[n]$  and  $x_{out}[n]$ , respectively (You need to mark the magnitude and corresponding frequency on each spectrum). (15%)

 


Fig. P1(a)

 


Fig. P1(b)

 


Fig. P1(c)

2. Briefly describe the following questions.

(a) Draw a latched comparator circuit. Explain why its input hysteresis, i.e., memory effect, exists. (5%)

(b) Please draw the circuit diagram of a 3-bit flash A/D converter. Explain what problems should be noticed in designing this type of ADC (List at least 2 problem). (10%)

(c) Please draw the circuit diagrams of a 3-bit binary-weighted DAC and a thermometer-code current-steering DAC. Please evaluate the maximum DNL and gain-error for these two DACs' in (a), respectively. Assume the maximum mismatch error of 1:1 current mirror is  $\pm 1\%$ . (20%)

(d) List and briefly explain a S/H circuit design with signal-independent switch errors. Please give 2 methods to minimize signal-dependent switch error, and explain how they work. (10%)

(e) Please explain the pre-filtering and post-filtering strategies for conventional high-resolution signal-processing systems utilizing Nyquist-rate ADCs and DACs, respectively. (20%)

(f) Please explain the pre-filtering strategies for conventional Nyquist-rate A/D converters (5%) and oversampling A/D converters. Explain the bandwidths chosen for the filters used. (5%)

(g) Draw the cross section of the parasitic PNP and the circuit diagram of CMOS N-well bandgap voltage reference operating in weak inversion. Derive an equation to express the reference voltage  $V_{ref}$ . Channel length modulation effect can be ignored. Please explain why a bandgap voltage reference is temperature independent. (10%)

3. What is the SNR of an ideal 12-bit unipolar ADC with  $V_{REF}=0.8V$  when a sinusoidal input of  $0.15V \sim 0.65V$  is applied? (5%) What size input ( $V_{pp}$ ) would result in an SNR of 35dB? (5%)

4. A sinusoidal input of  $0.8V_{pp}$  is applied to an ideal N-bit unipolar ADC with  $V_{ref}=1V$ . If the requirement of SNR is at least 70dB, please calculate the minimum bit number N and find SNR when the amplitude of sinusoidal input is changed to  $60mV_{pp}$ .

5. A Multiplying DAC (MDAC) and the waveform of its non-overlapped clock is shown in Fig. P5 (a) and Fig. P5 (b), respectively. In an ideal case, the MDAC output can be expressed as  $V_{out}=2V_{in}$ . However, in an actual case, the opamp finite DC gain,  $A$ , parasitic capacitor of opamp input node,  $C_p$ , and capacitor mismatch,  $C_s \neq C_f$ , would degrade the accuracy of the MDAC output.

(a) Please express the MDAC output in term of  $A$ ,  $C_s$ ,  $C_f$ ,  $C_p$  and  $V_{in}$ . (10%)

(b) Assuming  $C_f=C_s=C$  and  $C_p=1/20C$ , please calculate the minimum opamp DC gain  $A$  such that  $|2V_{in}-V_{out}|$  is less than  $0.001V_{in}$ ? (5%)

 


Fig. P5(a)

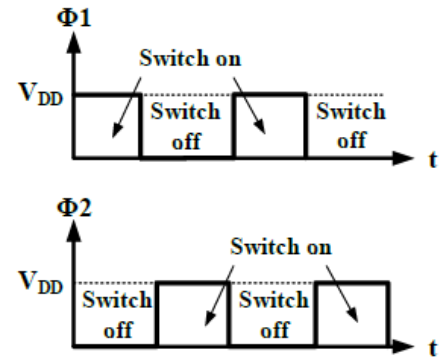


Fig. P5(b)

6. Fig. P6 shows a 3-bit R-2R-based DAC. Due to mismatch effect, the resistance of  $R_A$  and  $R_B$  are  $0.9R$  and  $1.1R$  respectively. Assume that the opamp is ideal,  $V_{REF}=1.8V$  and  $R_f=R$ . (Hint: Compared with ideal R-2R-based DAC)

(a) Find the offset and gain errors in unit of LSB. (6%)

(b) Find the INL (endpoint) errors in unit of LSB. (12%)

(c) Find the DNL errors in unit of LSB. (12%)

(d) Is this DAC monotonic? Why? (5%)

 


Fig. P6

7. Consider a 3-bit D/A converter in which  $V_{REF} = 1.2V$  (that is, 000 refers to 0V and 111 refers to 1.05V), with the following measured voltage values:  $\{ 0.031 : 0.204 : 0.312 : 0.467 : 0.619 : 0.814 : 0.802 : 1.124 \}$

(a) Find the offset and gain errors in unit of LSB. (10%)

(b) Find the INL (endpoint) errors in unit of LSB. (10%)

(c) Find the DNL errors in unit of LSB. (10%)

(d) Is the input/output transfer curve of the D/A converter monotonic? Why? (5%)

8. Fig. P8(a)~(c) shows a 5-bit modified successive approximation A/D converter which operates in different mode.
- According to Fig. P8(a)~(c), please describe the operation. (6%)
  - According to Fig. P8(a)~(c), please calculate the  $V_x$  value in terms of  $V_{in}$ ,  $V_{ref}$  where parasitic capacitance ( $C_p$ ) at node  $V_x$  can be ignored. (9%)
  - Assume parasitic capacitance ( $C_p$ ) at node  $V_x$  can be ignored. Please derive the digital output ( $b_1 \sim b_5$ ) where  $V_{in} = 1.15V$  and  $V_{ref} = 2V$ . (5%)
  - Assume parasitic capacitance ( $C_p$ ) of  $3C$  exists at node  $V_x$ . Please calculate the  $V_x$  value where  $b_1 \sim b_5$  is switch to the digital output calculated in (b). (5%)

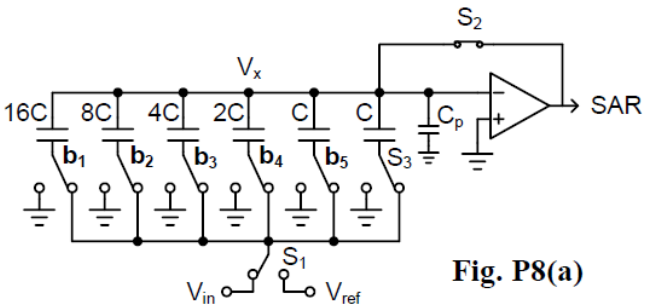


Fig. P8(a)

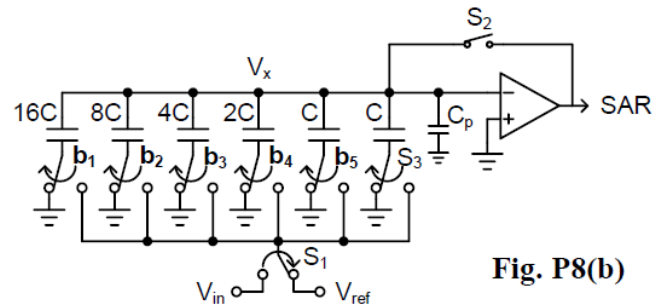


Fig. P8(b)

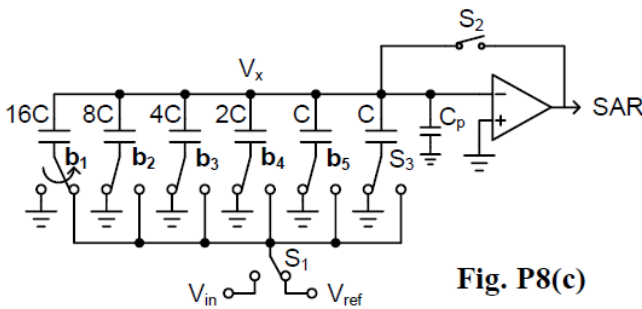


Fig. P8(c)

9. The deterministic approach for calculation of ADC quantization noise is shown in Fig. P9(a). A ramp input signal ( $V_{in}(t)$ ) is injected into the ADC and the staircase output signal ( $V_{out}(t)$ ) is the output of an ideal DAC converting the ADC digital output ( $B_{out}$ ). Quantization error ( $V_Q(t)$ ) can be given as  $V_{out}(t) - V_{in}(t)$ . Both  $V_{in}(t)$  and  $V_{out}(t)$  for the ideal 2-bit ADC is shown in Fig. P9(b). (No overloading is assumed.)
- Please plot  $V_Q(t)$  for the ideal 2-bit ADC and mark upper bound, lower bound, and timing. (10%)
  - Please derive root mean squared quantization error  $V_Q(rms) = V_{LSB}/\sqrt{12}$ . (10%)
  - Please derive SNR of N-bit ideal ADC under sine input signal with a peak-to-peak amplitude  $V_{ref}$ , where  $SNR(N\text{-bit}) = 6.02 \cdot N + 1.76$  (dB). (10%)

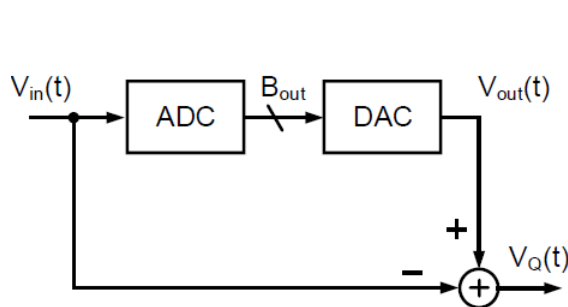


Fig. P9(a)

 


Fig. P9(b)

10. For a 4-bit R-2R-ladder DAC converter shown in Fig. P10, what is the output error (in LSBs) when input digital word is  $\{b_1 b_2 b_3 b_4\} = \{1 1 0 0\}$  and  $R_A$  is  $1.98R$  instead of ideal  $2R$ ?

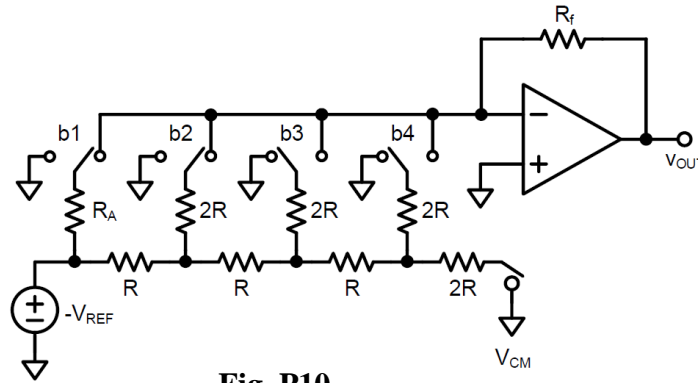


Fig. P10

11. Consider the multiply-by-two gain circuitry shown in Fig. P11.

- (a) For  $C_1$  is twice the capacitance of  $C_2$ , and assuming the opamp has an input offset designated as  $V_{off}$ , find the values of  $V_{C1}$ ,  $V_{C2}$  and  $V_{out}$  at the end of each of the phases shown. (8%)
- (b) What is the value of  $V_{out}$  when  $C_2$  is twice the capacitance of  $C_1$  at the end of the Phase4 ? (2%)
- (c) How to obtain  $V_{out} = 3 V_{in}$  with this circuit ? (5%)

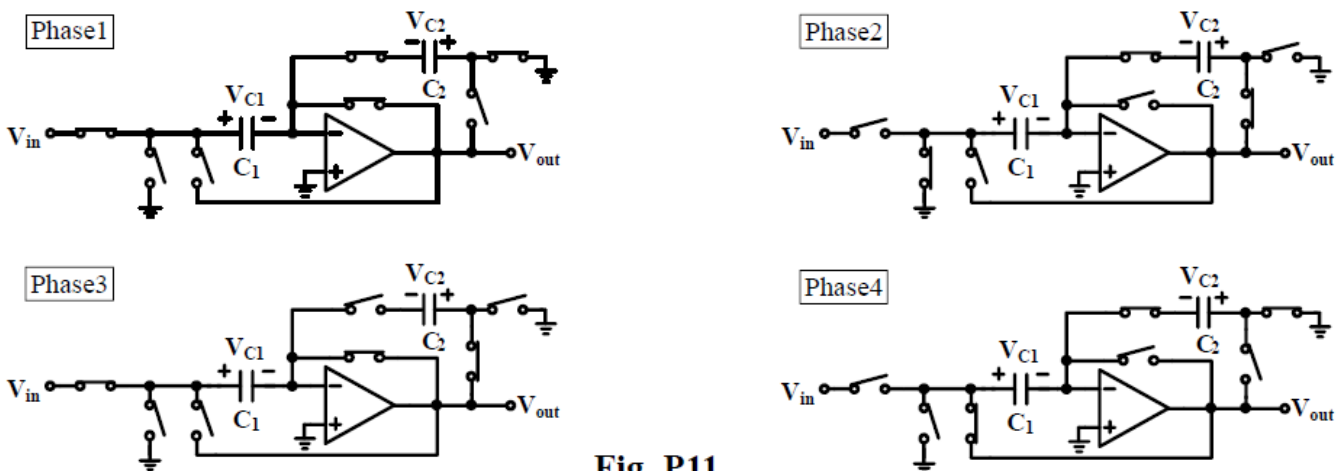


Fig. P11

12. Use  $C_H$ ,  $\mu_n C_{OX}$ ,  $(W/L)$ ,  $V_{DD}$  and NMOS threshold voltage ( $V_T$ ) to answer question (a) and (b).

- (a) In Fig P12 (a), please explain why an NMOS sampler passes a weak "1" and find the typical maximum output level of it. (5%)
- (b) For the sampling circuit in Fig. P12 (b), please derive the output voltage  $v_O$  as a function of time ( $t$ ),  $C_H$ ,  $\mu_n C_{OX}$ ,  $(W/L)$ ,  $V_{DD}$  and NMOS threshold voltage ( $V_T$ ), where the initial output voltage is assumed to be  $v_O(t=0) = V_{DD}$ . (Neglect early effect and body effect.) (15%) Hint: MOS current in

$$\text{triode region: } I_D = \frac{1}{2} \mu_n C_{OX} \left( \frac{W}{L} \right) \{ V_{DS} [ 2(V_{GS} - V_T) - V_{DS} ] \}$$

 


Fig. P12(a)

 


Fig. P12(b)

13. Two switched-capacitor integrators are shown in Fig. P13(a) and Fig. P13(b), where the non-overlapping clocks,  $\Phi_1$  and  $\Phi_2$ , for both of them are depicted in Fig. P13(c). An extra switch near the output is shown to indicate that output signal is valid at the end of  $\Phi_1$ . If the offset voltage  $V_{OFF}$  modelled at the non-inverting input are taken into consideration and the OPAMPs are assumed to be ideal, please

- (a) Derive the z-domain transfer function of  $V_{in}$  to  $V_{out}$  for Fig. P13(a) (7%)
- (b) Derive the z-domain transfer function of  $V_{in}$  to  $V_{out}$  for Fig. P13(b) (8%)
- (c) List 2 advantages of the integrator in Fig. P13(b) compared with the one in Fig. P13(a) (5%)

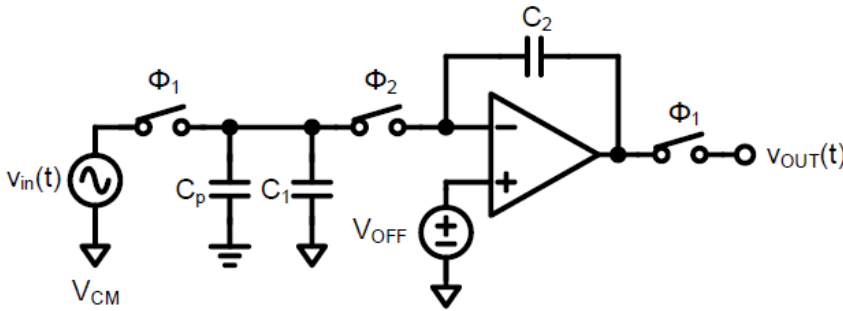


Fig. P13(a)

 


Fig. P13(c)

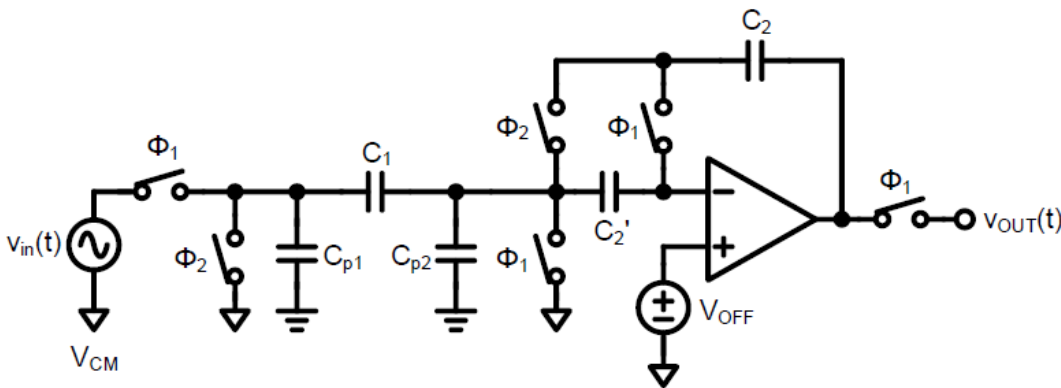


Fig. P13(b)

14. As shown in Fig. P14, the comparator is operated with offset cancellation, where  $C_{in}$  is the input capacitance of the OPAMP and  $A_o$  is the OPAMP gain. Assume that the three switches are ideal.

- (a) Briefly describe how this circuit operates. (5%)
- (b) Please derive  $V_{out}$  in terms of  $V_{in}$ ,  $C_{main}$ ,  $C_{parasitic}$ ,  $C_{in}$  and  $A_o$ . (5%)
- (c) If the two terminals of  $C$  are interchanged, derive  $V_{out}$  in terms of  $V_{in}$ ,  $C_{main}$ ,  $C_{parasitic}$ ,  $C_{in}$  and  $A_o$ . (5%)
- (d) Based on the derivations in (b) and (c), which placement of  $C$  is the better choice? (5%)

 
 


Fig. P14

15. A multiplying DAC (MDAC) of pipelined ADCs is shown in Fig. P15(a), where  $C_s=3C_f$ . Fig. P15(b) shows the corresponding non-overlapped waveforms. Neglect the effects of finite slew rate of OPAMP.

- (a) Assume the OPAMP has a finite dc gain of 60dB and an infinite unity-gain bandwidth, please calculate the gain of MDAC. (10%) If the gain error,  $|4V_{in}-V_{out}|$ , is less than  $0.002V_{in}$ , please find the minimum required OPAMP dc gain. (5%)
- (b) Assume the OPAMP has an infinite dc gain and a finite unity-gain bandwidth  $\omega_u$ , where the OPAMP transfer function  $A(s) = \frac{\omega_u}{s}$ . Please calculate the minimum required  $\omega_u$  such that 0.1% settling error in a time of 10ns can be achieved. (10%)

**Hint :**  $\mathcal{L}^{-1}\left[\frac{1}{s\left(1+\frac{s}{\alpha}\right)}\right] = (1-e^{-\alpha t}) \cdot u(t)$ , where  $u(t)$  is a unit step function.

 


Fig. P15(a)

 


Fig. P15(b)

16. As shown in Fig. P16, there is a multiplying-by-four gain amplifier. The accuracy of the amplifier is influenced by OPAMP's offset voltage  $V_{offset}$ , OPAMP's noise  $V_{n\_op}(t)$  and reference voltage's noise  $V_{n\_vcm}(t)$ . Assuming the gain of the OPAMP is infinite.

- (a) Only considering the offset voltage  $V_{offset}$ , briefly describe how the circuit reduces the offset voltage  $V_{offset}$ . (5%)
- (b) Only considering the OPAMP's noise  $V_{n\_op}(t)$ , please derive the z-domain transfer function of  $V_{n\_op}$  to  $V_{out}$  and plot the gain v.s. frequency. (5%)
- (c) Only considering the reference voltage's noise  $V_{n\_vcm}(t)$ , please derive the z-domain transfer function of  $V_{n\_vcm}$  to  $V_{out}$  and plot the gain v.s. frequency. (5%)

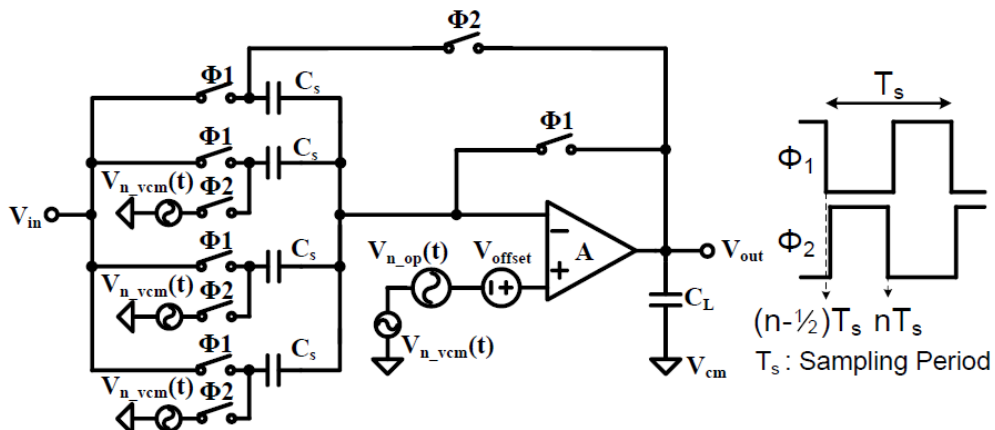


Fig. P16

17. For the circuit diagram shown in Fig. P17, please draw its ideal input/output characteristic, i.e., transfer curve and explain how the gain-error and offset-error are generated.

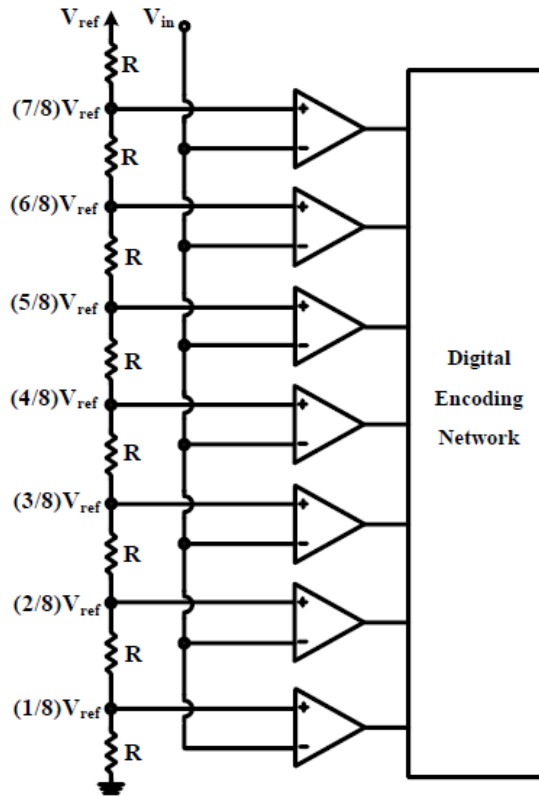


Fig. P17

18. Fig. P18(a) is a signal processing system including a switch-capacitor filter (SCF), an A/D converter, an ideal digital low pass filter (LPF), and a down-sampler. The ADC sampling rate  $f_s$  is 50kHz. The circuit of SCF is shown in Fig. P18(b), where  $f_c = 1/T_C = 500\text{kHz}$  and the ideal OPAMP has infinite dc gain and infinite unity-gain bandwidth. The frequency spectrum of the LPF response is shown in Fig. P18(c), where  $\omega_u$  is LPF cut-off frequency.

- Derive the s-domain transfer function of  $V_{in}$  to  $V_{out}$  and its unity-gain frequency by using  $\omega$ ,  $C_1$ ,  $C_2$ , and  $T_C$  in Fig. P18(b). Assume  $\omega T_C \ll 1$ .
- Derive the minimum  $C_2/C_1$  ratio for SCF to prevent A/D converter from aliasing.
- Derive the maximum output frequency (unit: Hz) of  $Y_{out}$  to reconstruct signal without aliasing.

 


Fig. P18(a)

Fig. P18(b)

 


Fig. P18(c)

19. (a) Consider an 6-bit binary-weighted resistor D/A converter composed of  $R_1, R_2, \dots, R_6$ , where all resistor tolerances are  $\pm 5\%$ . Please derive the worst-case differential nonlinearity in units of LSBs and if the D/A converter can be guaranteed to be monotonic? Why?
- (b) A 12-bit binary-weighted resistor D/A converter composed of  $R_1, R_2, \dots, R_{12}$  produce a glitch voltage of  $-0.5V$  when digital code changes from  $100\dots00$  to  $011\dots11$  because MSB switch turns off early. Please derive the glitch voltage when MSB switching if a thermometer-code approach is used for the top 7 bits, whereas binary-weighting is used for the remaining 5 bits.