

D/A Converters

Nyquist-Rate D/A Converts

- Four main types
 - ◆ Decoder-based
 - ◆ Binary-weighted
 - ◆ Thermometer-code
 - ◆ Hybrid


Decoder-Based DAC

- Most straight forward approach
 - ◆ Create 2^N reference signals and pass the appropriate signal to the output
- Three main types
 - ◆ Resistor string
 - ◆ Folded resistor-string
 - ◆ Multiple resistor-string

Resistor-String DAC

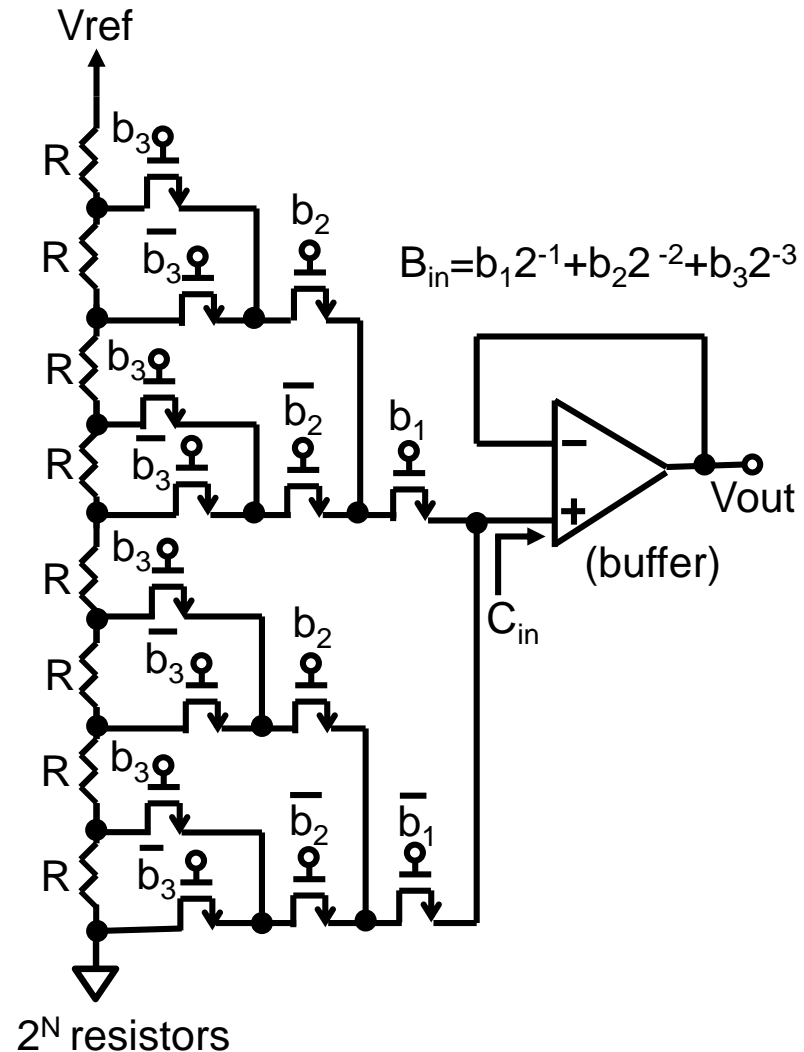- Example 1: a 3-bit DAC with transmission-gate, tree-like decoder

- ◆ Transmission gates might be used rather than n-channel switches
 - Extra drain and source capacitance (to GND) is offset by the reduced switch resistance
 - Larger layout
 - Can operate closer to positive supply voltage
- ◆ Only n-channel switches are used
 - About the same speed as the transmission gate implementation
 - Compact layout (no contacts are required in the tree)



Resistor-String DAC (Cont.)

- ◆ Monotonicity is guaranteed (if the buffer's offset does not depend on its input voltage)
- ◆ The accuracy of this DAC depends on the type of resistor used. Polysilicon (20-30 Ω /square) have up to 10-bit of matching accuracy.
- ◆ Speed:
Can be estimated using open-circuit time-constant approach (refer to microelectronics textbook by Sedra and Smith V.7 p.733, Ch.9)

Time constant

$$\approx 3R_{tr}C_{tr} + 2 \times 3R_{tr}C_{tr} + \dots + N \times 3R_{tr}C_{tr}$$


$$= \frac{N(N+1)}{2} \times 3R_{tr}C_{tr}$$

where R_{tr} is on resistance of switches

C_{tr} is drain or source capacitance of switches

N is bit number

 e.g. $N=6 \rightarrow 63R_{tr}C_{tr}$, $N=7 \rightarrow 84R_{tr}C_{tr}$



Resistor-String DAC (cont.)


- Example 2: a 3-bit DAC with digital decoding

- ◆ Compared to Example 1

- Higher speed
 - More area for decoding circuit


- ◆ Speed:

 - Time constant $\approx R_{tr} \cdot (2^N + 1) C_{tr}$
 - For $N \leq 6$ Example 2 is faster
 - For $N > 7$ Example 1 is faster




- Compromise between Examples 1 and 2

- ◆ Folded resistor-string DAC

 


Folded Resistor-String DAC

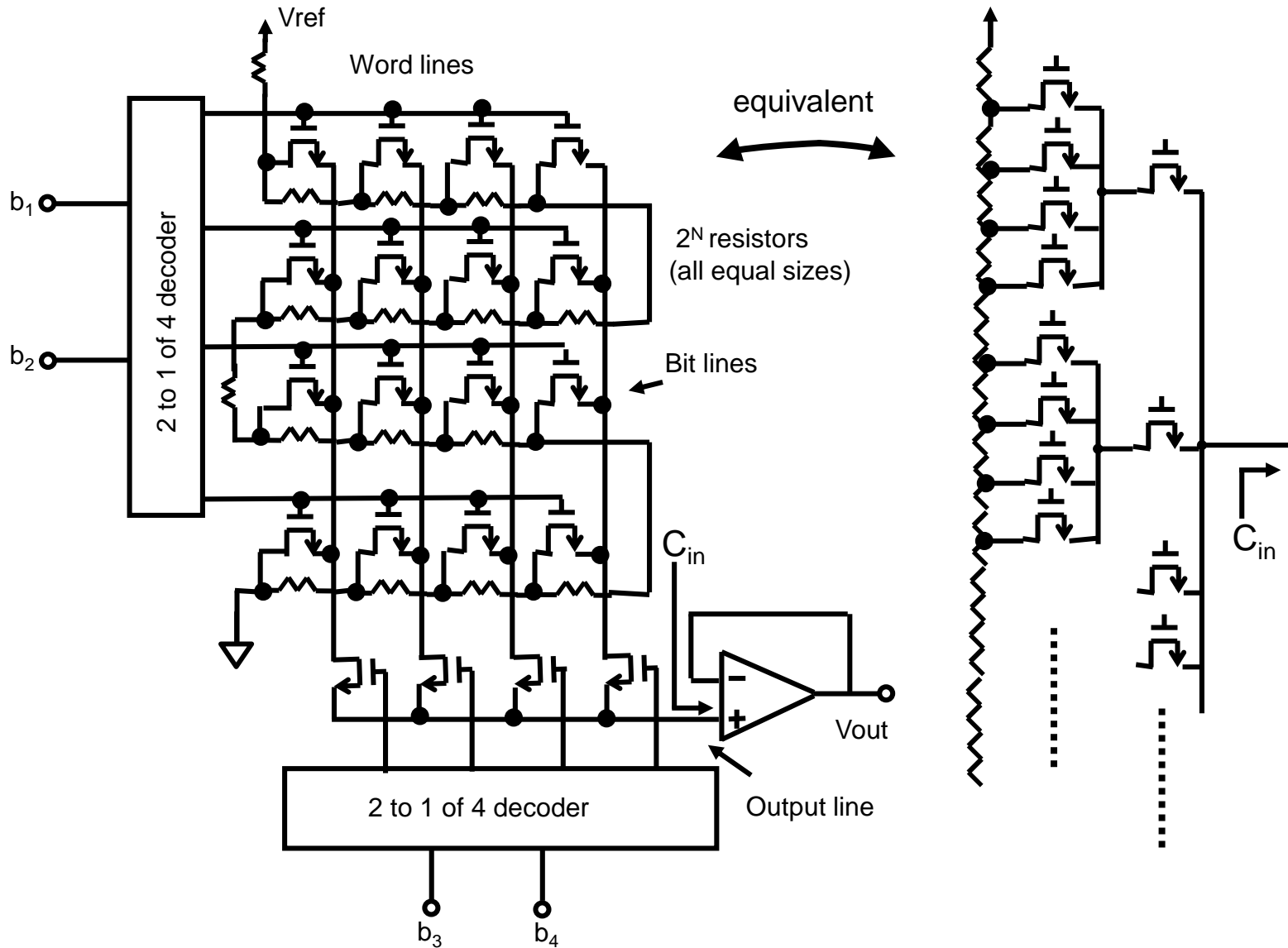

Folded Resistor-String DAC (Cont.)

 
- Reduce the amount of digital decoding
- Reduce large capacitive loading
- Decoding is very similar to that for a digital memory
- Example:
 - ◆ 4 bits (=2 bits+2 bits) DAC
 - ◆ Time constant $\approx R_{tr} (2^2+1)C_{tr} + 2 R_{tr} (2^2+1)C_{tr}$



- Other design examples
 - ◆ 12 bits=6 bits+6 bits, or 4 bits+4 bits+4 bits, or.....
 - ◆ 10 bits=5 bits+5 bits, or 3 bits+3 bits+4 bits, or.....
 - ⋮
etc.

Multiple Resistor-string DAC

 - 6-bit example
- Requires only $2 \cdot 2^{N/2}$ resistors
- Monotonic if OPAMPs have matched, voltage-insensitive offset voltages.
- For high speed, OPAMPs must be fast.
- For high resolution, OPAMPs must be low noise.
- The matching requirements of the second resistor string are not nearly as severe as those for the first string.




Binary-Weighted (or Binary-Scaled) Converters

- An appropriate set of signals that are all related in a binary fashion
The binary array of signals might be voltages, charges, or currents
- Binary-weighted resistor DAC
 - Reduced-resistance-ratio ladders
 - R-2R-based DAC
 - Charge-redistribution switched-capacitor DAC
 - Current-mode DAC

Binary-Weighted Resistor DAC

- 4-bit example

 


$$V_{\text{out}} = -R_F V_{\text{ref}} \left(-\frac{b_1}{2R} - \frac{b_2}{4R} - \frac{b_3}{8R} + \dots \right) = \left(\frac{R_F}{R} V_{\text{ref}} \right) B_{\text{in}}$$

where $B_{\text{in}} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots$

- If it does not be integrated in an IC, it would not require many resistors or switches.
- Disadvantages
 - ◆ Resistor ratio and current ratio are on the order of 2^N . If N is large, this large current ratio requires that the switches also be scaled so that equal voltage drops appear across them.
 - ◆ Monotonicity is not guaranteed
 - ◆ Prone to glitches

Reduced-Resistance-Ratio Ladders

 - Reduce the large resistor ratios in a binary-weighted array
- Introduce a series resistor to scale signals in portions of the array $V_A = -1/4 V_{ref}$




- An additional $4R$ was added such that resistance seen to the right of the $3R$ equals R .
- One-fourth the resistance ratio compared to the binary-weighted case
- Current ratio has remained unchanged
 - ◆ Switches must be scaled in size
- Repeating this procedure recursively, one can obtain an R-2R ladder

R-2R-Based DAC

- Smaller size and better accuracy than a binary-sized approach
 - ◆ Small number of components
 - ◆ Resistance ratio of only 2
- 4-bit example

$$I_r = \frac{V_{\text{ref}}}{2R}$$
 
$$V_{\text{out}} = R_F \sum_{i=1}^N \frac{b_i I_r}{2^{i-1}} = V_{\text{ref}} \left(\frac{R_F}{R} \right) \sum_{i=1}^N \frac{b_i}{2^i}$$




- Current ratio is still large
 - ◆ Large ratio of switch sizes

R-2R-Based DAC (Cont.)

- B_1 is 1 & all other bits are 0
 - ◆ $V_{\text{out}} = (R_F/R)(V_{\text{ref}}/2)$
- B_2 is 1 & all other bits are 0
 - ◆ $V_{\text{out}} = (R_F/R)(V_{\text{ref}}/4)$
- B_{N-1} is 1 & all other bits are 0
 - ◆ $V_{\text{out}} = (R_F/R)(V_{\text{ref}}/2^{N-1})$
- B_N is 1 & all other bits are 0
 - ◆ $V_{\text{out}} = (R_F/R)(V_{\text{ref}}/2^N)$
- Multiplying DAC (ref. p.12-47~12-48)
 - ◆ Use varying analog signal V_a instead of fixed reference voltage V_{ref}

R-2R-Based DAC (Cont.)

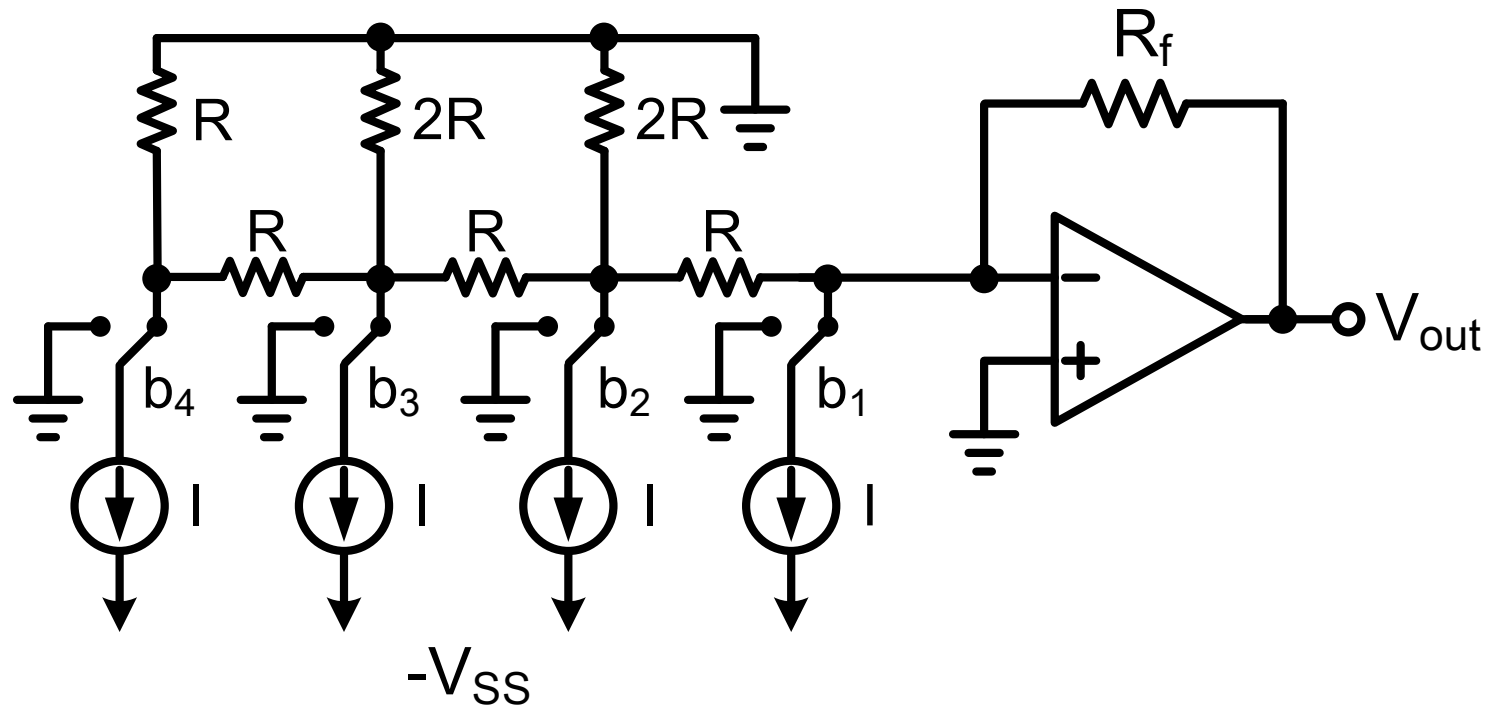- R-2R ladder DAC with equal currents through switches
 - ◆ Slower since the internal nodes exhibit some voltage swings (as opposed to the previous configuration where internal nodes all remain at fixed voltage)




R-2R-Based DAC (Cont.)

- Assume only $b_1 = 1$, the current drawn through R_f is I
- Assume only $b_2 = 1$, the current drawn through R_f is $I/2$
- Assume only $b_3 = 1$, the equivalent circuit to find the current through R_f is:

$$R_X = R + \frac{2}{3}R = \frac{5}{3}R$$

$$I_X = I \times \frac{(2R \parallel 2R)}{(2R \parallel 2R) + \frac{5}{3}R} = \frac{3}{8}I$$
 
$$i_f = \frac{2R}{2R+R} I_X = \frac{1}{4}I$$




- With similar analysis, it can be shown that the current through $b_4 \& R_f$ is $I/8$. Therefore,

$$V_{\text{out}} = 2R_f \times I(2^{-1}b_1 + 2^{-2}b_2 + 2^{-3}b_3 + 2^{-4}b_4)$$


Charge-Redistribution Switched-Capacitor DAC

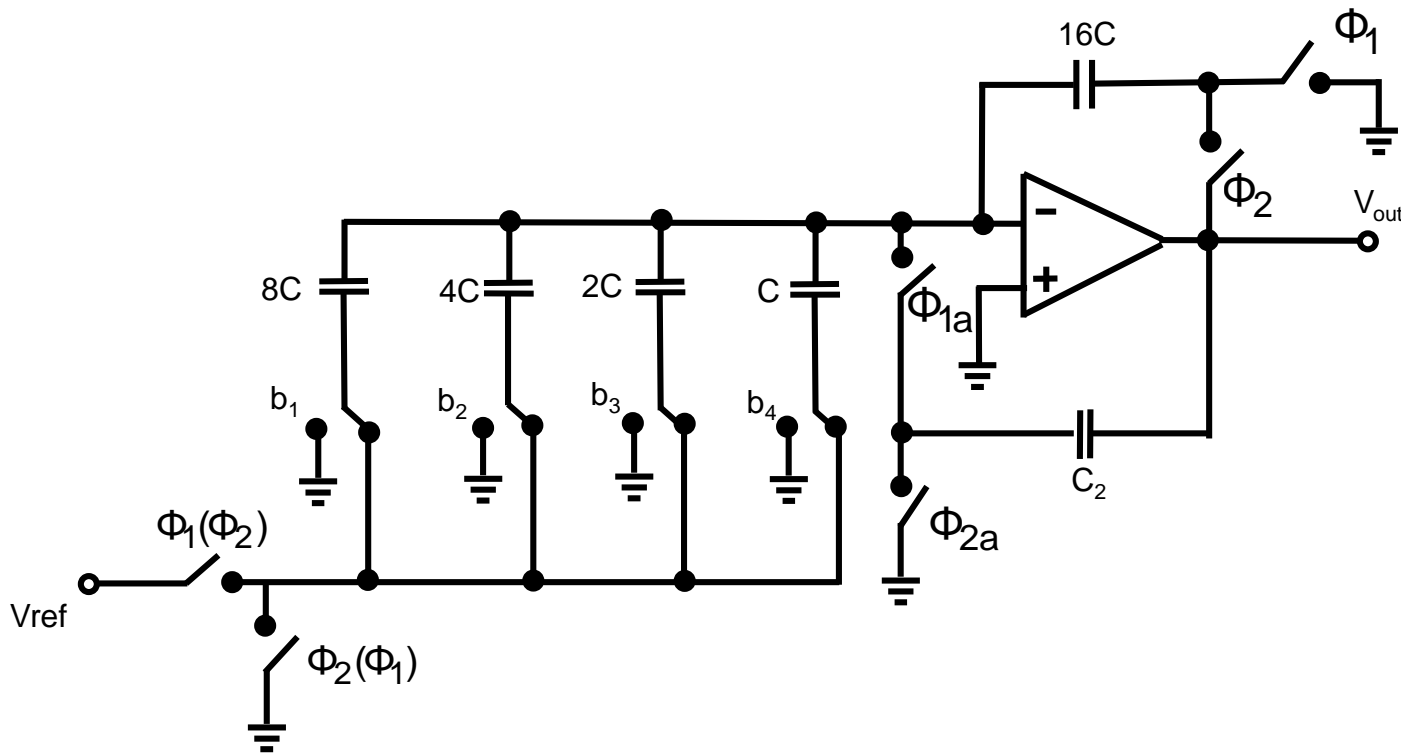- Insensitive to OPAMP input-offset voltage, $1/f$ noise, and finite amplifier gain
- An additional sign bit can be realized by interchanging the clock phases (shown in parentheses)




Current-Mode DAC

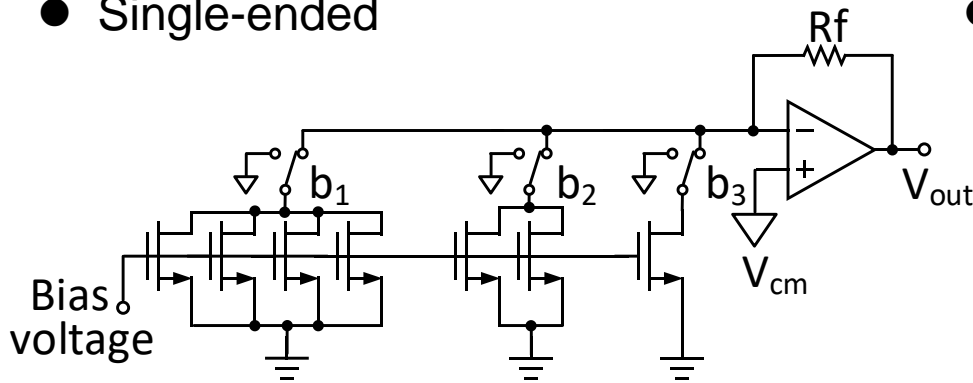
- High-speed
- Switch current to output or to ground
 - The output current is converted to a voltage through R_F
- Upper portion of current source always remains at ground potential (w/ OP)
- Single-ended



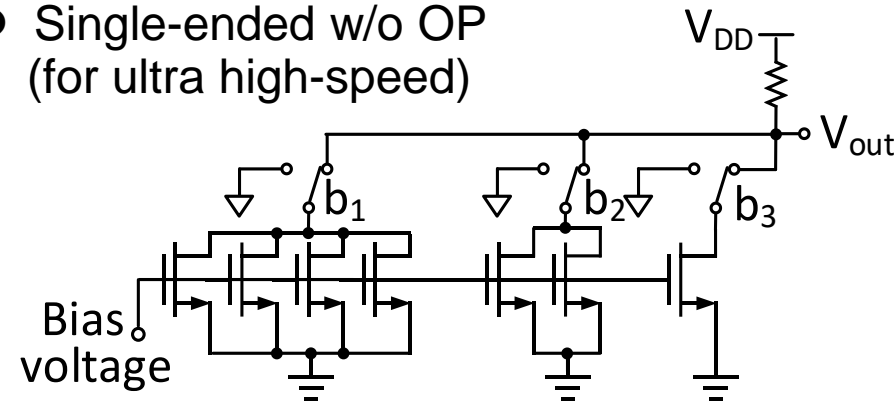
- Single-ended w/o OP (for ultra high-speed)



- Differential


 


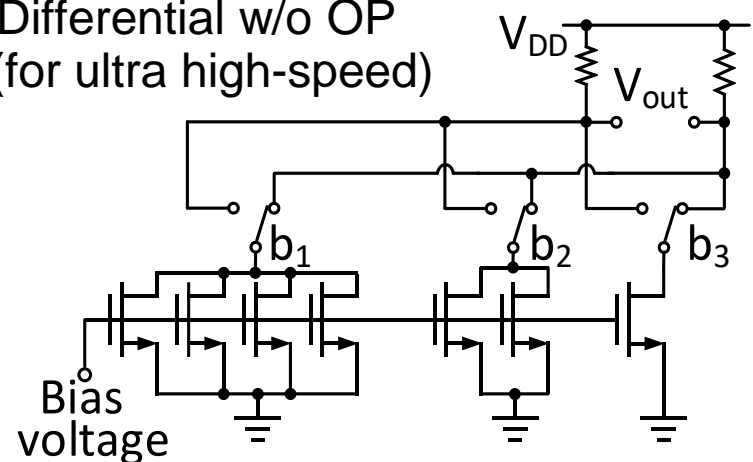- Differential w/o OP (for ultra high-speed)



Glitches

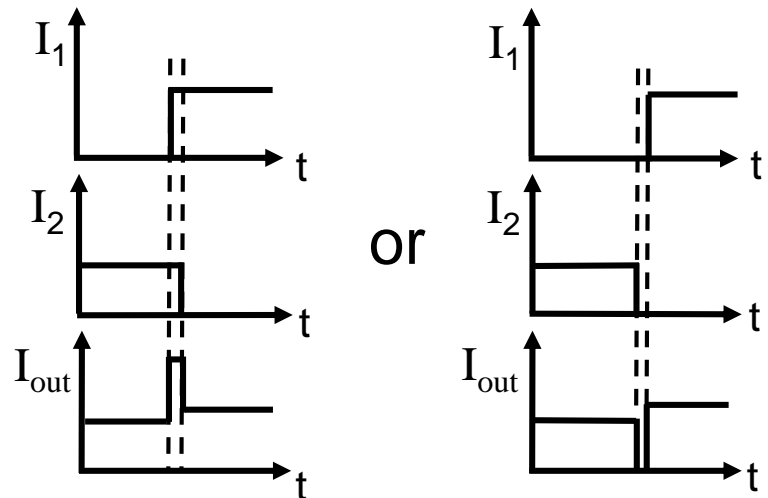 - A major limitation during high-speed operation
- Mainly the result of different delays occurring when switching different signals
- Example: 01111.....1--->10000
 - ◆ I_1 represents the MSB current, and I_2 represents the sum of (N-1) LSB currents.
 - ◆ MSB current turns off slightly early, causing a glitch of zero current



Glitches (Cont.)

- Glitch disturbance can be reduced by
 - ◆ Limiting the bandwidth (placing a capacitor across R_F)
This method slows down the circuit.
 - ◆ Using a sample and hold on the output signal.
 - ◆ Modifying some or all of the digital word from a binary code to a thermometer code. (The most popular method.)

Thermometer-Code DACs

- Digitally recode the input to a thermometer-code equivalent


Thermometer-code representations for 3-bit binary values

Decimal	Binary			Thermometer Code						
	b1	b2	b3	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1
2	0	1	0	0	0	0	0	0	1	1
3	0	1	1	0	0	0	0	1	1	1
4	1	0	0	0	0	0	1	1	1	1
5	1	0	1	0	0	1	1	1	1	1
6	1	1	0	0	1	1	1	1	1	1
7	1	1	1	1	1	1	1	1	1	1

- Advantages over its binary-weighted counterpart
 - ◆ Small DNL errors
 - ◆ Guaranteed monotonicity
 - ◆ Reduced glitching noise
- Does not increase the size of the analog circuitry compared to a binary-weighted approach


Thermometer-Code DACs (Cont.)

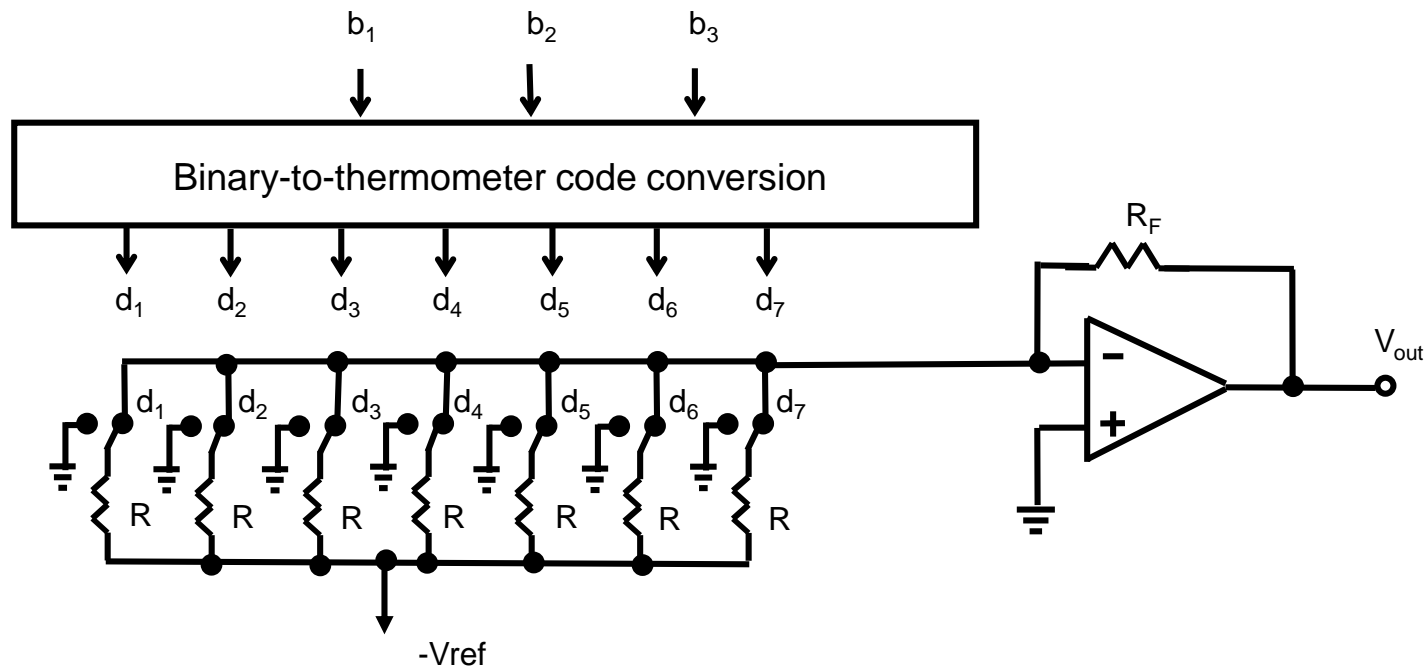- Total area required by the transistor switches is the same (compared to binary-weighted)
 - ◆ All transistor switches are of equal sizes since they all pass equal currents
- Examples
 - ◆ Thermometer-code resistor DAC




Thermometer-Code DACs (Cont.)

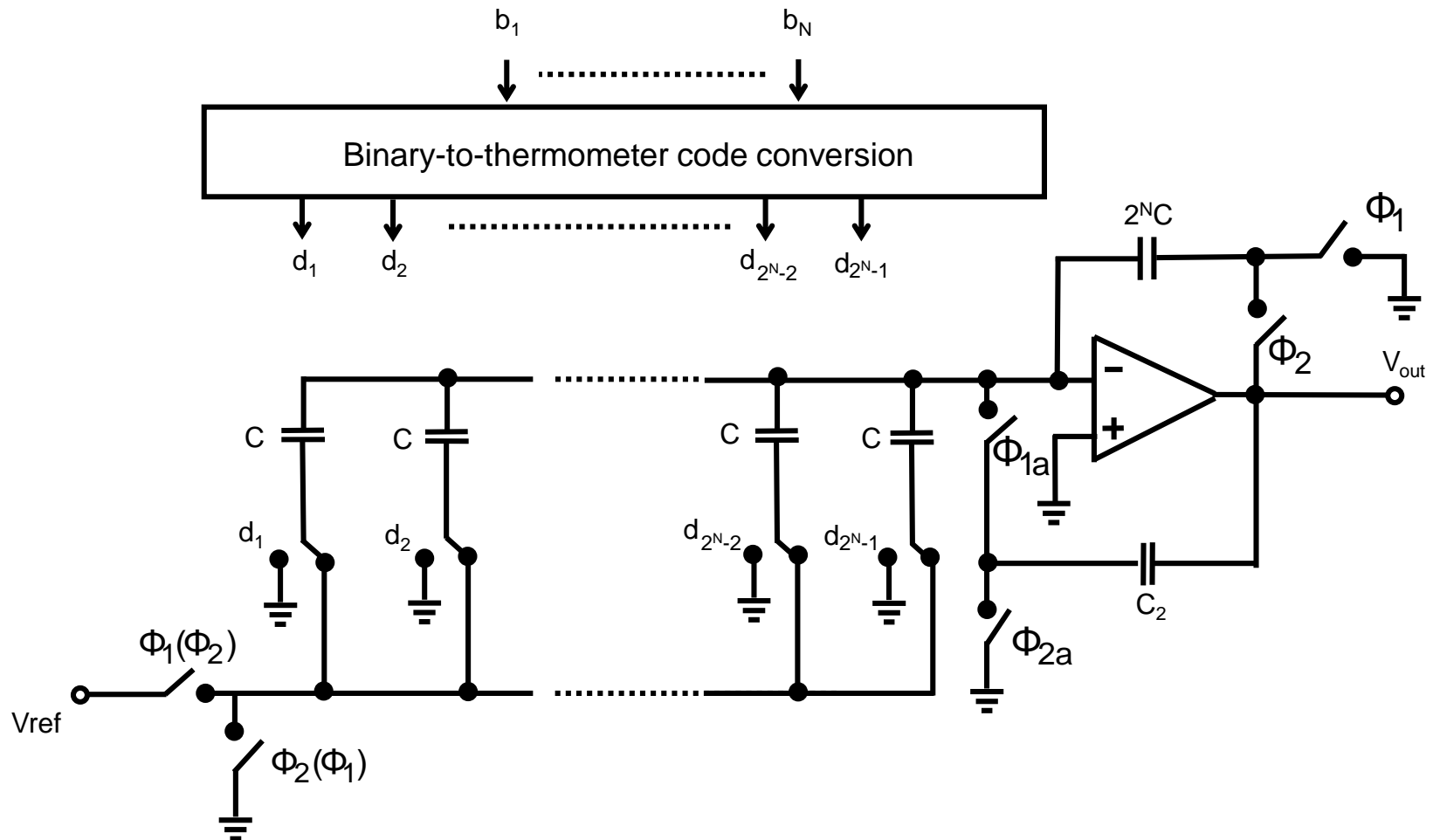- ◆ Thermometer-code charge-redistribution DAC




Thermometer-Code Current-Mode DAC

 - Row and column decoders
- Inherent monotonicity
- Small DNL errors
 - ◆ INL errors depend on the placement of the current sources
- In high-speed applications
 - ◆ The output current feeds directly into an off-chip 50Ω or 75Ω resistor, rather than an output OPAMP.
 - ◆ Cascode current sources are used to reduce current-source variation due to voltage changes in V_{out}



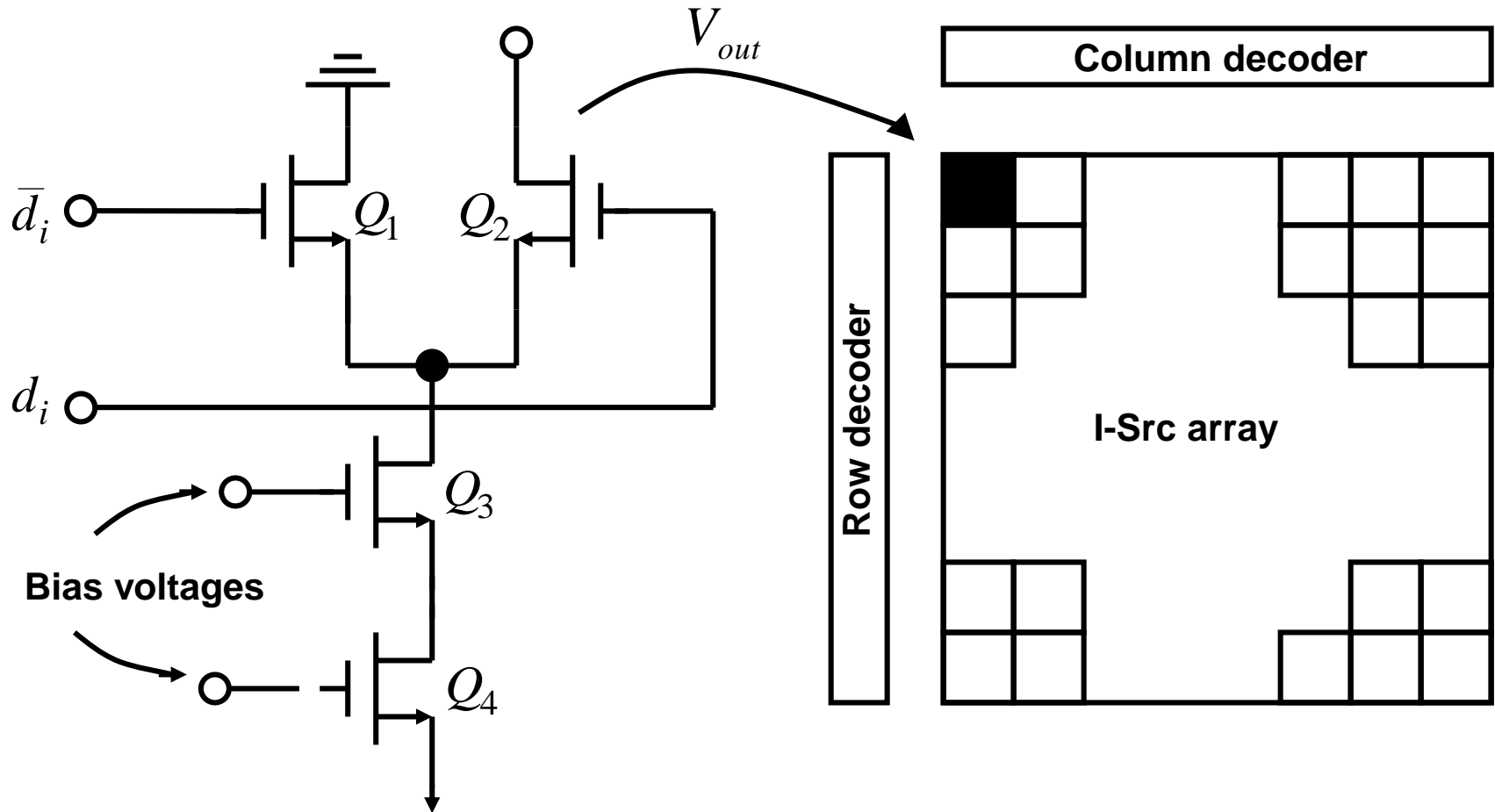Thermometer-Code Current-Mode DAC (Cont.)



[1] T. Miki, "An 80-MHz CMOS D/A converter," IEEE J. Solid-State Circuits, vol. SC-21, no. 6, pp. 983-988, Dec. 1986.


[2] L. Letham, "Larsen, R.E.A high-performance CMOS 70-MHz palette/DAC", IEEE Journal of Solid-State Circuits, Volume 22, Issue 6, pp:1041-1047, Dec 1987.

[3] K. K. Chi et al., "A CMOS triple 100Mbit/s video D/A converter with shift registers and color map," IEEE J. Solid-State Circuits, vol. SC-21, no. 6, pp. 989-995, Dec. 1986

Thermometer-Code Current-Mode DAC (Cont.)

- Precisely timed edges are needed
 - ◆ If both \bar{d}_i and d_i are low simultaneously, the drain of Q_3 is pulled low and the circuit takes longer time to respond.
 - ◆ If both \bar{d}_i and d_i are high simultaneously, V_{out} is shorted to ground.
- To avoid the use of the two logic levels, the gate of Q_2 should be connected to a dc bias voltage

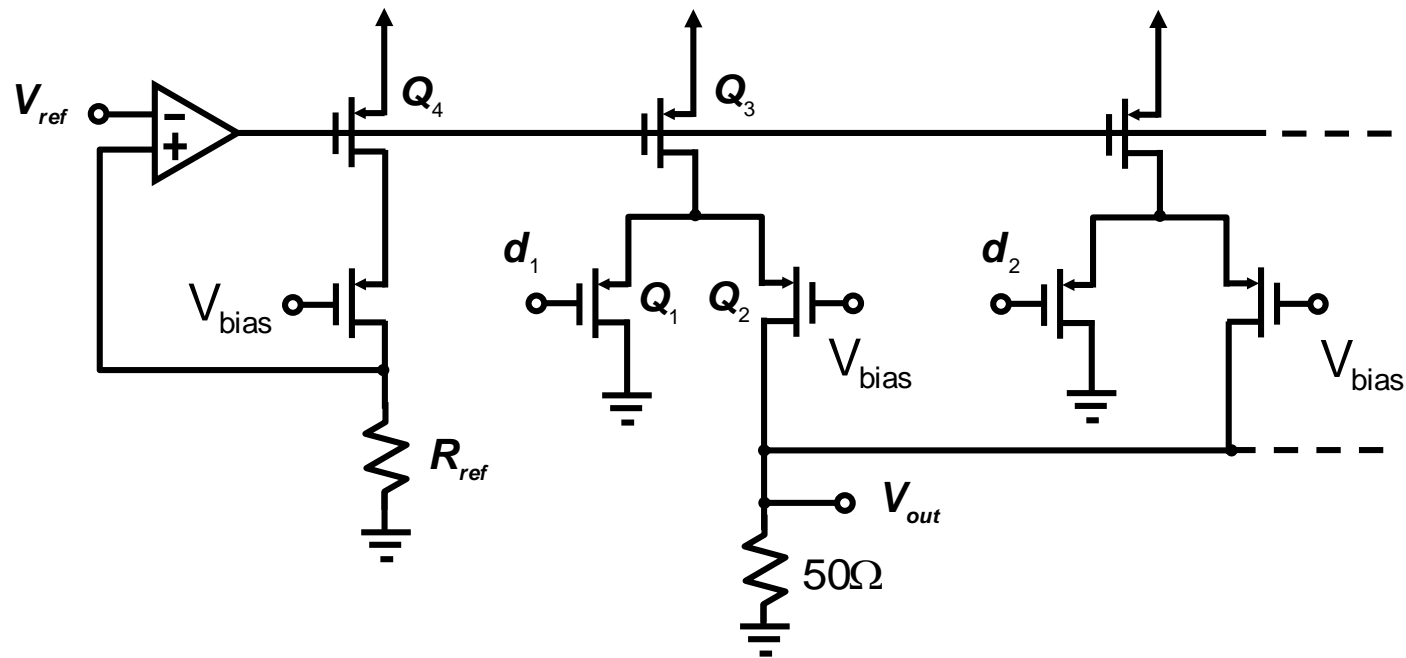
Thermometer-Code Current-Mode DAC (Cont.)




- Can be clocked at the maximum rate without the need for precisely timed edges
- Q_2 and Q_3 effectively form a cascode current source when they drive current to the output.
- To maximize speed, the voltage swing at the common connection (e.g. Q_1 , Q_2 and Q_3) of the current switches should be small.

Dynamically Matched Current Sources

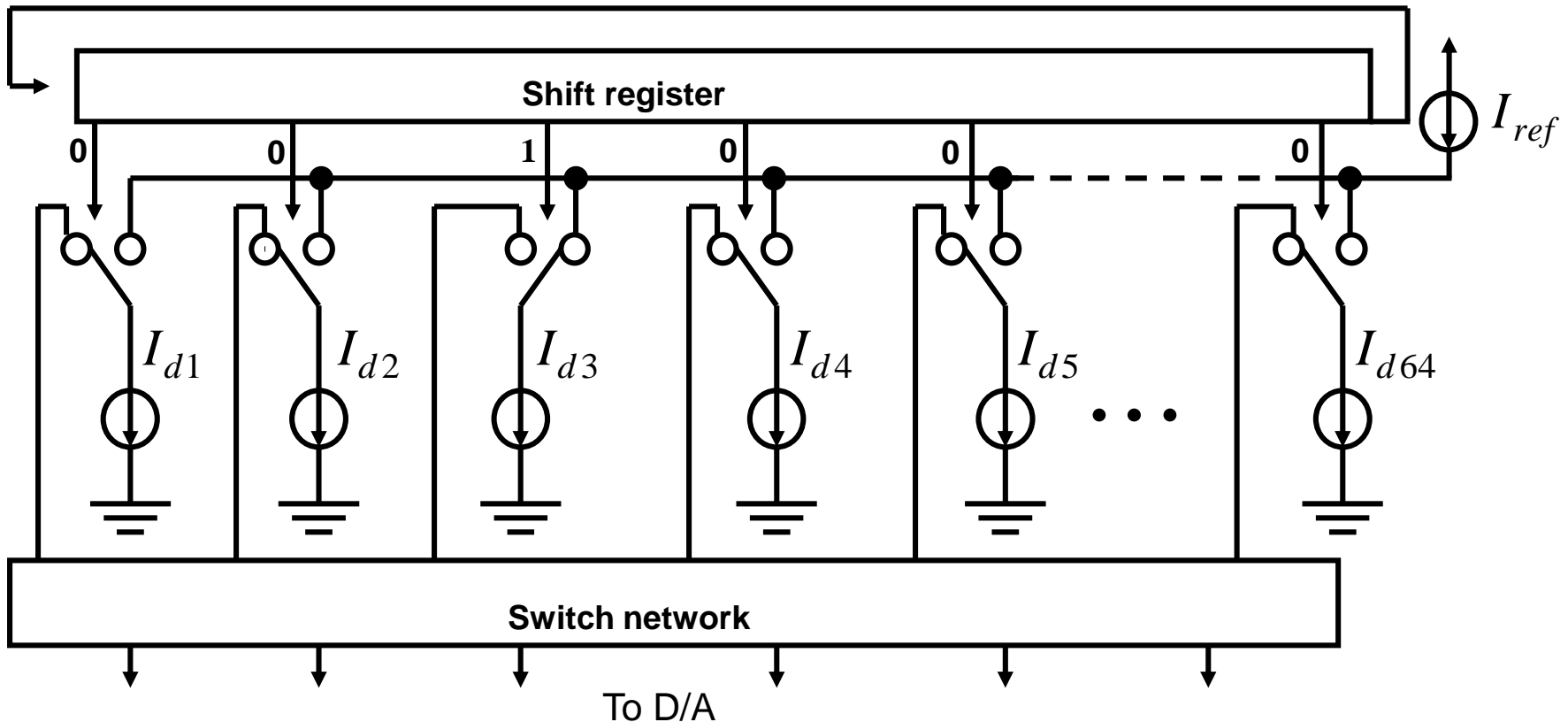- A method for realizing very well-matched current sources (up to 16-bit accuracy) for audio DACs
- Continuously and cyclically calibrate MSB portions
- 16-bit example



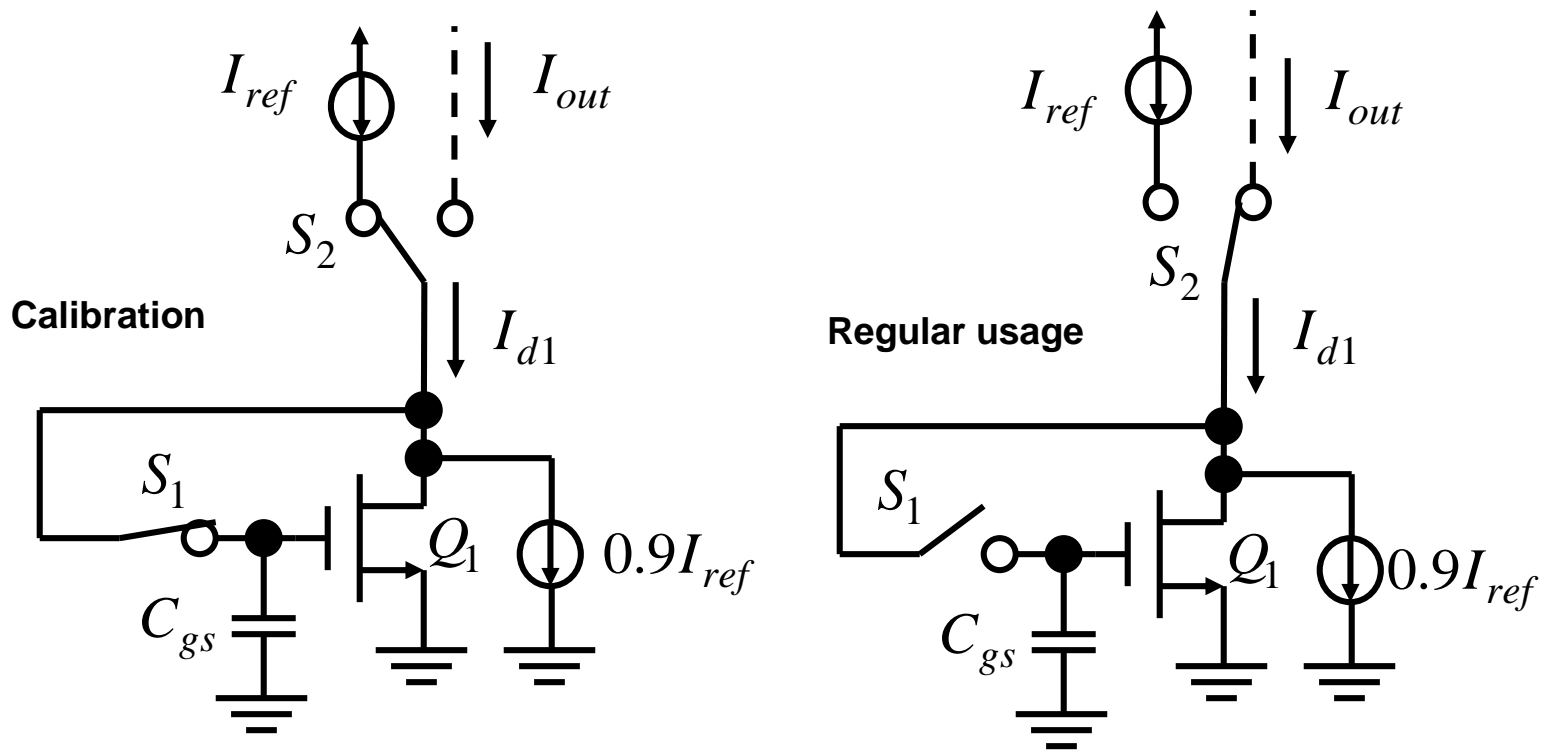Dynamically Matched Current Sources (Cont.)





- 6MSBs were realized using a thermometer code
- Since the accuracy requirements are reduced for the remaining bits, a binary array was used in their implementation.

Dynamically Matched Current Sources (Cont.)

- 64 accurately matched current sources for the 6 MSBs
 - ◆ Current sources are calibrated
 - ◆ Dynamically setting current sources
 - ◆ Even though only 63 are required, the extra one is needed so that DAC can continuously operate when one of them is being calibrated
- Major limitation in matching 64 current sources is due to the differences in clock feedthrough and charge injection switches S_i
 - ◆ The best way is to minimize them
 - Large C_{gs} and large V_{gs} of Q_1
 - Q_1 only source a small current
 - W_{small} / L_{large} can be used for Q_1
- Large C_{gs} to minimize leakage current effect before current sources are recalibrated
- Dummy transistor can be added to S_i
- Other methods to minimize these errors are referred to switched-current (SI) papers


Dynamic Element Matching (DEM)

- Motivation: Repeated selection on the same mismatch elements
→ Accumulated error & Distortion
- DEM Policy: Balancing the selected times of each element
 - ◆ Reduction of repeated pattern → Eliminating distortion
 - ◆ Purely digital circuit for element selection → Scaling friendly
 - ◆ Less power and area consumption than calibration
- Popular DEM algorithms
 - ◆ Data weighted averaging (DWA)
 - ◆ DEM Randomization

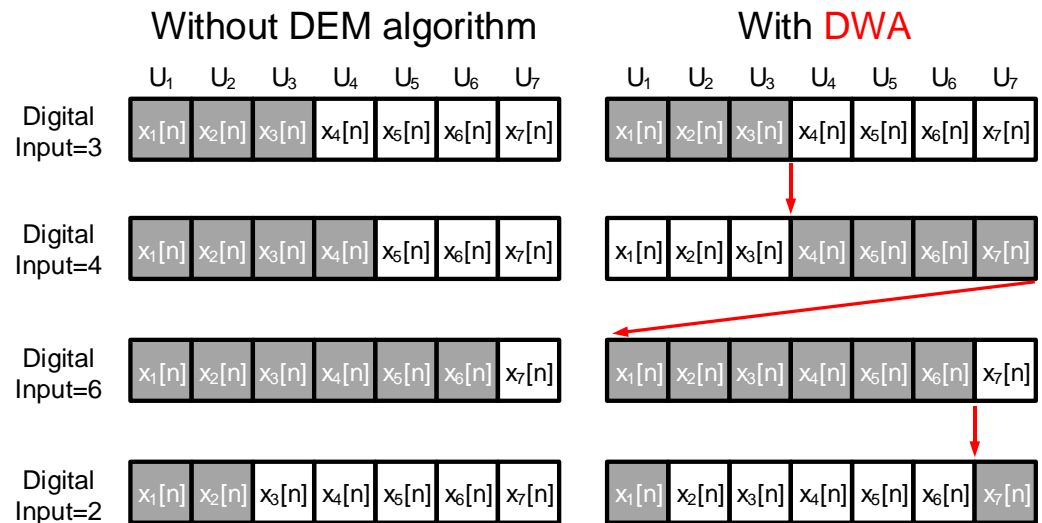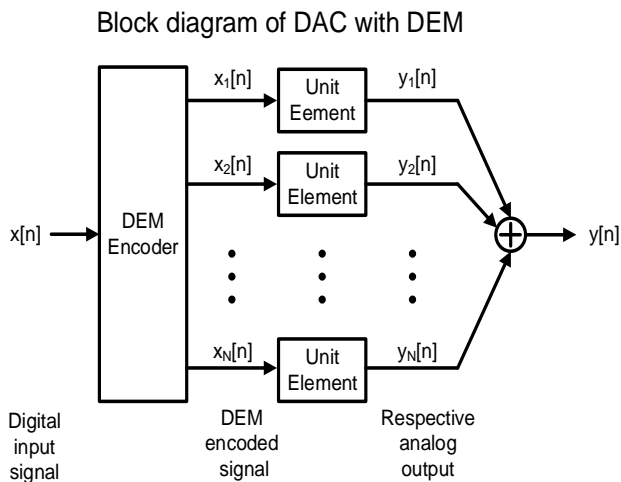

Layout Placement for Gradient Error Compensation

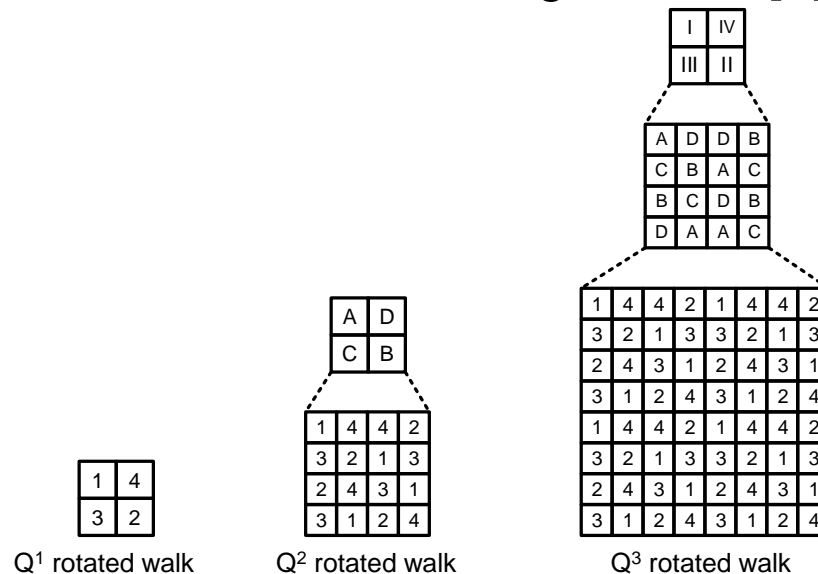- Gradient error → Mismatch between each current cell
- Layout technique to compensate gradient error
 - ◆ Partitioning of single current cell into multiple smaller segments
 - ◆ Balancing of current segments placement → Cancel mismatch
- Can be applied with DEM simultaneously for smaller output errors
- Example of a Q^N rotated walk switching scheme[1]



[1] D. Lee, Y. Lin, and T. Kuo, "Nyquist-rate current-steering digital-to-analog converters with random multiple data-weighted averaging technique and Q^N rotated walk switching scheme," *IEEE Trans. Circuits Syst. II, Exp. Briefs*, vol. 53, no. 11, pp. 1264–1268, Nov. 2006.

Hybrid Converters

- Combine the advantages of different approaches
- It's quite common to use a thermometer-code approach for the top few MSBs while using a binary-scaled technique for the lower LSBs
 - ◆ Glitching is significantly reduced and accuracy is high
 - ◆ Circuit area is saved with a binary-scaled approach for LSBs
- Examples
 - ◆ Resistor-capacitor hybrid DAC (Refer to p.12-19)
 - ◆ Segmented DAC (Refer to textbook p.640)

1. The DAC is segmented into the 2 most significant bits (MSBs), 2 upper least significant bits (ULSBs) and 2 least significant bits (LSBs)
2. The current weighting of the segments are $I_{MSB}=16I_{LSB}$ and $I_{ULSB}=4I_{LSB}$

