

Component Matching Issues

Component Matching Issues

- Effective component sizes differ from mask sizes

- Examples




- ◆ Lateral diffusion due to

- Ion implantation
- Annealing

- ◆ Overetching


- ◆ Narrow channel effect

   - High doping density at the sides of transistors
 - Due to channel stop implantation
- Decrease channel charge density at edges
- Decrease effective channel width




Component Matching Issues (Cont.)

- Absolute component sizes can seldom be accurately determined. The inaccuracies also affect the ratio of sizes (with a lesser degree) when the ratio is not unity.
- Matching second-order size error effects is done mainly by making larger objects out of several unit-sized components connected together. Also, for best ratio accuracy, the boundary conditions around all objects should be matched, even when this means adding extra unused components. (Examples given later)
- Mismatch profile
 - ◆ Random mismatch
 - ◆ Gradient mismatch

 

Component Matching Issues (Cont.)

 
- Random mismatch: Larger capacitance area \rightarrow Smaller mismatch (%)



- Gradient mismatch: Larger capacitance spacing \rightarrow Larger mismatch (%)


1st order

Gradient mismatch model

 


2nd order

Gradient mismatch model

 



1st + 2nd order

Gradient mismatch model

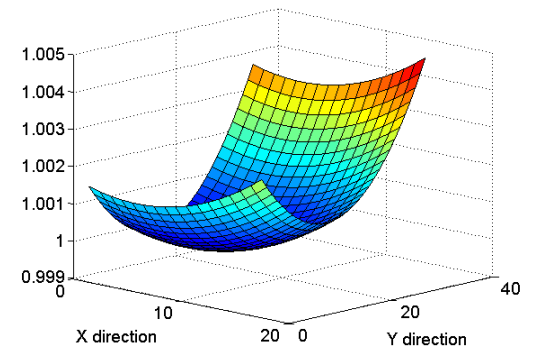

Transistor Layouts

  
- Common-centroid layout for better matching accuracy
- Example: A differential source-coupled pair



- ◆ The layout for M_1 and M_2 is symmetric in both the X and Y axes, and any gradients would affect both M_1 and M_2 in the same way
- ◆ This layout technique greatly minimize nonidealities such as OPAMP input-offset voltage errors when using a differential pair (M_1/M_2 , M_3/M_4) in the input stage of an OPAMP


Capacitor Matching

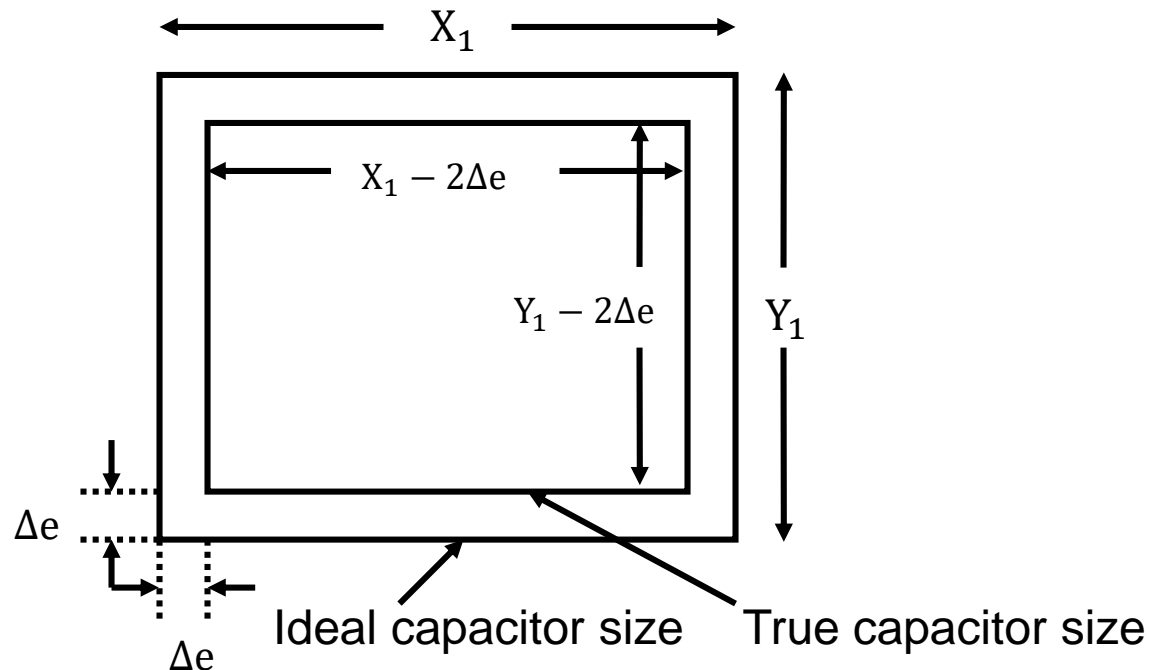- Two major sources of match errors are due to
 - ◆ Oxide-thickness gradient
 - Common-centroid layout can be used to minimize this error
 - ◆ Over-etching
 - Capacitor area is smaller than mask area




Capacitor Matching (Cont.)

 - Error can be minimized
 - ◆ Use unit-sized capacitor
 - ◆ Perimeter-to-area ratios are kept the same, even where the capacitors are different sizes (Refer to p.104~106 of textbook).
e.g. A capacitor layout with equal perimeter-to-area ratios of 4 units and 2.314units




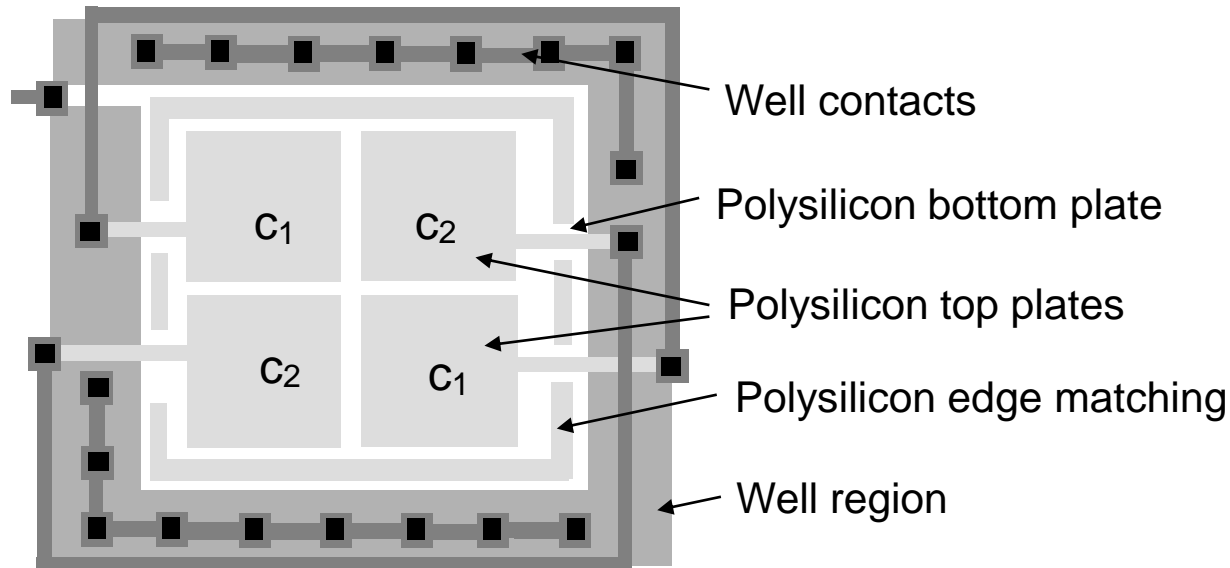- To minimize 2nd-order effect (Refer to p.106~107 of textbook)




Resistor Matching

 - The structure below might result in about 0.1% matching accuracy of identical resistors if the finger widths are relatively wide (say, 3 μm in a 28nm technology)




Noise Considerations in Analog Layout

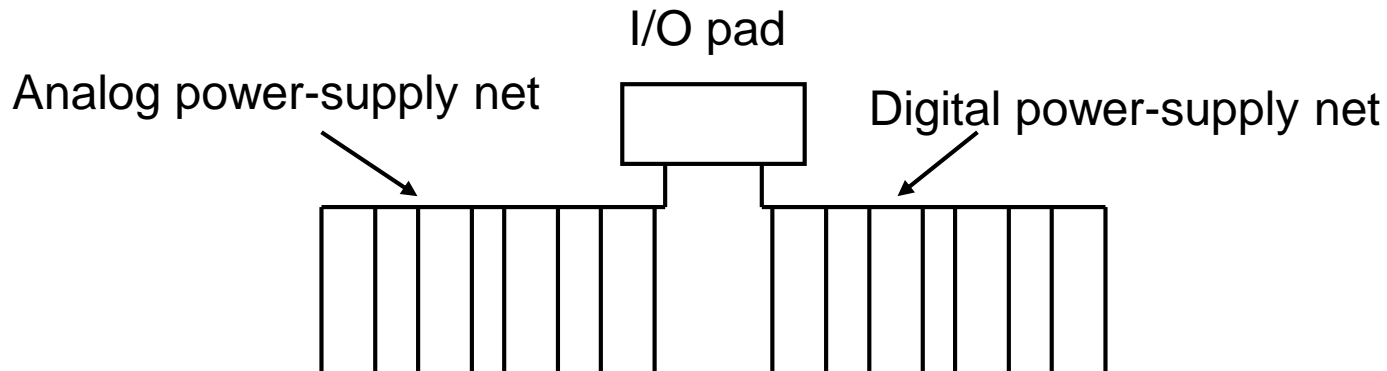- Minimize noise in analog circuits
 - ◆ Minimize noise from digital circuits coupling into substrate or analog power supplies
 - ◆ Minimize substrate noise that affects analog circuits
- Example of noise reduction technique (Refer to p.109~112 of textbook)
 - ◆ Use separate nets for analog and digital power supplies




Noise Considerations in Analog Layout (Cont.)

 - Examples of noise reduction technique (Cont.)
 - ◆ Separating analog and digital areas with guard rings and wells in an attempt to minimize the injection of noise from digital circuits into the substrate under the analog circuit.




 - ◆ Using shields helps keep noise from being capacitively coupled into and out of the substrate.



Noise Considerations in Analog Layout (Cont.)

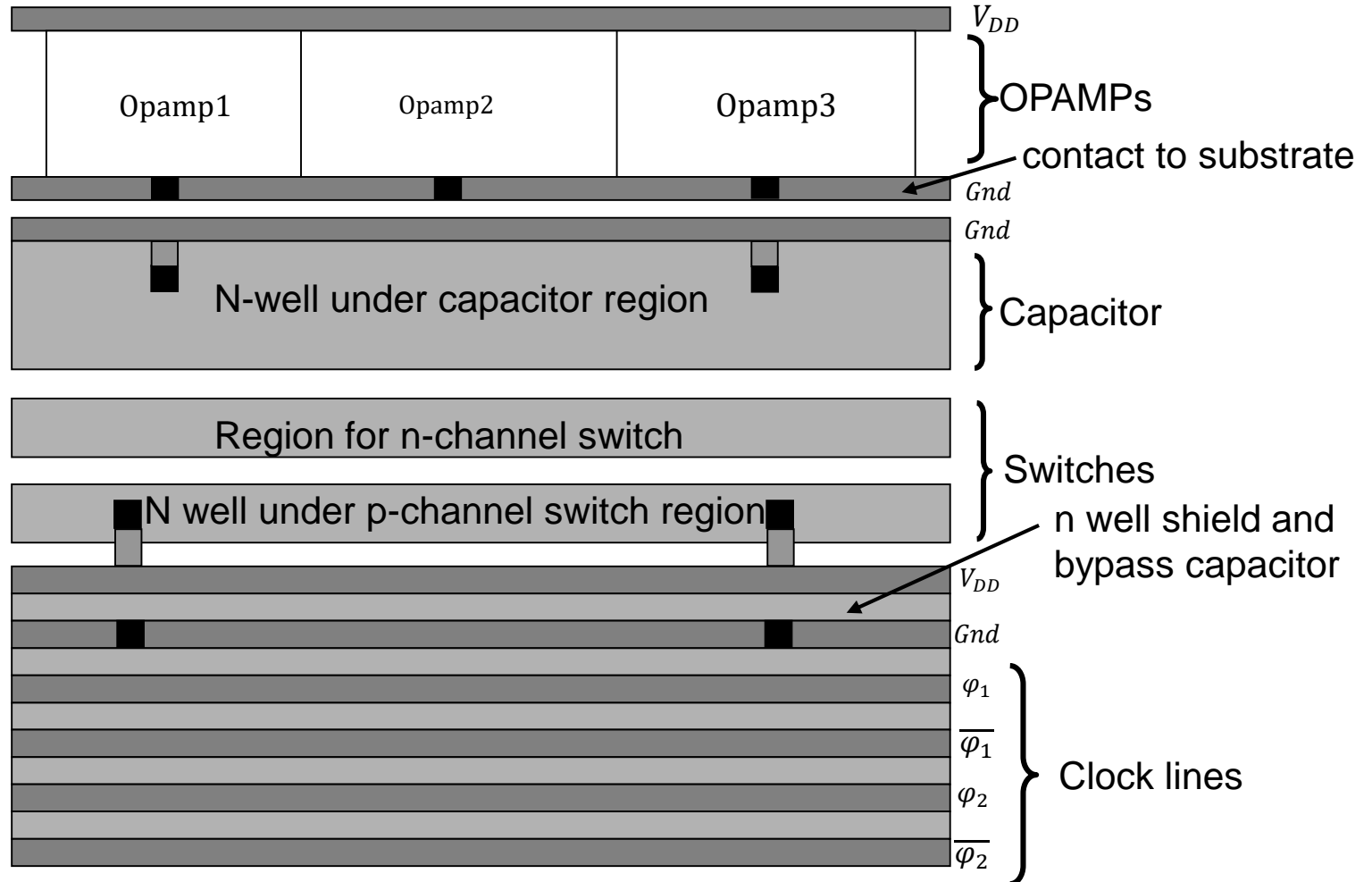- ◆ Any unused space should be filled with additional contacts to both the substrate and to the wells, which are used as bypass capacitors.
- A possible floorplan for an analog section containing switched-capacitor circuits.



Mismatch Effects in MOSFET Current Mirrors

- Mismatch between M1 and M2: W/L ratio & Threshold voltage
- Mathematical expression

- ◆ Drain currents of M1 and M2

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{t1})^2, I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS} - V_{t2})^2$$

- ◆ Define average and mismatch quantities

$$I_D = \frac{I_{D1} + I_{D2}}{2}, \Delta I_D = I_{D1} - I_{D2} \quad V_t = \frac{V_{t1} + V_{t2}}{2}, \Delta V_t = V_{t1} - V_{t2}$$

$$\frac{W}{L} = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right], \Delta \frac{W}{L} = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$$


- ◆ Substitute these expressions into I_{D1} , I_{D2} (Neglect high-order terms)

$$\frac{\Delta I_D}{I_D} = \frac{\frac{1}{2} \mu_n C_{ox} \left[\left(\frac{W}{L} + \frac{1}{2} \Delta \frac{W}{L}\right) (V_{GS} - V_t - \frac{1}{2} \Delta V_t)^2 - \left(\frac{W}{L} - \frac{1}{2} \Delta \frac{W}{L}\right) (V_{GS} - V_t + \frac{1}{2} \Delta V_t)^2 \right]}{\frac{1}{2} \times \frac{1}{2} \mu_n C_{ox} \left[\left(\frac{W}{L} + \frac{1}{2} \Delta \frac{W}{L}\right) (V_{GS} - V_t - \frac{1}{2} \Delta V_t)^2 + \left(\frac{W}{L} - \frac{1}{2} \Delta \frac{W}{L}\right) (V_{GS} - V_t + \frac{1}{2} \Delta V_t)^2 \right]} \cong \frac{\Delta \frac{W}{L}}{\frac{W}{L}} - \frac{2}{(V_{GS} - V_t)} \Delta V_t$$

- Two mismatch components

- Geometry dependent mismatch & Threshold voltage mismatch

 
- I_D mismatch increases as $(V_{GS} - V_t)$ is reduced



Mismatch Effects in BJT Current Mirrors

$$\frac{\Delta I_C}{I_C} = \left(\frac{1}{1 + \frac{g_m R}{\alpha_F}} \right) \frac{\Delta I_S}{I_S} + \frac{\frac{g_m R}{\alpha_F}}{1 + \frac{g_m R}{\alpha_F}} \left(-\frac{\Delta R}{R} + \frac{\Delta \alpha_F}{\alpha_F} \right)$$

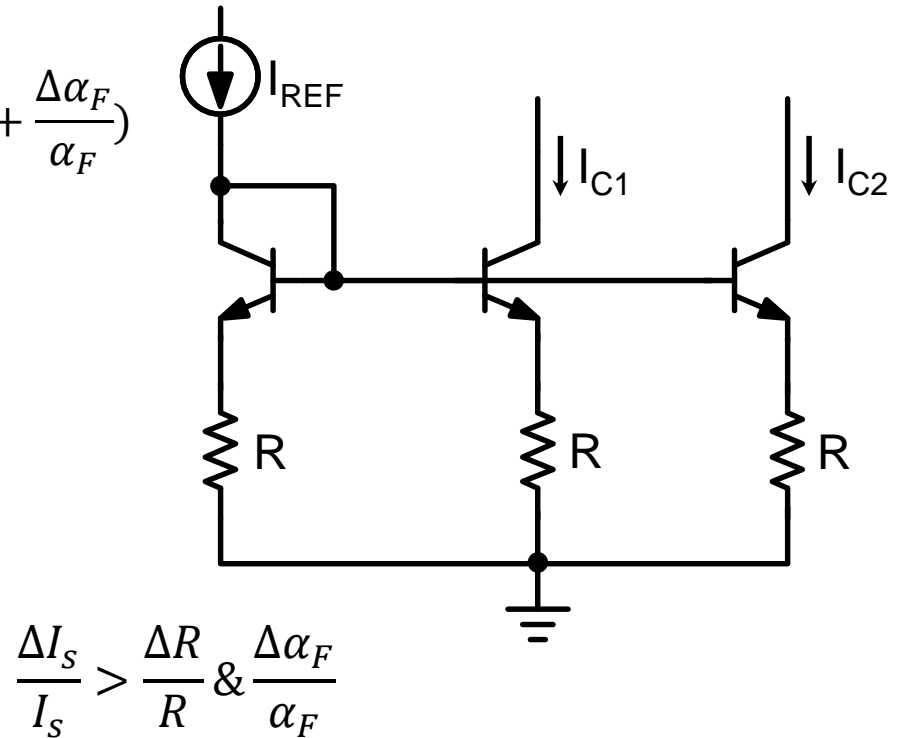- $g_m R \gg 1 \Rightarrow$ 2nd term dominates
- $g_m R \ll 1 \Rightarrow$ 1st term dominates
- $g_m R \gg 1$ is preferred because



Input Offset Voltage of Source-Coupled MOS Pair

- V_{OS} : Differential voltage \rightarrow Make differential output voltage exactly zero
- Define difference and average quantities

$$I_D = \frac{I_{D1} + I_{D2}}{2}, \Delta I_D = I_{D1} - I_{D2}$$

$$R_L = \frac{R_{L1} + R_{L2}}{2}, \Delta R_L = R_{L1} - R_{L2}$$

$$V_t = \frac{V_{t1} + V_{t2}}{2}, \Delta V_t = V_{t1} - V_{t2}$$

$$\frac{W}{L} = \frac{1}{2} \left[\left(\frac{W}{L} \right)_1 + \left(\frac{W}{L} \right)_2 \right], \Delta \frac{W}{L} = \left(\frac{W}{L} \right)_1 - \left(\frac{W}{L} \right)_2$$

- Let $I_{D1}R_{L1} = I_{D2}R_{L2} \rightarrow \frac{\Delta I_D}{I_D} = \frac{-\Delta R_L}{R_L}$

$$V_{OS} = V_{GS1} - V_{GS2} = (V_{t1} + V_{ov1}) - (V_{t2} + V_{ov2})$$

$$= \Delta V_t + \sqrt{\frac{2}{\mu_n C_{ox}}} \left(\sqrt{\left(\frac{I_D + \frac{1}{2}\Delta I_D}{\frac{W}{L} + \frac{1}{2}\Delta \frac{W}{L}} \right)} - \sqrt{\left(\frac{I_D - \frac{1}{2}\Delta I_D}{\frac{W}{L} - \frac{1}{2}\Delta \frac{W}{L}} \right)} \right)$$


$$\cong \Delta V_t + \frac{(V_{GS} - V_t)}{2} \left[\left(\frac{-\Delta R_L}{R_L} \right) - \left(\frac{\Delta(W/L)}{(W/L)} \right) \right] \quad (\text{Neglect higher order terms})$$

◆ Mismatch components

➢ Threshold voltage mismatch

➢ Geometry dependent mismatch \rightarrow Increase as $(V_{GS} - V_t)$ is increased

 - For same level of geometric mismatch or process gradient: $V_{OS}(\text{MOSFET}) > V_{OS}(\text{BJT})$




Input Offset Voltage of Emitter-Couple BJT Pair

- Offset voltage with resistor load



$$V_{os} \approx V_T \left(-\frac{\Delta R_C}{R_C} - \frac{\Delta I_S}{I_S} \right); \quad \frac{dV_{os}}{dT} = \frac{V_{os}}{T}$$

- Offset current with resistor load
 
$$I_{os} \approx -\frac{I_C}{\beta_F} \frac{\Delta R_C}{R_C} - \frac{I_C}{\beta_F} \frac{\Delta \beta_F}{\beta_F}$$



Common-Centroid Layout of BJT Pair

  

Input Offset Voltage of MOS OPAMP

- Assume that the matching is perfect with inputs grounded

$$V_{OUT} = V_{DD} - |V_{GS3}| \dots (1)$$

- Differential input required to drive the output to the value given by (1) is the input-referred offset voltage. With device mismatch, offset is usually nonzero.

$$V_{ID} = V_{GS1} - V_{GS2} = V_{t1} + V_{ov1} - V_{t2} - V_{ov2} \dots (2)$$

- Assume that λ of M_1 & M_2 are identical ($V_{DS1} = V_{DS2} = V_{DSN}$ when $V_{ID} = V_{OS}$)

$$V_{OS} = V_{t1} - V_{t2} + \sqrt{\frac{1}{1+\lambda_N V_{DSN}}} \left(\sqrt{\frac{2I_1}{k'(W/L)_1}} - \sqrt{\frac{2I_2}{k'(W/L)_2}} \right) \dots (3)$$

- Assume that the mismatches are small

$$V_{OS} \approx V_{t1} - V_{t2} + \frac{V_{ovN}}{2} \left(\frac{\Delta I_N}{I_N} - \frac{\Delta(W/L)_N}{(W/L)_N} \right) \dots (4)$$

where


$$V_{ovN} = \sqrt{\frac{2I_N}{k'(W/L)_N(1+\lambda_N V_{DSN})}} \dots (5)$$

$$\Delta I_N = I_1 - I_2 \dots (6)$$

$$I_N = \frac{I_1 + I_2}{2} \dots (7)$$

$$\Delta(W/L)_N = (W/L)_1 - (W/L)_2 \dots (8)$$
 
$$(W/L)_N = \frac{(W/L)_1 + (W/L)_2}{2} \dots (9)$$



Input Offset Voltage of MOS OPAMP (Cont.)

- Since $I_1 = -I_3$ & $I_2 = -I_4$, where

$$\frac{\Delta I_N}{I_N} = \frac{\Delta I_P}{I_P} \dots (10) \quad \Delta I_P = I_3 - I_4 \dots (11) \quad I_P = \frac{I_3 + I_4}{2} \dots (12)$$


- Use KVL in the gate-source loop in the load to find $\Delta I_p/I_p$

$$0 = V_{GS3} - V_{GS4} = V_{t3} + V_{OV3} - V_{t4} - V_{OV4} \dots (13)$$

- Since M3 and M4 are p-channel transistors, their overdrives are negative. Assume that the Early voltages of M3 and M4 are identical. Since $V_{DS3} = V_{DS4} = V_{DSP}$ when $V_{ID} = V_{OS}$, (13) can be rewritten as

$$0 = V_{t3} - V_{t4} - \sqrt{\frac{1}{1 + |\lambda_P V_{DSP}|}} \left(\sqrt{\frac{2|I_3|}{k'(W/L)_3}} - \sqrt{\frac{2|I_4|}{k'(W/L)_4}} \right) \dots (14)$$

 - In (14), absolute value functions have been used
 - ◆ The arguments of the square-root functions are positive



Input Offset Voltage of MOS OPAMP (Cont.)

- If the mismatches are small, (14) can be approximated as

$$\frac{\Delta I_P}{I_P} \approx \frac{V_{t3} - V_{t4}}{|V_{OV P}|/2} + \frac{\Delta(W/L)_P}{(W/L)_P} \dots (15)$$


where $|V_{OV P}| = \sqrt{\frac{2|I_P|}{k'(W/L)_P(1+|\lambda_P V_{DS P}|)}} \dots (16)$

$$\Delta(W/L)_P = (W/L)_3 - (W/L)_4 \dots (17)$$

$$(W/L)_P = \frac{(W/L)_3 + (W/L)_4}{2} \dots (18)$$

- Substitute (15) and (10) into (4) gives

$$V_{OS} \approx V_{t1} - V_{t2} + \frac{V_{OV N}}{2} \left(\frac{V_{t3} - V_{t4}}{\frac{|V_{OV P}|}{2}} + \frac{\Delta(W/L)_P}{(W/L)_P} - \frac{\Delta(W/L)_N}{(W/L)_N} \right) \dots (19)$$

 

Parameter Relevant for Transistor Performance

- T-like 0.18 μm process

Parameter	Symbol	Typical value	Absolute accuracy	Matching accuracy
Threshold	V_{th}	0.45 V	$\pm 0.15 V$	5 mV
Gamma	γ	0.3 ~ 0.6	-	-
Mobility (n)	μ_n	$250\text{cm}^2/\text{Vsec}$	$\pm 10\%$	-
Mobility (p)	μ_p	$80\text{cm}^2/\text{Vsec}$	$\pm 15\%$	-
Oxide capacitance	C_{ox}	$9\text{fF}/\mu\text{m}^2$	-	-
Length	L	-	$0.015 \mu\text{m}$	-
Width	W	-	$0.02 \mu\text{m}$	-

Parameter Relevant for Capacitor Performance

- T-like 0.18 μm process

Parameter	Symbol	Typical value	Absolute accuracy	Matching accuracy
Dielectric	$\epsilon_{R(SiO_2)}$	3.9	-	-
Oxide thickness	t_{ox}	4.2 ± 0.2 nm	$\pm 5\%$	-
Poly-oxide thick	$t_{p,ox}$	25 nm	-	-
MIM capacitor	C_{unit}	$6.1 \text{ fF}/\mu\text{m}^2$	-	0.4% on p-well 0.07% on n-well
VCC(PIP)	VCC	< 150 ppm	-	-
TCC(PIP)	TCC	< 50 ppm	-	-

Parameter Relevant for Resistor Performance

- T-like 0.18 μm process

Parameter	Symbol	Typical value	Absolute accuracy	Matching accuracy
Diff. resistivity	ρ_{diff}	200 Ω/sq	25 %	2 %
Poly resistivity	ρ_{poly}	150 Ω/sq	20 %	4 %
Diff. thickness	$x_{j,diff}$	80 nm	15 %	0.5 %
Poly thickness	$x_{j,poly}$	80~100 nm	15 %	1 %