

Electronics (3) Homework3

1. Fig.1 shows a filter, where $R_1=2\text{M}\Omega$, $R_2=2\text{M}\Omega$, $C_1=1\text{nF}$, $C_2=10\text{pF}$, $C_L=2\text{pF}$. Assume that the OP_1 has an infinite DC gain and an infinite bandwidth, please


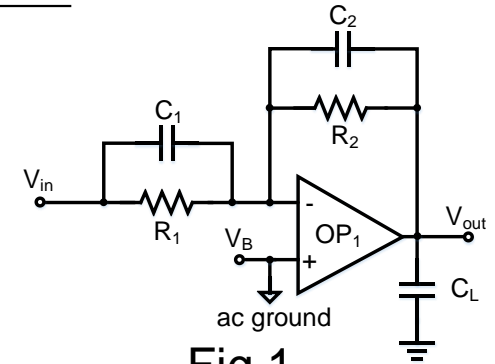


Fig.1

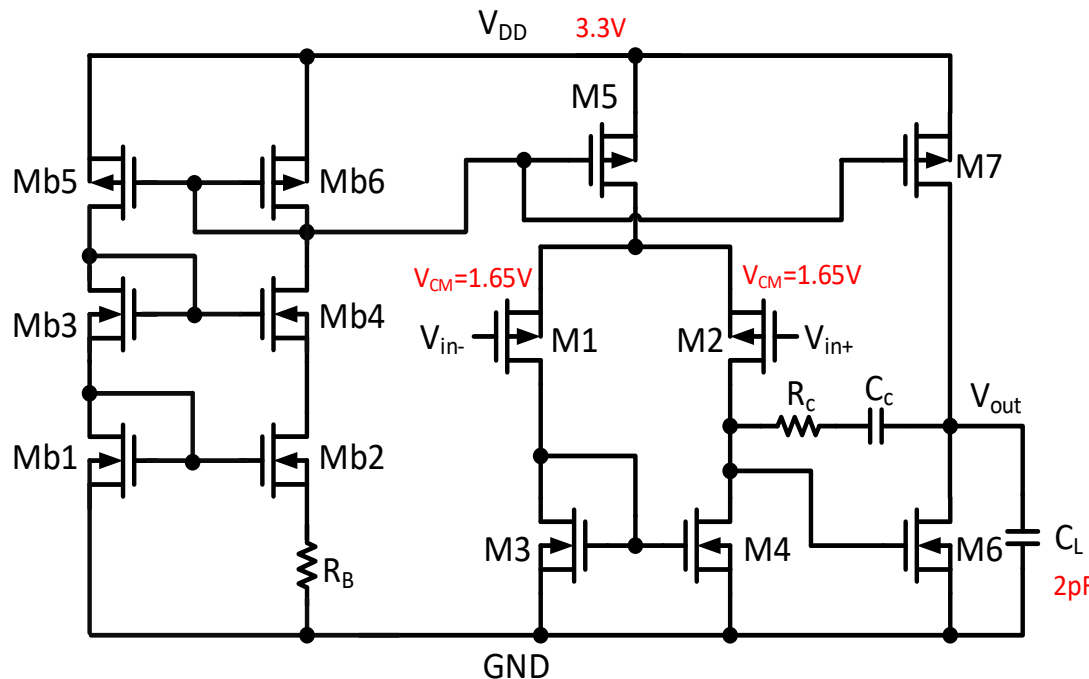2. In Fig.1, assume that $V_{DD}=3.3\text{V}$, V_B is biased at 1.65V , and the common-mode voltage of V_{in} is $V_{CM}=1.65\text{V}$. Please replace the OP_1 with the transistor-level circuit of the two-stage op amp designed by yourself in HW2.
 - (a) List the DC gain (A_0), unity-gain bandwidth (f_t), phase margin (PM), and slew rates (SR^+ and SR^-) of the op amp you used.
 - (b) Draw the magnitude/phase Bode plots of the filter by PSpice AC-sweep simulation.
 - (c) Discuss the difference of the plots in 1(b) and 2(b).
3. To verify 2(b), assume that $V_{in}(t) = V_{CM} + V_P \times \sin(2\pi f_{in} t)$, where $V_{CM}=1.65\text{V}$.
 - (a) Let $V_P=0.01\text{V}$, please use PSpice time-domain simulation to measure the swing of $V_{out}(t)$ when $f_{in}=10\text{Hz}$, 1KHz , 100KHz and 100MHz , respectively. Check if the results match the magnitude Bode plots in 2(b).
 - (b) If V_P is changed to 0.02V , repeat 3(a) and discuss the difference.

Notes

- When verifying the filter circuit by PSpice, you **MUST** use an op amp which meets **ALL** specifications listed in HW2.
- If your original op amp in HW2 doesn't meet **ALL** of the specifications, you can re-design a two-stage op amp. Or, you can use the following op amp to finish HW3.



$$\begin{aligned} \left(\frac{W}{L}\right)_{M1,2} &= \frac{5.5\mu m}{0.5\mu m}, \quad \left(\frac{W}{L}\right)_{M3,4} = \frac{1.4\mu m}{0.5\mu m}, \\ \left(\frac{W}{L}\right)_{M5} &= \frac{11\mu m}{0.5\mu m}, \quad \left(\frac{W}{L}\right)_{M6} = \frac{27\mu m}{0.5\mu m}, \\ \left(\frac{W}{L}\right)_{M7} &= \frac{105\mu m}{0.5\mu m}, \quad \left(\frac{W}{L}\right)_{Mb1,3\sim6} = \frac{1.25\mu m}{0.5\mu m}, \\ \left(\frac{W}{L}\right)_{Mb2} &= \frac{5\mu m}{0.5\mu m}, \quad R_B = 18k\Omega, \\ C_C &= 0.15pF, \quad R_C = 685\Omega. \end{aligned}$$

- Finishing HW3 with an op amp designed by yourself will get a better grade.

Notes (Cont.)

- Hints
 - ◆ According to page 38 of ch13's lecture slides, non-idealities of OP₁ might affect the frequency response of the filter.
 - ◆ Maximum slope of a signal $V_P \times \sin(2\pi f_{in} t)$ is $2\pi f_{in} \times V_P$.
- Your report should include
 - ◆ Hand-calculation progress
 - Derivation procedure in 1(a)
 - Brief drawing of magnitude/phase Bode plots in 1(b)
 - ◆ PSpice circuit schematics
 - Schematic of AC-sweep simulation in 2(b)
 - Schematic of time-domain simulation in 3(a)
 - ◆ PSpice verification results
 - Magnitude/phase Bode plots of filter in 2(b)
 - Time-domain waveforms of V_{out} in 3(a) and 3(b)
 - ◆ Discussion in 2(c) and 3(b)
- If you have re-designed a new op amp, your report should also include
 - ◆ Hand-calculation design procedure of the new op amp
 - ◆ Diagrams for verifying A_0 , f_t , PM, SR⁺, and SR⁻ of the new op amp

Notes (Cont.)

- When verifying your hand calculation by PSpice
 - ◆ 軟體安裝方式與使用介紹請參考Homework1的PSpice Tutorial
 - ◆ Correct the value of LAMBDA for NMOS0P5 to 0.1 (the same as on pp. B-9 of Appendix B in Sedra's CD)
 - ◆ Use 4-terminal MOSFET models (NMOS0P5_BODY and PMOS0P5_BODY)
- Upload your report to **MOODLE** in **Word** format
 - ◆ **Deadline: 23:59:59 on 2023/11/20 (Mon.)** (不接受作業補交)
 - ◆ Filename example: HW3_鄭聿程_E2408XXXX_v1.doc (如更新請用v2, v3, ...)
 - ◆ Word format請參考Homework1, Homework2的Notes
- Others
 - ◆ 請勿抄襲，抄襲等同考試作弊，將依校規處理
 - ◆ 完成此次作業加學期總成績之1% (bonus)
 - ◆ 作業若遇到問題，可於下列時段至奇美樓95304室與助教討論
 - 原定office hours：每週一17:00~18:00 and 每週五16:00~17:00
 - 新增時段：2023/11/09(Thu.) and 2023/11/16(Thu.) 14:00~15:00
 - ◆ 請注意手算過程之掃描圖檔務必清晰並轉正以利助教判讀